

CPE201

Digital Design

By Benjamin Haas

Class 22: Shift Registers 2



Outline

- Shift Register Counters
 - Johnson Counter
 - Ring Counter
- Shift Register Applications
- Troubleshooting



Shift Register Counter

- Output is connected back to input
 - Are also considered counters (Ch9)
- Have a specified sequence of states




Johnson Counter

- Creates a clock frequency that is 2^n slower than CLK
 - n is the number of bits in the counter
- Ex: if CLK is 1MHz and the counter has 5 bits
 - Johnson counter freq = $1\text{MHz}/(2^5) = 100\text{kHz}$



Circuit

 


Four-bit Johnson counter

Four-bit Johnson sequence.

Clock Pulse	Q_0	Q_1	Q_2	Q_3
0	0	0	0	0
1	1	0	0	0
2	1	1	0	0
3	1	1	1	0
4	1	1	1	1
5	0	1	1	1
6	0	0	1	1
7	0	0	0	1

Five-bit Johnson sequence.


Clock Pulse	Q_0	Q_1	Q_2	Q_3	Q_4
0	0	0	0	0	0
1	1	0	0	0	0
2	1	1	0	0	0
3	1	1	1	0	0
4	1	1	1	1	0
5	1	1	1	1	1
6	0	1	1	1	1
7	0	0	1	1	1
8	0	0	0	1	1
9	0	0	0	0	1

 


Five-bit Johnson counter

Signal Example

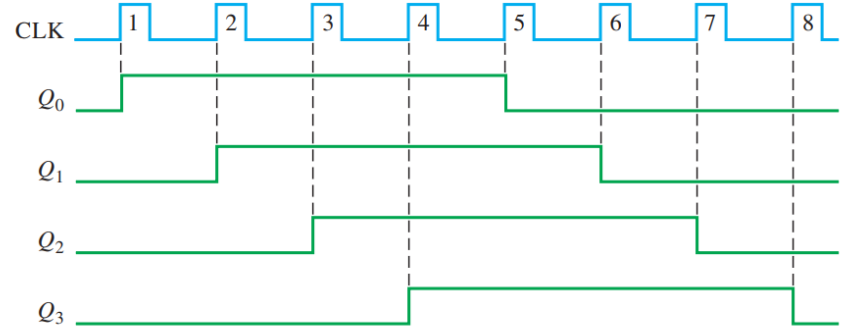- Measure output i one spot
- No signal setup required



 Timing sequence for a 4-bit Johnson counter.



Timing sequence for a 5-bit Johnson counter.


Ring Counter

- Like a Johnson counter, but with any bit pattern
- The pattern continuously goes through all flip-flops and then back to the beginning



Circuit

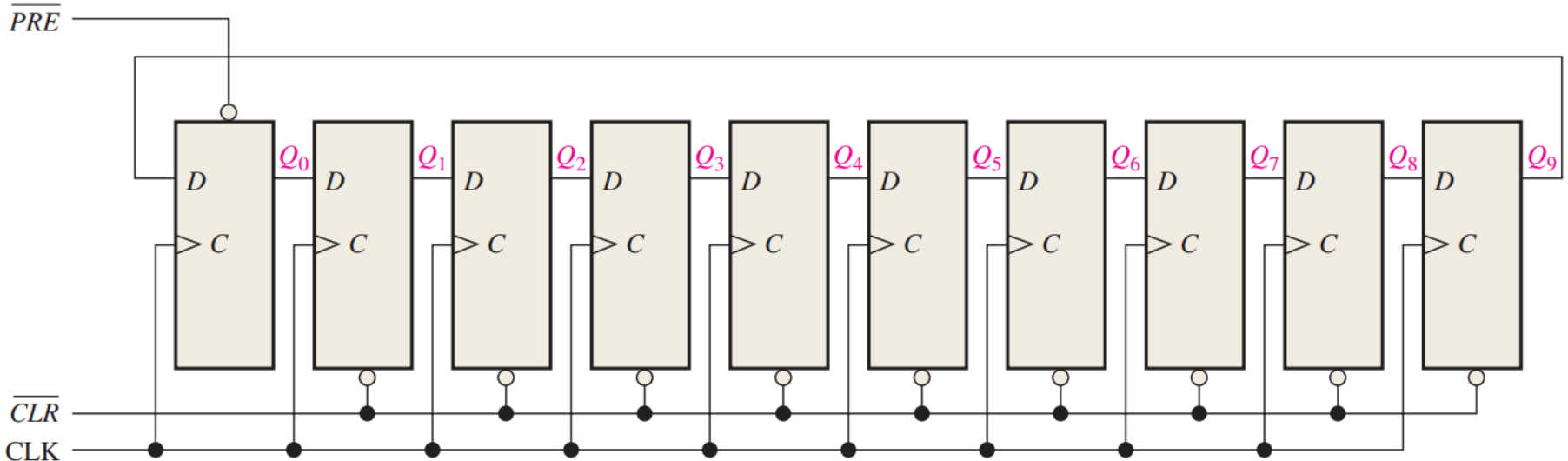- No use of Q'
- Use Preset to insert bit sequence



Logic Table

- Read any flip-flop output to watch the sequence


Ten-bit ring counter sequence.

Clock Pulse	Q_0	Q_1	Q_2	Q_3	Q_4	Q_5	Q_6	Q_7	Q_8	Q_9
0	1	0	0	0	0	0	0	0	0	0
1	0	1	0	0	0	0	0	0	0	0
2	0	0	1	0	0	0	0	0	0	0
3	0	0	0	1	0	0	0	0	0	0
4	0	0	0	0	1	0	0	0	0	0
5	0	0	0	0	0	1	0	0	0	0
6	0	0	0	0	0	0	1	0	0	0
7	0	0	0	0	0	0	0	1	0	0
8	0	0	0	0	0	0	0	0	1	0
9	0	0	0	0	0	0	0	0	0	1



Signal Example

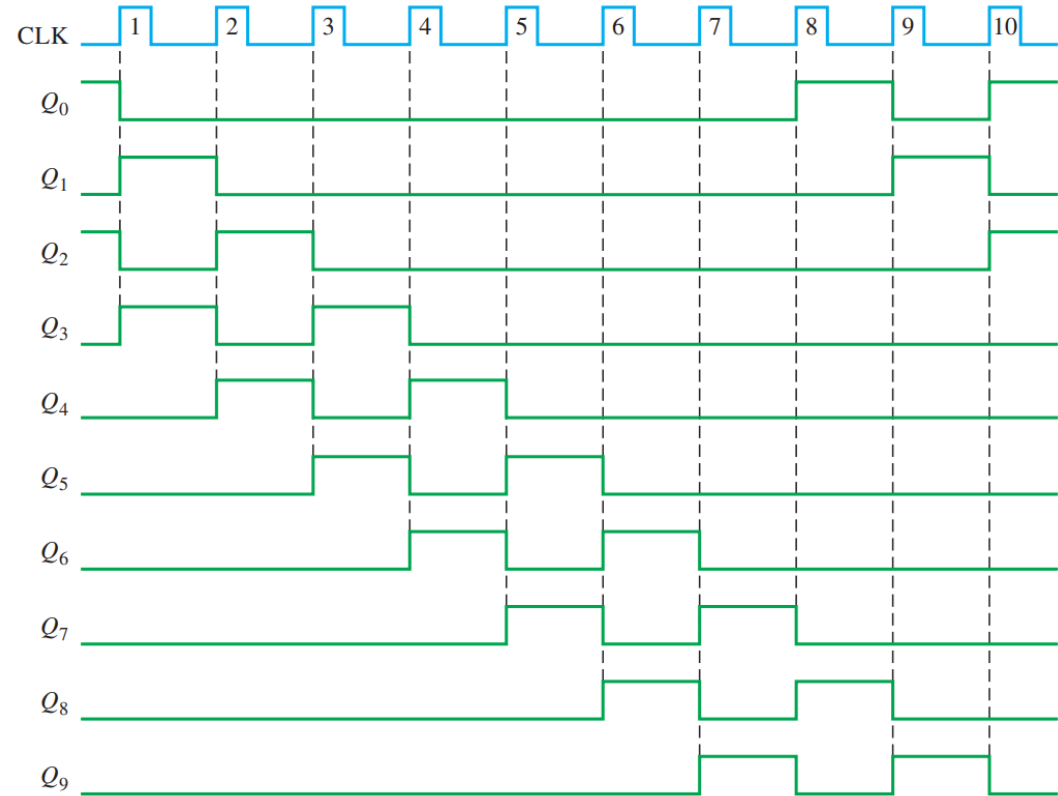- Needs PRE' on CLK 1 & 3 to set the seq – You set that up externally




Applications

- Time Delay
- Serial to Parallel Converter
- UART Transmitter
- Keyboard Encoder




Time Delay

 
- Insert a delay into some signals
 - Allow for setup time on a part w/o delaying



Another Option

 

* Data shifts from Q_0 toward Q_7 .


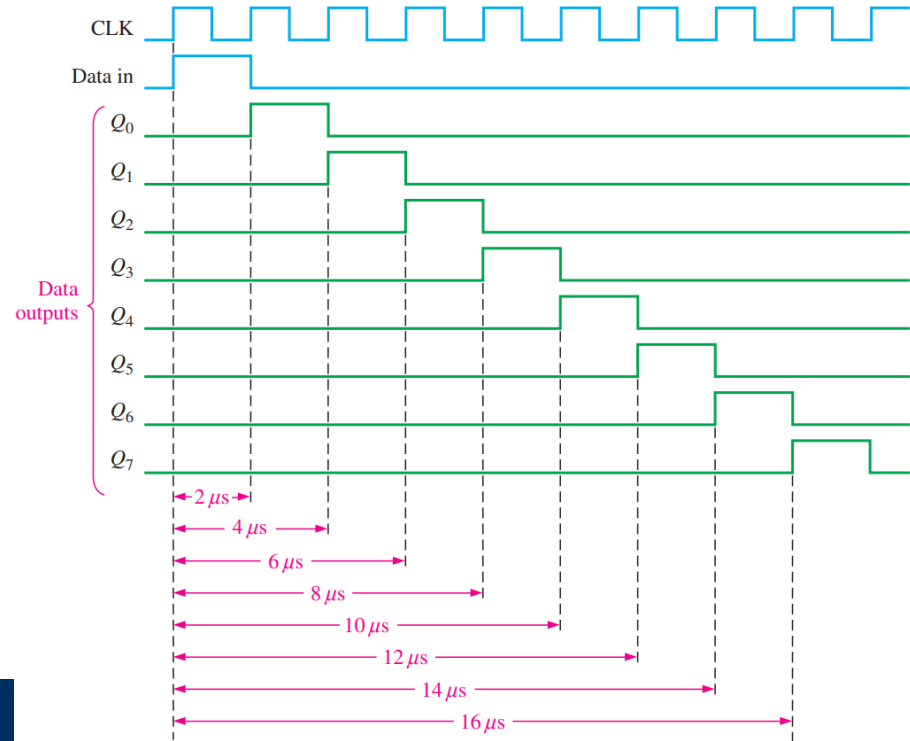


Serial to Parallel Converter

- Serial is one line
 - Connection count is small and takes little space
- Parallel is one line per bit
 - Very fast because all bits are xferred at once
 - Takes up much more space than serial




Serial to Parallel Converter

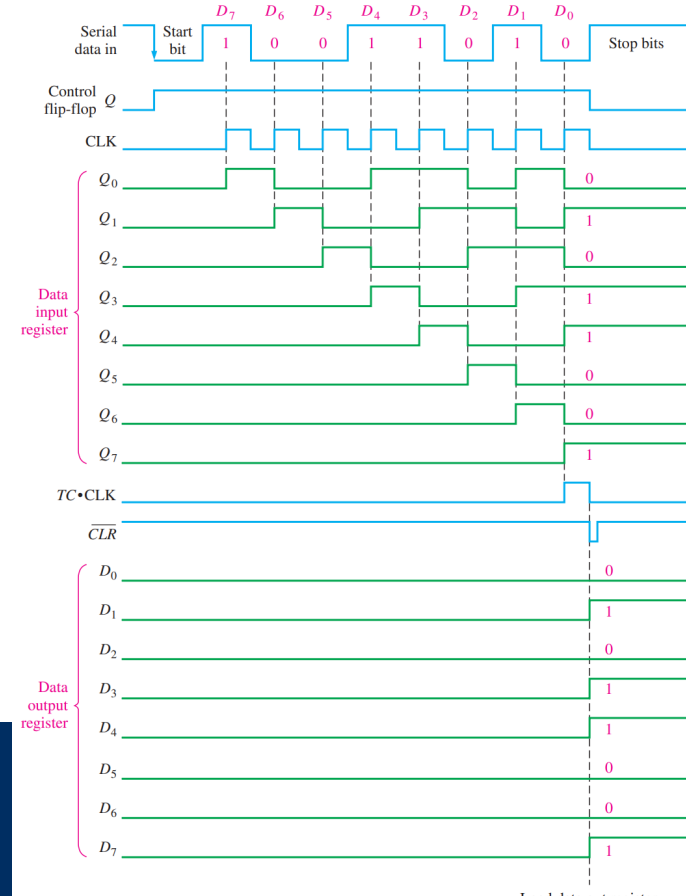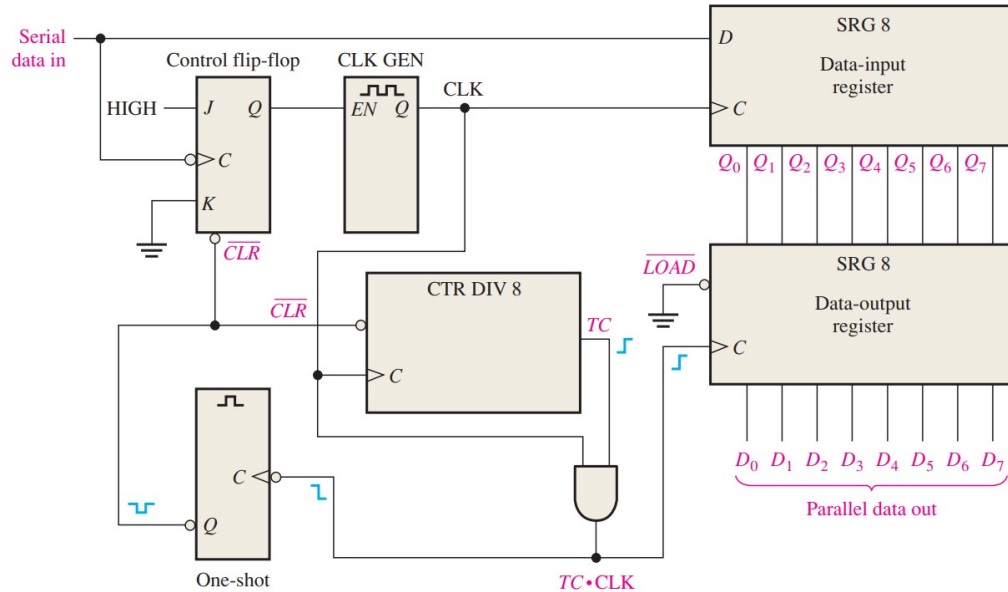

UART




 - Universal Asynchronous Receiver Transmitter
 - Full Duplex (RX and TX as same time)
 - Asynchronous (no cl
 - Serial data xfer
 - Low overhead



UART


- PISO transmit / SIPO receive

 

Keyboard Encoder

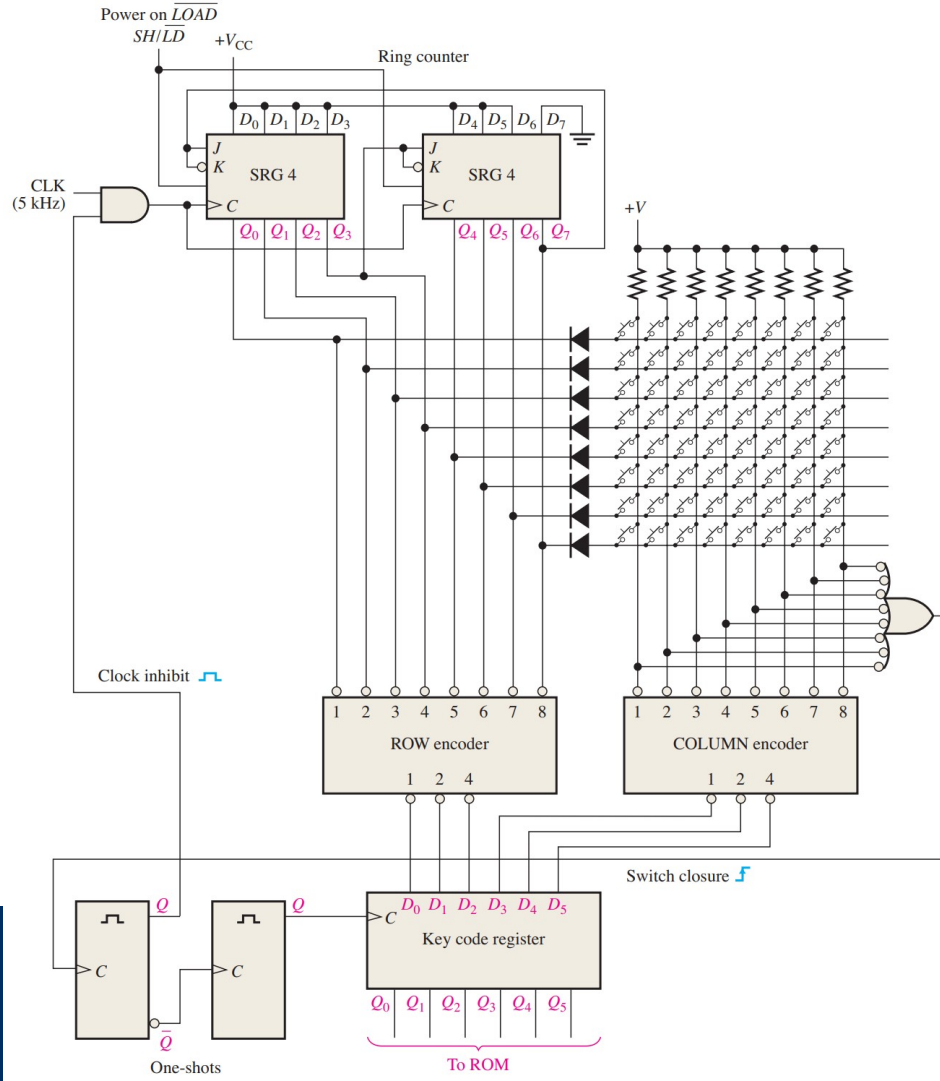- Get key press data to send over USB to computer
 - Simplified with no key press memory buffer
- Scans for pressed keys
- Encodes key presses and stores for TX
- Debounces a key press






Real Chip – 74HC194

- Universal shift reg

Do nothing:	$S_0 = 0, S_1 = 0$	(mode 0)
Shift right:	$S_0 = 1, S_1 = 0$	(mode 1, as in 1, 4D)
Shift left:	$S_0 = 0, S_1 = 1$	(mode 2, as in 2, 4D)
Parallel load:	$S_0 = 1, S_1 = 1$	(mode 3, as in 3, 4D)

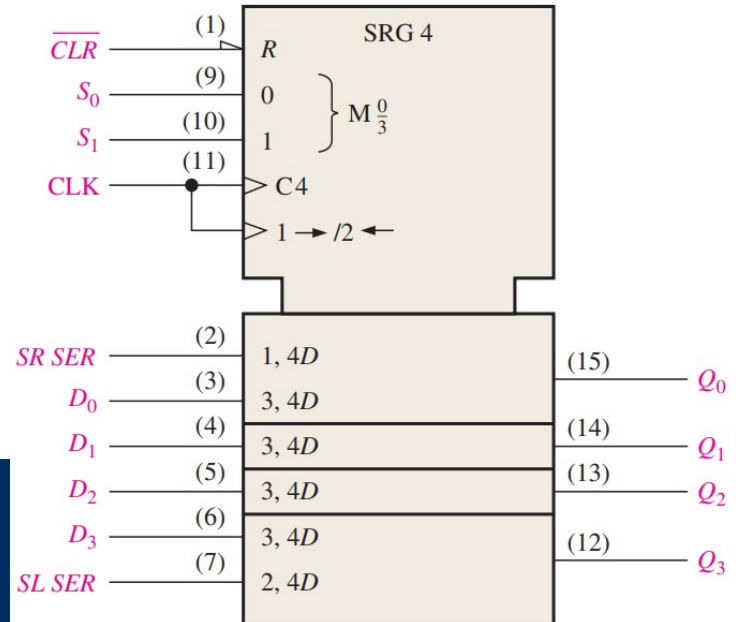


Exercising a Circuit

- Put all parts of the circuit through all possible states
 - Tests all chips for working status
 - Tests all circuit connections
 - More complicated with more memory parts or complexity



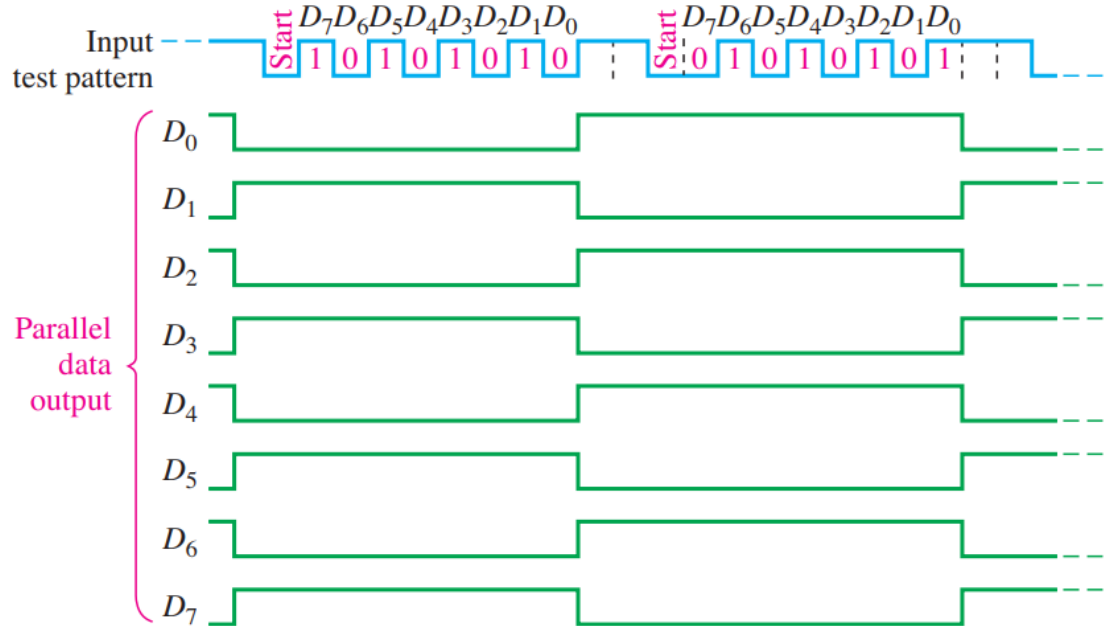Example (SIPO Test)

- Using circuit from Serial to Parallel Converter example



Reading

- This lecture
 - Sections 8.4-8.7
- Next lecture
 - 9.1-9.4

