

Chapter 10

Sinusoidal Steady-State Analysis (Problems)


Example 10.2-1

- Consider the voltages $v_1 = 10\cos(200t+45^\circ)$ V and $v_2 = 8\sin(200t+15^\circ)$ V. Determine the time by which $v_2(t)$ is advanced or delayed with respect to $v_1(t)$.

$$\sin(\omega t) = \cos(\omega t - 90^\circ) = \cos\left(\omega t - \frac{\pi}{2}\right)$$

$$\cos(\omega t) = \sin(90^\circ - \omega t) = \sin\left(\frac{\pi}{2} - \omega t\right)$$
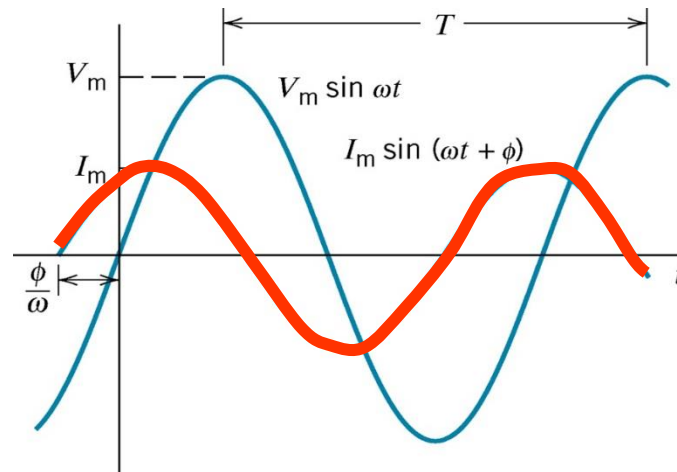
$$\sin(\omega t + 180^\circ) = -\sin(\omega t)$$



Current **leads** the voltage OR Voltage **lags** the current

Example 10.2-1 Solution

$$v_2 = \sin(200t + 15^\circ)$$

$$v_2 = 8 \cos(200t + 15^\circ - 90^\circ) = 8 \cos(200t - 75^\circ) V$$

$$\theta_2 - \theta_1 = -75^\circ - 45^\circ = -120^\circ = -\frac{\pi}{3} \text{ rad}$$

$$\frac{\phi}{\omega} = -\frac{\frac{\pi}{3}}{200} = -5.2 \text{ ms}$$

$$\theta_2 - \theta_1 < 0$$

This indicates a delay (lag)

Example 3

- Transform the current expression in time domain $i(t) = 5\sin(100t+120^\circ)$ to the frequency domain.

$$\sin(\omega t) = \cos(\omega t - 90^\circ) = \cos\left(\omega t - \frac{\pi}{2}\right)$$

$$\cos(\omega t) = \sin(90^\circ - \omega t) = \sin\left(\frac{\pi}{2} - \omega t\right)$$

$$\sin(\omega t + 180^\circ) = -\sin(\omega t)$$

Example 3 Solution

$$i(t) = 5 \sin(100t + 120^\circ)$$

$$[\sin(\omega t) = \cos(\omega t - 90^\circ)]$$

$$= 5 \cos(100t + 120^\circ - 90^\circ)$$

$$= 5 \cos(100t + 30^\circ)$$

$$i(t) = \operatorname{Re}\{5 e^{j100t} e^{j30^\circ}\} \Leftarrow$$

$$I = 5 e^{j30^\circ} = 5 \angle 30^\circ$$

Example 4

- Transform the voltage expression in frequency domain $V = 24 \angle 125^\circ$ to time domain.

$$\sin(\omega t) = \cos(\omega t - 90^\circ) = \cos\left(\omega t - \frac{\pi}{2}\right)$$

$$\cos(\omega t) = \sin(90^\circ - \omega t) = \sin\left(\frac{\pi}{2} - \omega t\right)$$

$$\sin(\omega t + 180^\circ) = -\sin(\omega t)$$

Example 4 Solution

$V = 24 \angle 125^\circ$ to time domain.

$$v(t) = \text{Re} \{ 24 \cdot e^{j\omega t} \cdot e^{j125^\circ} \}$$

$$= 24 \cos \left(\underbrace{\omega t}_{\uparrow} + 125^\circ \right)$$

Example 10.3-2

Consider the phasors

$$\mathbf{V}_1 = 4.25 \angle 115^\circ \text{ and } \mathbf{V}_2 = -4 + j3$$

Convert \mathbf{V}_1 to rectangular form and \mathbf{V}_2 to polar form.

Polar to rectangular

$$x = r \cos \phi$$

$$y = r \sin \phi$$

$$z = r(\cos \phi + j \sin \phi)$$

Rectangular to polar

$$r = \sqrt{x^2 + y^2} \quad \phi = \tan^{-1} \frac{y}{x}$$

$$z = \sqrt{x^2 + y^2} \angle \tan^{-1} \frac{y}{x}$$

Example 10.3-2 Solution

EX 10.3-2

$$V_1 = 4.25 \angle 115^\circ$$

$$V_2 = -4 + j3$$

Rectangular

$$x = r \cos \phi$$

$$y = r \sin \phi$$

$$V_1 \Rightarrow \begin{cases} 4.25 \cos 115^\circ = -1.796 \\ 4.25 \sin 115^\circ = 3.852 \end{cases}$$

$$V_1 = r(\cos \phi + j \sin \phi)$$

$$V_1 = -1.796 + j3.852$$

$$V_2 = -4 + j3$$

$$\begin{cases} r = \sqrt{x^2 + y^2} \\ \phi = \tan^{-1} y/x \end{cases}$$

$$V_2 =$$

$$r = \sqrt{(-4)^2 + (3)^2} = 5$$

$$\phi = \tan^{-1}(3/4) = -36.87^\circ = 143^\circ$$

$$V_2 = 5 \angle 143^\circ$$

Example 10.3-3

Consider the phasors

$$\mathbf{V}_1 = -1.796 + j3.852 = 4.25 \angle 115^\circ \text{ and } \mathbf{V}_2 = -4 + j3 = 5 \angle 143^\circ$$

Determine $\mathbf{V}_1 + \mathbf{V}_2$, $\mathbf{V}_1 \cdot \mathbf{V}_2$ and $\frac{\mathbf{V}_1}{\mathbf{V}_2}$.

Addition and Subtraction of Complex Number (rectangular)

$$Z_1 + Z_2 = (x_1 + x_2) + j(y_1 + y_2)$$

$$Z_1 - Z_2 = (x_1 - x_2) + j(y_1 - y_2)$$

Multiplication/Division of Complex Number (polar)

$$Z_1 \cdot Z_2 = r_1 \cdot r_2 \angle (\phi_1 + \phi_2)$$

$$\frac{Z_1}{Z_2} = \frac{r_1}{r_2} \angle (\phi_1 - \phi_2)$$

Example 10.3-3 Solution

$$V_1 = -1.796 + j3.852 = 4.25 \angle 115^\circ$$

$$V_2 = -4 + j3 = 5 \angle 143^\circ$$

$$V_1 + V_2 = (-1.796 + j3.852) + (-4 + j3)$$

$$V_1 + V_2 = (-1.796 - 4) + j(3.852 + 3)$$

$$V_1 \cdot V_2 = (4.25 \angle 115^\circ) \cdot (5 \angle 143^\circ)$$

$$= (4.25 \cdot 5) \angle (115^\circ + 143^\circ)$$

$$= 21.25 \angle \cancel{258^\circ} - 360^\circ$$

$$= 21.25 \angle -102^\circ$$

$$\frac{V_1}{V_2} = \frac{4.25 \angle 115^\circ}{5 \angle 143^\circ} = \left(\frac{4.25}{5} \right) \angle 115^\circ - 143^\circ$$

$$= 0.85 \angle -28^\circ$$

Example 10.3-4 – Kirchhoff's Law for AC Circuits

The input to the circuit shown in Figure 10.3-3 is the voltage source voltage,

$$v_s(t) = 25 \cos(100t + 15^\circ) \text{ V}$$

The output is the voltage across the capacitor,

$$v_C(t) = 20 \cos(100t - 22^\circ) \text{ V}$$

Determine the resistor voltage $v_R(t)$.

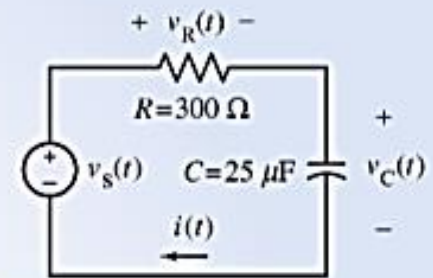


FIGURE 10.3-3 The circuit in Example 10.3-4

Addition and Subtraction of Complex Number (rectangular)

$$Z_1 + Z_2 = (x_1 + x_2) + j(y_1 + y_2)$$

$$Z_1 - Z_2 = (x_1 - x_2) + j(y_1 - y_2)$$


Multiplication/Division of Complex Number (polar)

$$Z_1 \cdot Z_2 = r_1 \cdot r_2 \angle(\phi_1 + \phi_2)$$

$$\frac{Z_1}{Z_2} = \frac{r_1}{r_2} \angle(\phi_1 - \phi_2)$$

Example 10.3-4 Solution

Ex 10.3-4

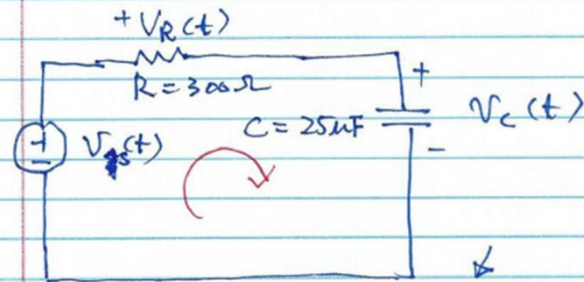

$$v_s(t) = 25 \cos(100t + 15^\circ) \text{ V} = 25 \angle 15^\circ$$

$$v_C(t) = 20 \cos(100t - 22^\circ) \text{ V} = 20 \angle -22^\circ$$

$$v_R(t) = ?$$

$$-v_s + v_R + v_C = 0. \quad v_R = v_s - v_C$$

KVL

$$\begin{aligned} v_R(t) &= v_s(t) - v_C(t) \\ &= 25 \cos(100t + 15^\circ) \\ &\quad - 20 \cos(100t - 22^\circ) \end{aligned}$$

$$V_R(\omega) = V_s(\omega) - V_C(\omega)$$

$$= 25 \angle 15^\circ - 20 \angle -22^\circ$$

$$= (24.15 + j6.47) - (18.54 - j7.49)$$

$$= (24.15 - 18.54) + j(6.47 + 7.49)$$

$$= 5.61 + j13.96$$

$$= 15 \angle 68.1^\circ \text{ V}$$


$$v_R(t) = 15 \cos(100t + 68.1^\circ)$$

Example 10.4-1

The input to the AC circuit shown below is the source voltage

$$v_s(t) = 12 \cos(1000t + 15^\circ) \text{ V}$$

Determine (a) the impedances of the capacitor, inductor, and resistance and (b) the current $i(t)$

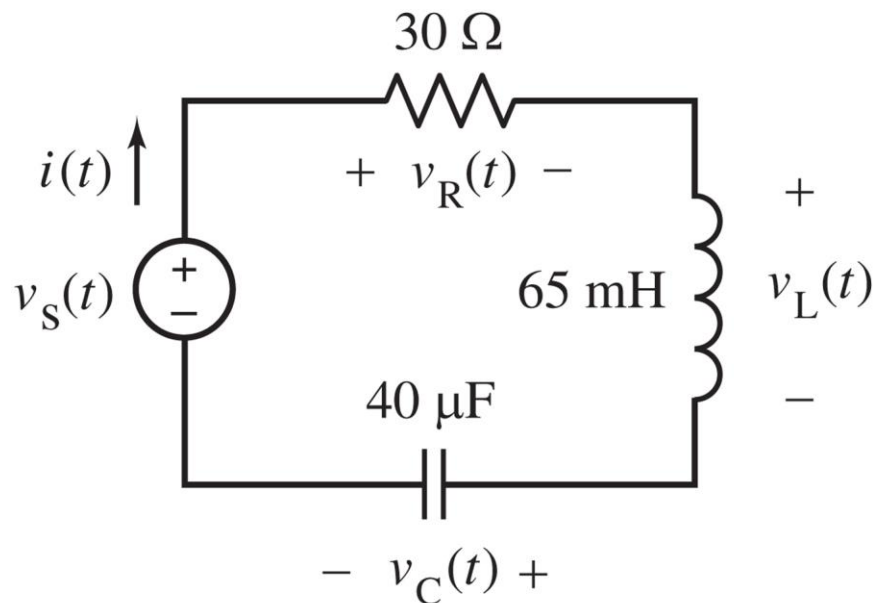

Example 10.4-1 Solution

- (a) The input frequency is $\omega = 1000$ rad/s. Using Eq. 10.4-4 shows that the impedance of the capacitor is

Example 10.4-1.

$$Z_C(\omega) = \frac{1}{j\omega C} = \frac{1}{j1000(40 \times 10^{-6})} = \frac{25}{j} = -j25 \ \Omega$$

Using Eq. 10.4-6 shows that the impedance of the inductor is

$$Z_L(\omega) = j\omega L = j1000(0.065) = j65 \ \Omega$$

Using Eq. 10.4-8, the impedance of the resistor is

$$Z_R(\omega) = R = 30 \ \Omega$$

- (b) Apply KVL to write

$$12 \cos(1000t + 15^\circ) = v_R(t) + v_L(t) + v_C(t)$$

Using phasors, we get

$$12 \angle 15^\circ = \mathbf{V}_R(\omega) + \mathbf{V}_L(\omega) + \mathbf{V}_C(\omega) \quad (10.4-10)$$

Using Eqs. 10.4-5, 10.4-7, and 10.4-9, we get

$$12 \angle 15^\circ = 30 \mathbf{I}(\omega) + j65 \mathbf{I}(\omega) - j25 \mathbf{I}(\omega) = (30 + j40) \mathbf{I}(\omega) \quad (10.4-11)$$


Solving for $\mathbf{I}(\omega)$ gives

$$\mathbf{I}(\omega) = \frac{12 \angle 15^\circ}{30 + j40} = \frac{12 \angle 15^\circ}{50 \angle 53.13^\circ} = 0.24 \angle -38.13^\circ \text{ A}$$

The corresponding sinusoid is

$$i(t) = 0.24 \cos(1000t - 38.13^\circ) \text{ A}$$

Example 7

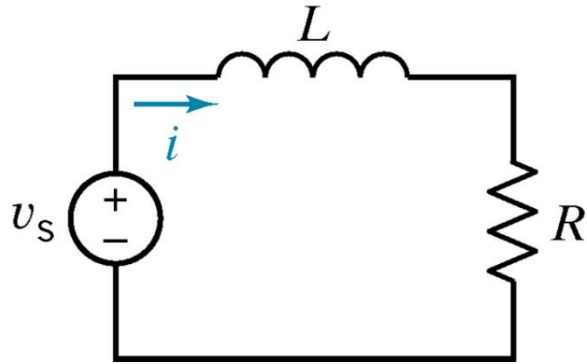

$$\omega = 100 \text{ rad/s}, R = 200 \Omega, L = 2 \text{ H}, v(t) = V_m \cos \omega t \text{ V}$$


$$i = ?$$

$$I = \frac{V}{j\omega L + R} = \frac{V_m \angle 0^\circ}{j \times 100 \times 2 + 200} = \frac{V_m \angle 0^\circ}{j \times 200 + 200} = \frac{V_m \angle 0^\circ}{283 \angle 45^\circ} = \frac{V_m \angle -45^\circ}{283}$$


$$\Rightarrow i(t) = \frac{V_m}{283} \cos(100t - 45^\circ)$$

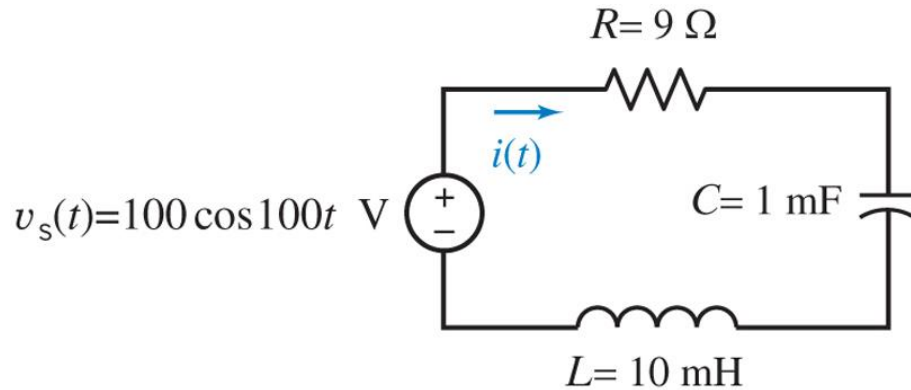Example 10.5-1 – KVL

- Determine the steady state current $i(t)$ using phasor and impedances



(a)

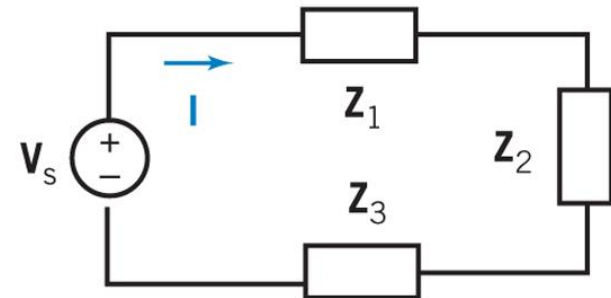


(b)

Example 10.5-1 Solution

example 10.5 -1.

Determine the steady state current $i(t)$ using phasor and impedances.

$$R = 9\Omega = 9\Omega$$

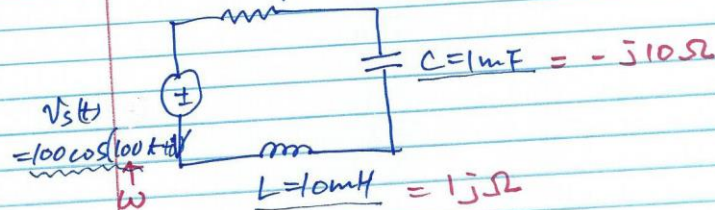

$$\begin{aligned} Z_R &= R = 9\Omega \\ Z_C &= \frac{1}{j\omega C} = \frac{1}{j \cdot 100 \cdot 10^{-3}} = \frac{j}{-100 \cdot 10^{-3}} = -j10\Omega \\ Z_L &= j\omega L = j \cdot 100 \cdot 10^{-2} = j1\Omega \\ V &= 100 \angle 0^\circ \text{ V} \end{aligned}$$

$$V = I \cdot Z, \quad I = \frac{V}{Z} = \frac{100 \angle 0^\circ}{9 - j10 + j1} = \frac{100 \angle 0^\circ}{9 - j9}$$

$$(\sqrt{9^2 + (-9)^2}) = 12.7, \quad \tan^{-1}(-9/9) = -45^\circ$$


$$\begin{aligned} I &= \frac{100 \angle 0^\circ}{12.7 \angle -45^\circ} = \frac{100}{12.7} \angle 0 - (-45^\circ) \\ &= 7.86 \angle 45^\circ \text{ (A)} \end{aligned}$$

$$\underline{i(t)} = \underline{7.86 \cos(100t + 45^\circ) \text{ (A)}}$$

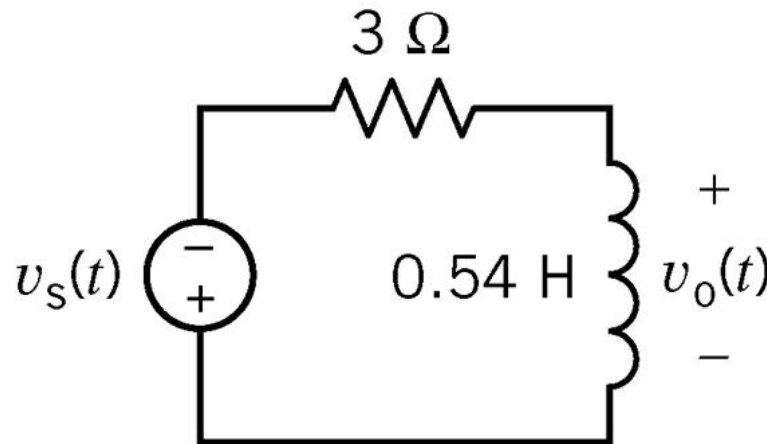Example 10.5-2 – Voltage Division


- Determine the steady-state output voltage, $v_o(t)$ if the source voltage is:

$$v_s(t) = 7.28 \cos(4t + 77^\circ) \text{ V}$$



(a)

Example 10.5-2 Solution

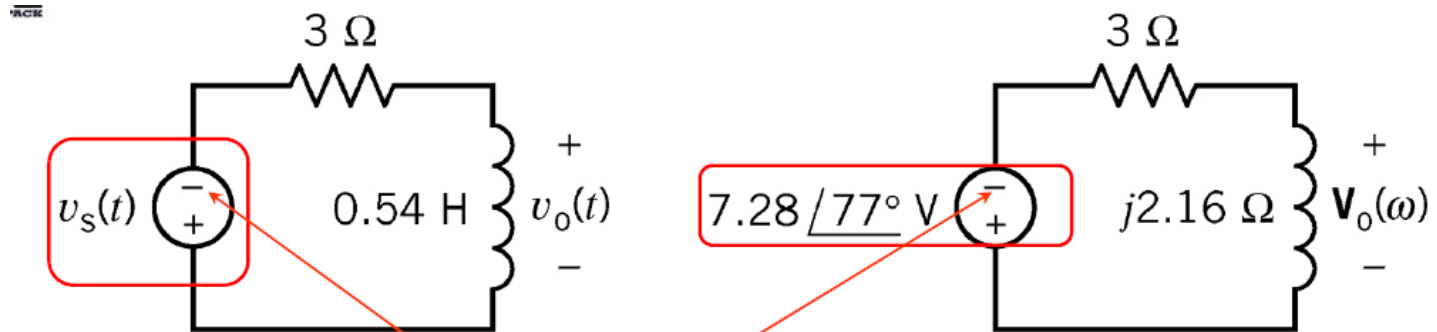

When you use voltage division, you have to be careful with the direction:

$$V_o = -V_s \cdot Z_{0.54H} / (Z_{3\Omega} + Z_{0.54H})$$

$$\begin{aligned} V_o &= -7.28 \angle 77^\circ \times \frac{j4 \times 0.54}{3 + j4 \times 0.54} = -7.28 \angle 77^\circ \times \frac{j2.16}{3 + j2.16} \\ &= e^{j180^\circ} \times 7.28 \times e^{j77^\circ} \times \frac{2.16 \times e^{j90^\circ}}{3 + j2.16} \\ &= \frac{7.28 \times 2.16}{3 + j2.16} \times e^{j180^\circ} \times e^{j77^\circ} \times e^{j90^\circ} \\ &= \frac{7.28 \times 2.16}{3 + j2.16} e^{j(180+77+90)} = \frac{7.28 \times 2.16}{3.70 \times e^{j36^\circ}} e^{j(180+77+90)} \\ &= \frac{7.28 \times 2.16}{3.70} e^{j(180+77+90-36)} \end{aligned}$$

Example 10.5-3 – KVL


The input to the circuit is the voltage of the voltage source:

$$v_s(t) = 7.68 \cos(2t + 47^\circ) \text{ V}$$


The output is the voltage across the resistor:

$$v_o(t) = 1.59 \cos(2t + 125^\circ)$$

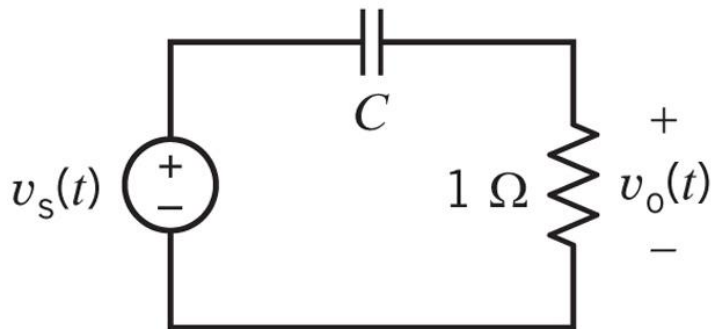Determine capacitance C of the capacitor.



(a)

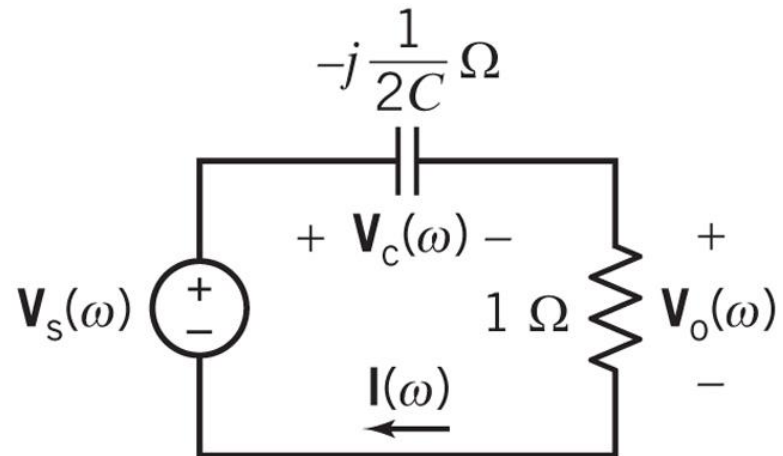


(b)

Example 10.5-3 Solution

Example 10.5-3

$$v_s(t) = 7.68 \cos(2t + 47^\circ) \text{ V} \quad v_o(t) = 1.59 \cos(2t + 125^\circ)$$

Determine capacitance C of the capacitor

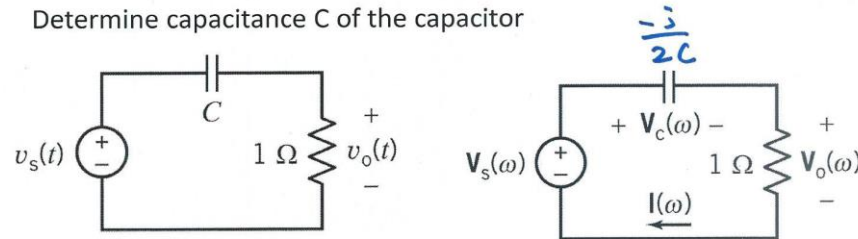

$$Z_c = \frac{1}{j\omega C} = \frac{j \times 1}{j \times j\omega C} = -\frac{j}{\omega C} = -\frac{j}{2C} \Omega$$

$$Z_R = R = 1 \Omega, \quad V_S = 7.68 \angle 47^\circ, \quad V_O = 1.59 \angle 125^\circ$$

$$I = \frac{V_O}{R} = \frac{1.59 \angle 125^\circ}{1} = 1.59 \angle 125^\circ \text{ (A)}$$

$$\text{KVL } V_C = V_S - V_O = 7.68 \angle 47^\circ - 1.59 \angle 125^\circ$$

$$\begin{aligned} \text{Convert to Rect. } & m(\cos\theta + j\sin\theta) \\ &= (5.23 + j5.62) - (-0.91 + j1.3) \\ &= (5.23 + 0.91) + (j5.62 - j1.3) \\ &= 6.14 + j4.32 = 7.51 \angle 35^\circ \text{ (V)} \end{aligned}$$


The impedance of capacitor

$$-\frac{j}{2C} = \frac{V_C}{I} = \frac{7.51 \angle 35^\circ}{1.59 \angle 125^\circ} = \frac{4.72 \angle -90^\circ}{1 \angle -90^\circ}$$

$$\begin{aligned} C &= \frac{-j1}{2(4.72 \angle -90^\circ)} = \frac{1 \angle -90^\circ}{2(4.72 \angle -90^\circ)} \\ &= 0.106 \text{ F} \end{aligned}$$

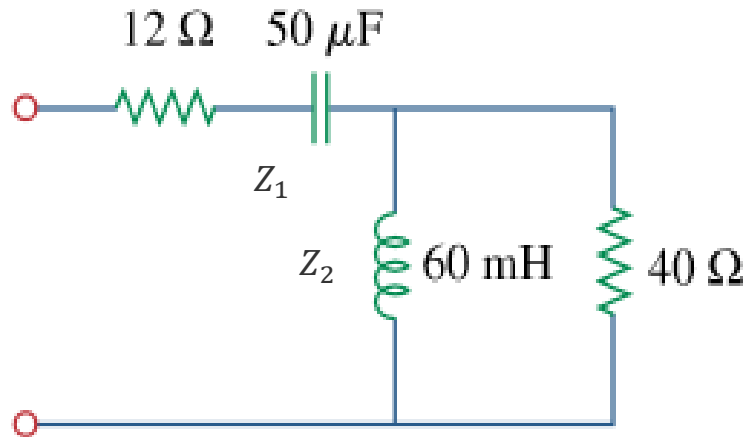Example 8 – Z_{eq}

- At $\omega = 377 \text{ rad/s}$, find the input impedance of the circuit.




$$\text{R: } Z = R$$

$$\text{L: } Z = j\omega L$$

$$\text{C: } Z = -j \frac{1}{\omega C}$$

Example 8 Solution

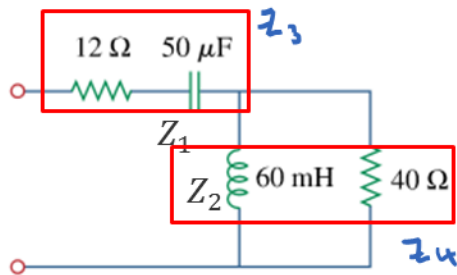

$$Z_1 = -j \frac{1}{(377) \cdot (50 \times 10^{-6})} = -j 53.1\ \Omega$$

$$Z_2 = j(377) \cdot (60 \times 10^{-3}) = j 22.6\ \Omega$$

$$Z_3 = 12\ \Omega + (-j 53.1\ \Omega)$$


$$Z_3 = 12 - j 53.1\ \Omega$$

$$Z_4 = \frac{(40\ \Omega)(j 22.6\ \Omega)}{(40\ \Omega) + (j 22.6\ \Omega)} = 9.7 + j 17.1\ \Omega$$

$$\begin{aligned} Z_{eq} &= Z_3 + Z_4 = (12 - j 53.1) + 9.7 + j 17.1 \\ &= 21.7 - j 36 \end{aligned}$$

Example 9 – Mesh Analysis

- Calculate i_o

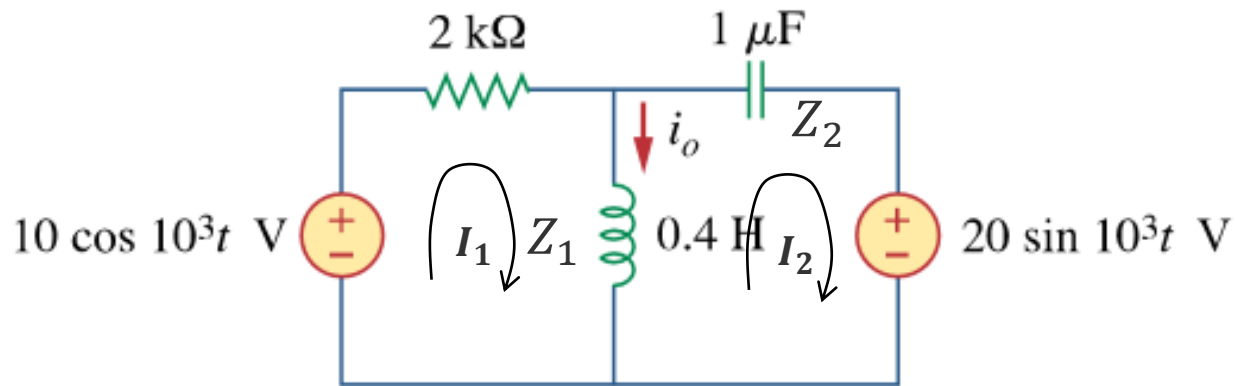

$$\sin(\omega t) = \cos(\omega t - 90^\circ) = 1 \angle -90^\circ = -1j$$

Example 9 Solution

$$\omega = 1000 \text{ rad/s}$$

$$Z_1 = j\omega L = j400$$

$$Z_2 = -j\frac{1}{\omega C} = -j\frac{1}{(10^3)(10^{-6})} = -j1000$$

Mesh analysis


$$I_1 - I_o - I_2 = 0 \quad I_o = I_1 - I_2 \quad (\text{KCL})$$

$$-10 + 2000I_1 + j400(I_1 - I_2) = 0$$

$$-10 + (2000 + j400)I_1 - j400I_2 = 0$$


$$j400(I_2 - I_1) - j1000I_2 - 20j = 0$$

$$+ j400I_1 + (-600j)I_2 - 20j = 0$$

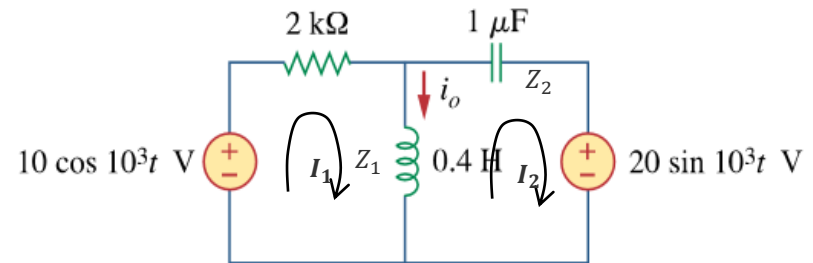


Example 10.6-2 – Mesh Analysis

- Determine the mesh currents for the circuit shown below.

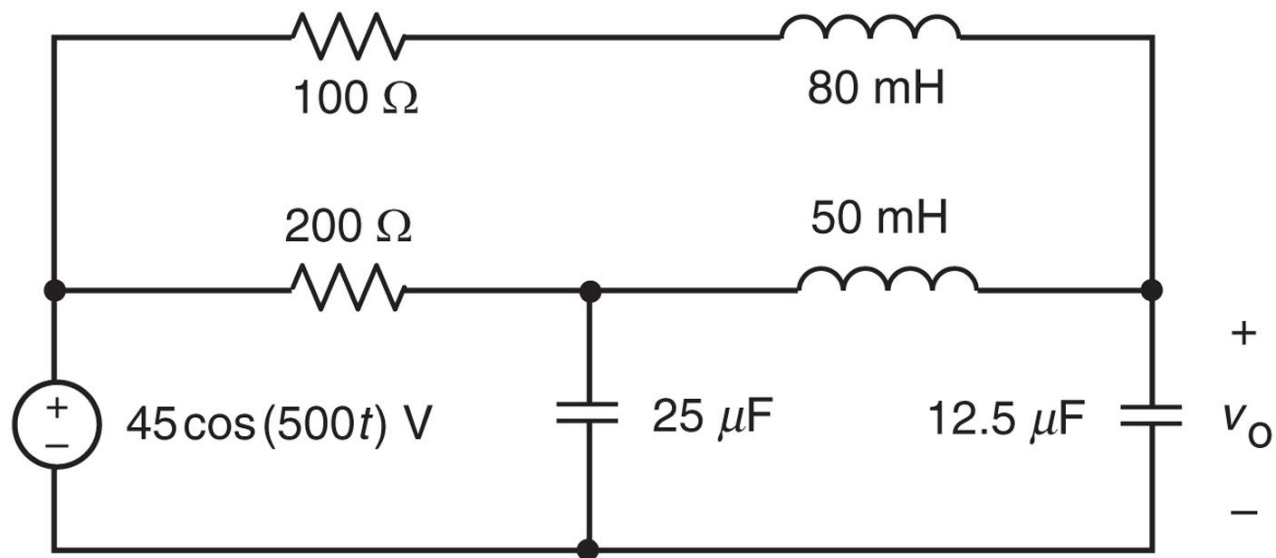

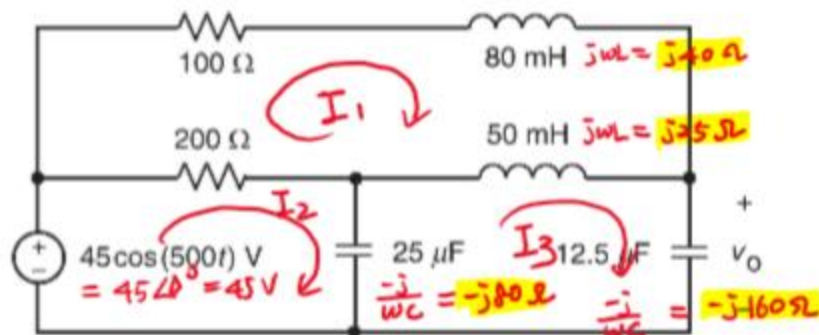Example 10.6-2

Determine the mesh currents for the circuit shown in the figure



$$100 \cdot I_1 + j40 \cdot I_1 + j25(I_1 - I_3) + 200(I_1 - I_2) = 0 \quad \text{--- (1)}$$

$$-45 \angle 0^\circ + 200(I_2 - I_1) + (-j80)(I_2 - I_3) = 0 \quad \text{--- (2)}$$

$$-j80(I_3 - I_2) + j25(I_3 - I_1) + (-j160)(I_3) = 0 \quad \text{--- (3)}$$

$$\begin{bmatrix} 360 + j65 & -200 & -j25 \\ -200 & 200 - j80 & j80 \\ -25 & j80 & -j215 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 45 \\ 0 \end{bmatrix}$$

$$\begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 0.374 \angle 115^\circ \\ 0.575 \angle 25^\circ \\ 0.171 \angle 28^\circ \end{bmatrix}$$

Exercise 10.6-3 – Node Analysis

The input to the circuit shown in Figure 10.6-10 is the voltage source voltage

$$v_s(t) = 10 \cos(10t) \text{ V}$$

The output is the current $i(t)$ in resistor R_1 . Determine $i(t)$.


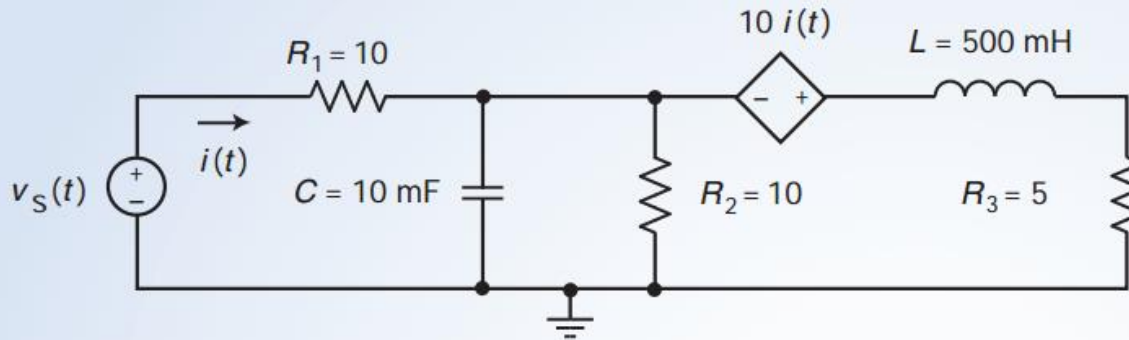


FIGURE
Example

Example 10.6-3 Solution

The output is the current $i(t)$ in resistor R_1 . Determine $i(t)$.

Node analysis.

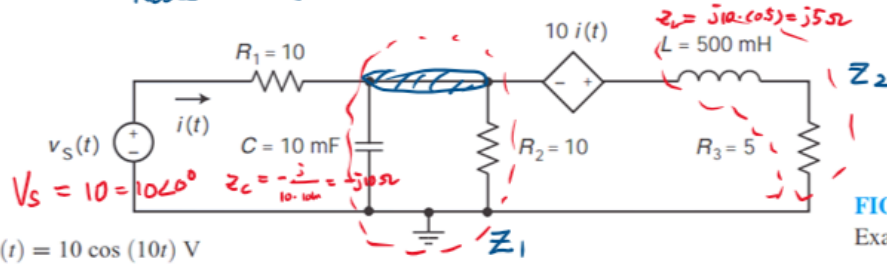


$$Z_1 = 10 \parallel -j10 = \frac{10 \cdot (-j10)}{10 - j10} = \frac{10 \cdot (-j10)(10 + j10)}{(10 - j10)(10 + j10)} = \frac{1000 - 1000j}{100 + 100}$$

$$= 5 - 5j \Omega$$

$$Z_2 = 5 + j5 \Omega$$

FIGURE
Example

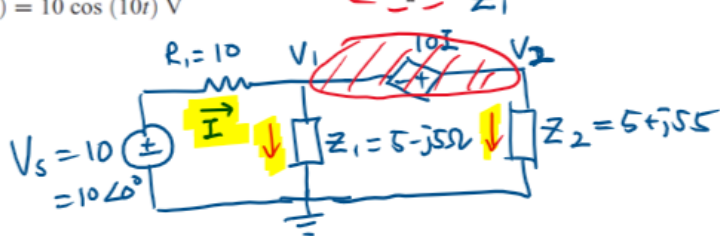

For Dep. source $\Rightarrow I = \frac{10 - V_1}{10}$

Supernode $V_2 - V_1 = 10 \cdot I$, $V_2 - V_1 = 10 \cdot \frac{10 - V_1}{10}$, $V_2 = 10$ or $10 \angle 0^\circ$

$$\frac{10 - V_1}{10} - \frac{V_1}{Z_1} - \frac{V_2}{Z_2} = 0$$

$$\frac{10 - V_1}{10} - \frac{V_1}{5 - j5} - \frac{10}{5 + j5} = 0$$

$$1 - \frac{V_1}{10} - \frac{V_1}{5 - j5} - (1 - j) = 0$$

$$-V_1 \left(\frac{1}{10} + \frac{1}{5 - j5} \right) = 1 + j$$


$$V_1 = \frac{-j \left(\frac{1}{10} + \frac{1}{5 - j5} \right)}{1 + j} = 2 + 4j$$

$$I = \frac{10 - (2 + 4j)}{10} = 0.89 \angle -26.6^\circ$$


$$i(t) = 0.89 \cos(10t - 26.6^\circ)$$

Exercise 10.7-2

- Determine the phasor representation of each circuit element. Calculate $v(t)$.

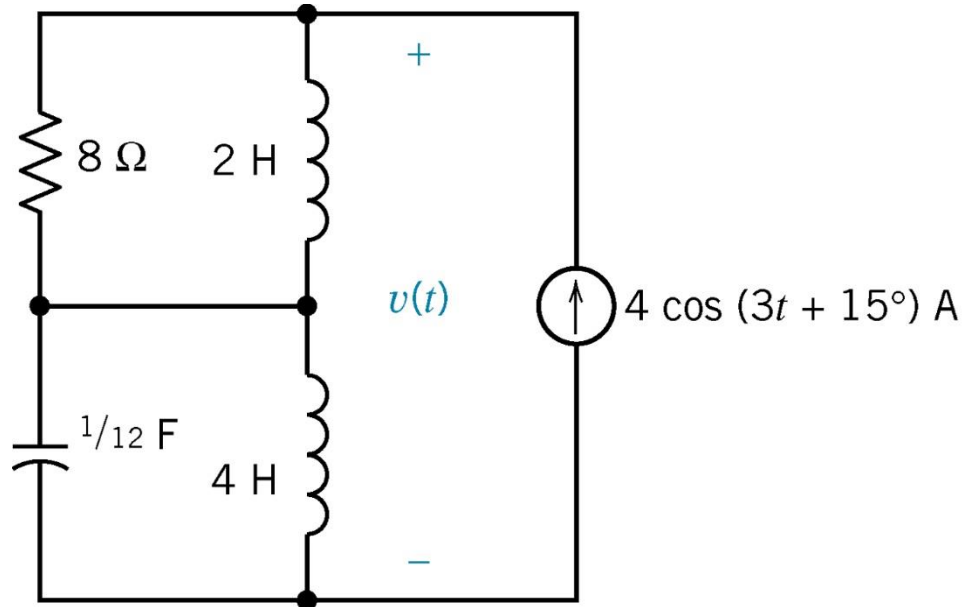


Exercise 10.7-2 Solution

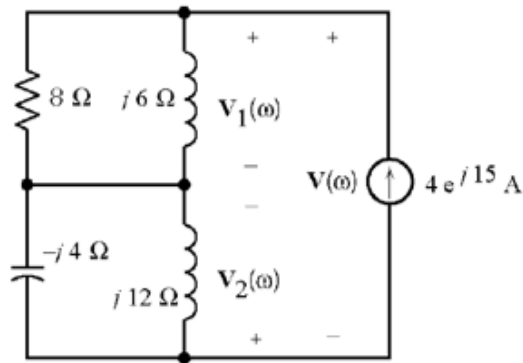

$v(t) =$

$$V_1 = \frac{8 \cdot j6}{8 + j6} \cdot 4 \angle 15^\circ = 19.2 \angle 68.7^\circ$$

Exercise 10.7-2

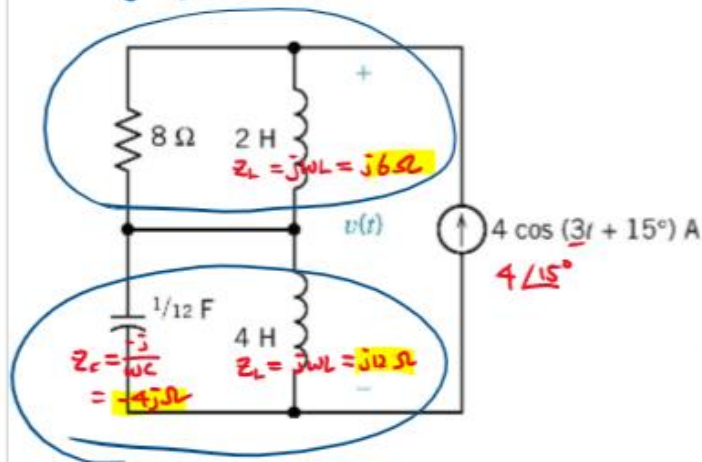

$$V_1 + V_2 = 19.2 \angle 68.7^\circ + 24 \angle -15^\circ$$

$$= 14.4 \angle -22^\circ$$

$$V_2 = \frac{j12(-j4)}{j12 - j4} \cdot 4 \angle 15^\circ = 24 \angle -15^\circ$$


$$v(t) = 14.4 \cos(3t - 22^\circ) \text{ [V]}$$

Example 10.6-4 – OpAmp

The input to the ac circuit shown in Figure 10.6-13 is the voltage source voltage

$$v_s(t) = 125 \cos(5000t + 15^\circ) \text{ mV}$$

Determine the output voltage $v_o(t)$.

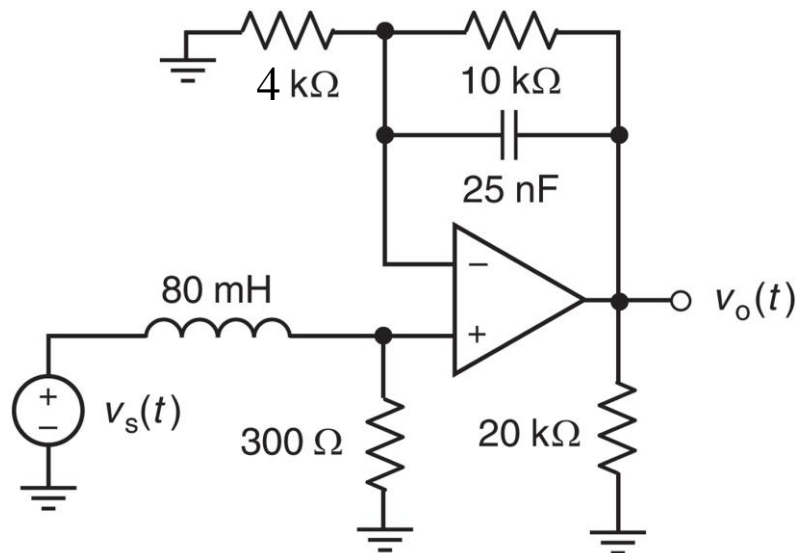

Example 10.6-4 Solution

Solution

The impedances of the capacitor and inductor are

$$Z_C = -j \frac{1}{5000(25 \times 10^{-9})} = -j8000 \, \Omega \text{ and } Z_L = j5000(80 \times 10^{-3}) = j400 \, \Omega$$

Figure 10.6-14 show the circuit represented in the frequency domain using phasors and impedances.

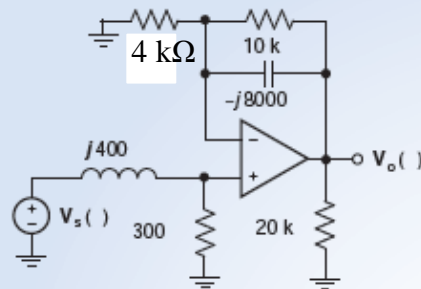


FIGURE 10.6-14 The frequency domain representation of the circuit from Figure 10.6-13.

Applying KCL at the noninverting node of the op amp, we get

$$\frac{V_s - V_a}{j400} = \frac{V_a}{300} + 0 \Rightarrow V_s = V_a \left(1 + \frac{j400}{300} \right)$$

Solving for V_a gives

$$V_a = \left(\frac{300}{300 + j400} \right) V_s = (0.6 \angle -53.1^\circ) (0.125 \angle 15^\circ) = 0.075 \angle -38.1^\circ \text{ V}$$

Next, apply KCL at the inverting node of the op amp to get

$$\frac{V_a}{4000} + \frac{V_a - V_o}{10,000} + \frac{V_a - V_o}{-j8000} = 0$$

Multiplying by 80,000 gives

$$0 = 20V_a + 8(V_a - V_o) + j10(V_a - V_o)$$

Solving for V_o gives


$$V_o = \frac{28 + j10}{8 + j10} V_a = \frac{29.73 \angle 19.65^\circ}{12.81 \angle 51.34^\circ} (0.075 \angle -38.1^\circ) = 0.174 \angle -69.79^\circ$$

In the time domain, the output voltage is

$$v_o(t) = 174 \cos(5000t - 69.79^\circ) \text{ mV}$$

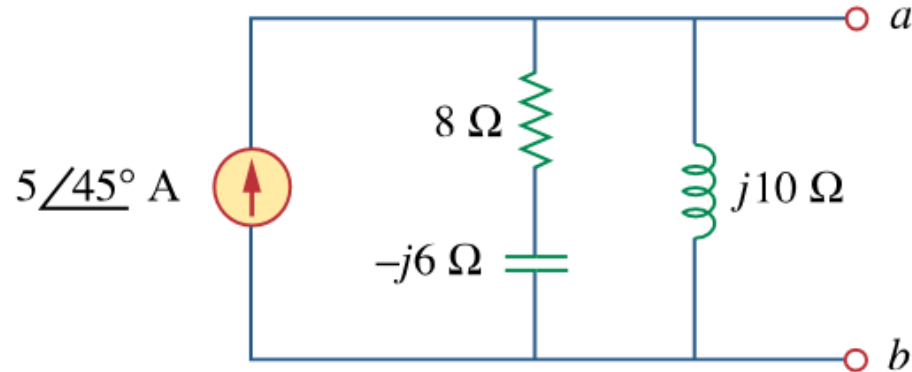
Example 10

For the circuit depicted in Fig. 10.101, find the Thevenin equivalent circuit at terminals a - b .



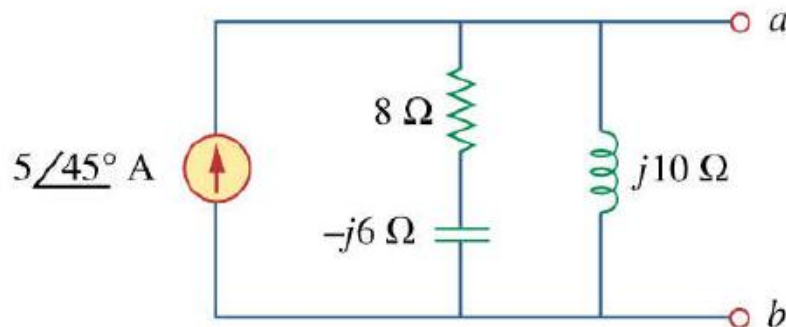Example 10 Solution

For the circuit depicted in Fig. 10.101, find the Thevenin equivalent circuit at terminals $a-b$.



$$V_{Th} = ?$$



$$Z_1 = 8 - j6$$

$$Z_2 = j10$$

$$I_1 = (5\angle 45^\circ) \frac{Z_1}{Z_1 + Z_2}$$


$$I_1 = (5\angle 45^\circ) \frac{8 - j6}{8 - j6 + j10} = 5.6 - 0.5j$$

$$V_{Th} = I_1 Z_2 = (5.6 - 0.5j)(j10)$$

$$V_{Th} = 5 + j55.7$$

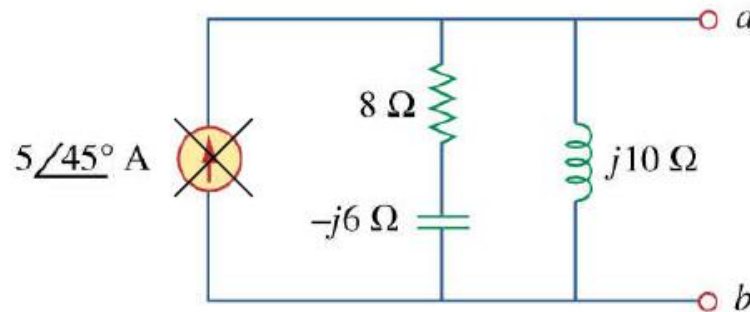Example 10 Solution


For the circuit depicted in Fig. 10.101, find the Thevenin equivalent circuit at terminals $a-b$.



$$V_m = ?$$

$$V_{Th} = 5 + j 55.7$$

$$Z_{Th} = ?$$

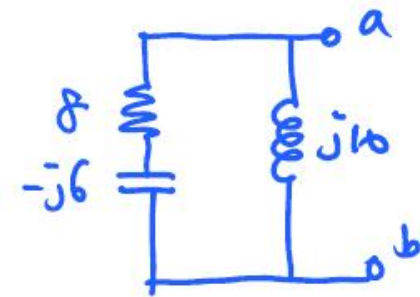


$$Z_{eq} = Z_1 \parallel Z_2 = \frac{Z_1 Z_2}{Z_1 + Z_2}$$

$$\rightarrow Z_{eq} = \frac{(8 - j6)(j10)}{8 - j6 + j10}$$

$$\rightarrow Z_{eq} = 10 + j5$$

Example 11 – Thévenin/Norton

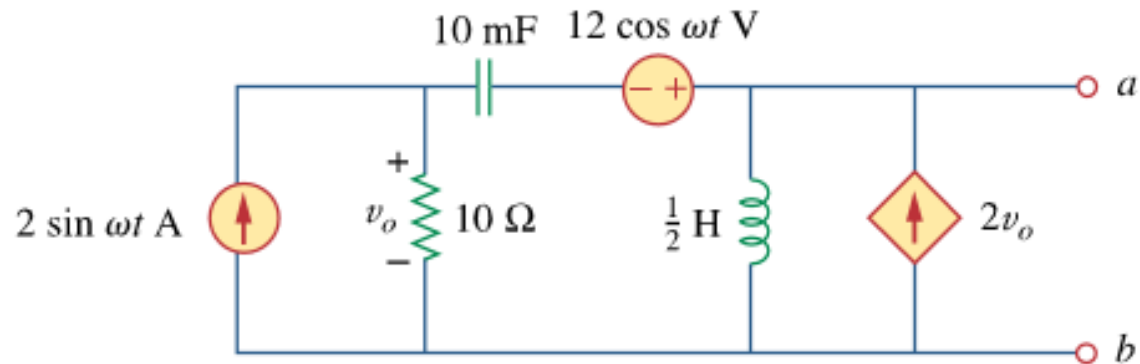- 10.66** At terminals a - b , obtain Thevenin and Norton equivalent circuits for the network depicted in Fig. 10.109. Take $\omega = 10$ rad/s.




Example 11 Solution

$$\omega = 10$$

$$0.5 \text{ H} \longrightarrow j\omega L = j(10)(0.5) = j5$$

$$10 \text{ mF} \longrightarrow \frac{1}{j\omega C} = \frac{1}{j(10)(10 \times 10^{-3})} = -j10$$

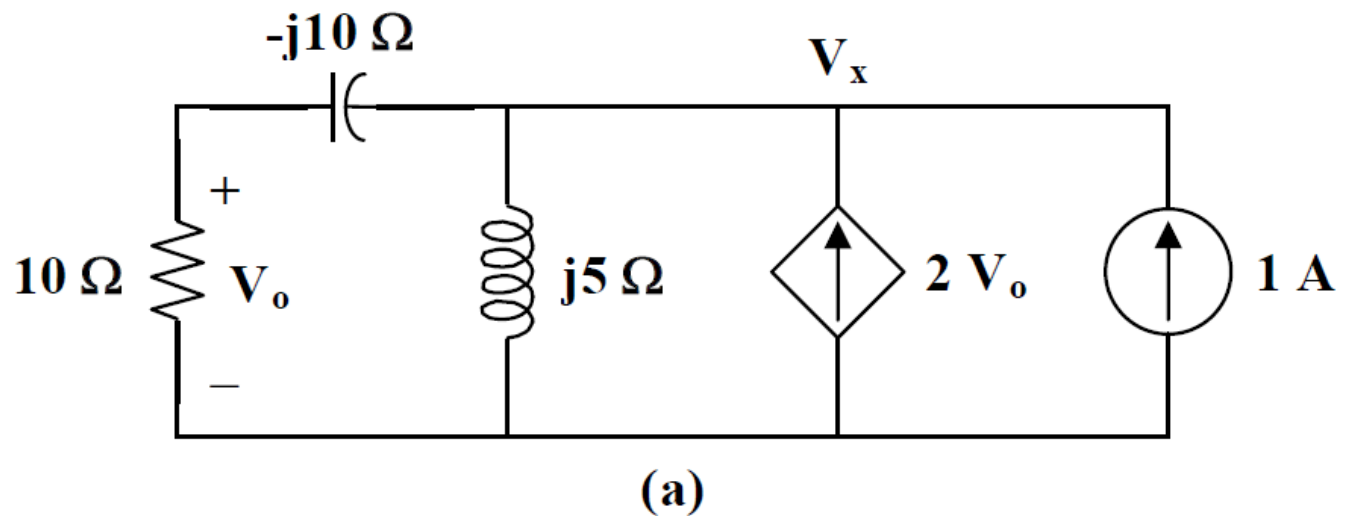To find \mathbf{Z}_{th} , consider the circuit in Fig. (a).



Example 11 Solution


$$1 + 2V_o = \frac{V_x}{j5} + \frac{V_x}{10 - j10},$$

$$\text{where } V_o = \frac{10V_x}{10 - j10}$$

$$1 + \frac{19V_x}{10 - j10} = \frac{V_x}{j5} \longrightarrow V_x = \frac{-10 + j10}{21 + j2}$$

$$Z_N = Z_{th} = \frac{V_x}{1} = \frac{14.142 \angle 135^\circ}{21.095 \angle 5.44^\circ} = 670 \angle 129.56^\circ \text{ m}\Omega$$

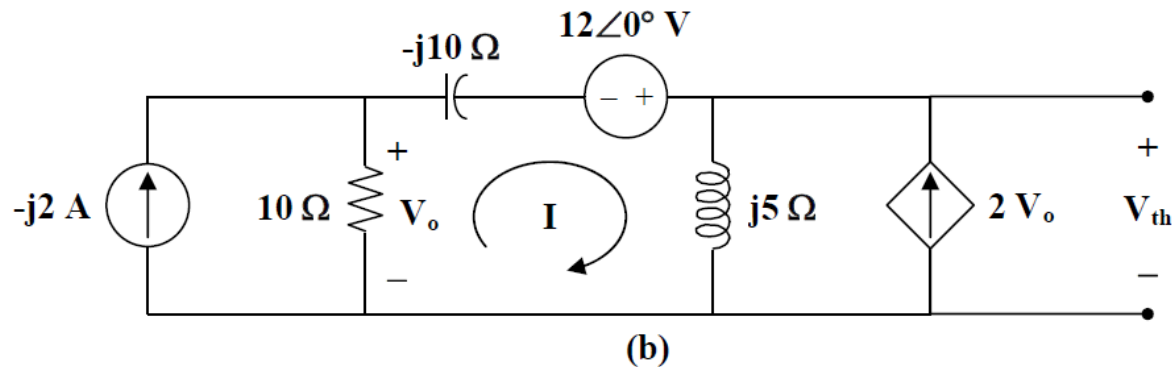To find V_{th} and I_N , consider the circuit in Fig. (b).



$$(10 - j10 + j5)I - (10)(-j2) + j5(2V_o) - 12 = 0$$

where $V_o = (10)(-j2 - I)$

Example 11 Solution

Thus,

$$(10 - j105)\mathbf{I} = -188 - j20$$

$$\mathbf{I} = \frac{188 + j20}{-10 + j105}$$


$$\mathbf{V}_{th} = j5(\mathbf{I} + 2\mathbf{V}_o) = j5(-19\mathbf{I} - j40) = -j95\mathbf{I} + 200$$

$$\begin{aligned}\mathbf{V}_{th} &= \frac{-j95(188 + j20)}{-10 + j105} + 200 = \frac{(95\angle -90^\circ)(189.06\angle 6.07^\circ)}{105.48\angle 95.44} + 200 \\ &= 170.28\angle -179.37^\circ + 200 = -170.27 - j1.8723 + 200 = 29.73 - j1.8723\end{aligned}$$


$$\mathbf{V}_{th} = \mathbf{29.79\angle -3.6^\circ V}$$

$$\mathbf{I}_N = \frac{\mathbf{V}_{th}}{\mathbf{Z}_{th}} = \frac{29.79\angle -3.6^\circ}{0.67\angle 129.56^\circ} = \mathbf{44.46\angle -133.16^\circ A}$$

Example 12

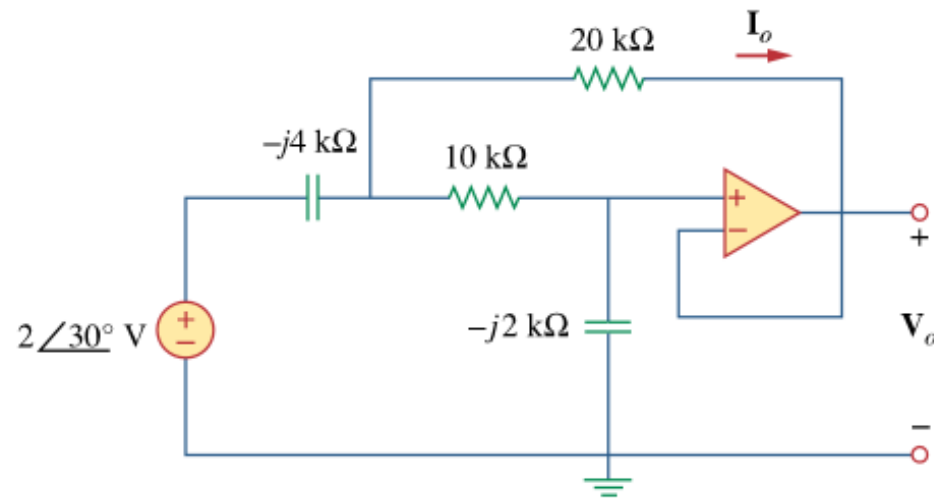

Example 12 Solution

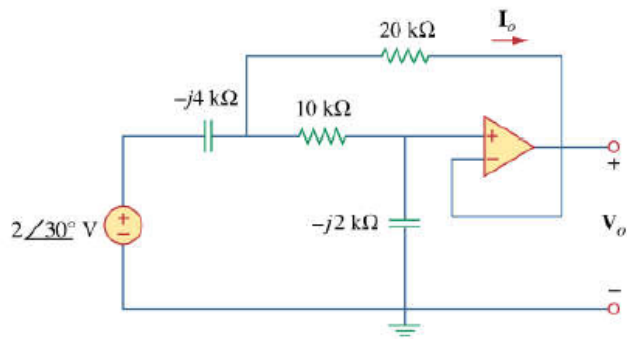

$$I_o = \frac{V_1 - V_o}{20k}$$

Nodal @ V_1 :


$$0 = -\frac{V_1 - (2\angle 30^\circ)}{-j4,000} - \frac{V_1 - V_o}{10,000} - \frac{V_1 - V_o}{20,000}$$

$$2\angle 30^\circ \Rightarrow 1.73 + j1$$

$$V_1 \left(-\frac{1}{-j4,000} - \frac{1}{10,000} - \frac{1}{20,000} \right) + V_o \left(\frac{1}{10,000} + \frac{1}{20,000} \right) + \frac{1.73+j1}{-j4,000} = 0$$

$$\textcircled{1} \rightarrow (1.73 + j1) = (1 - j0.6)V_1 + (0 + j0.6)V_o$$

Example 12 Solution

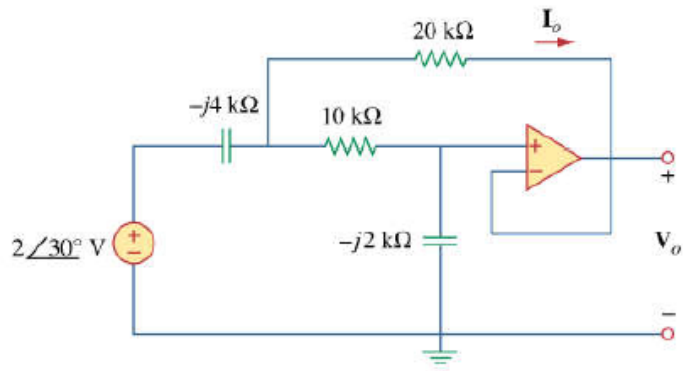

Nodal @ V_o

$$-\frac{V_o - V_i}{10,000} - \frac{V_o}{-j2,000} = 0$$

$$\rightarrow V_o \left(-\frac{1}{10k} + \frac{1}{j2,000} \right) + V_i \left(\frac{1}{10,000} \right) = 0$$

$$\textcircled{2} \rightarrow V_i = V_o (1 + j5)$$

$$\therefore (1.73 + j5) = (4 + j5) V_o$$

$$\rightarrow V_o = 0.31 \angle -21.3^\circ \text{ V}$$

$$\rightarrow I_o = \frac{V_i - V_o}{20,000} = 78 \angle 69^\circ \mu\text{A}$$