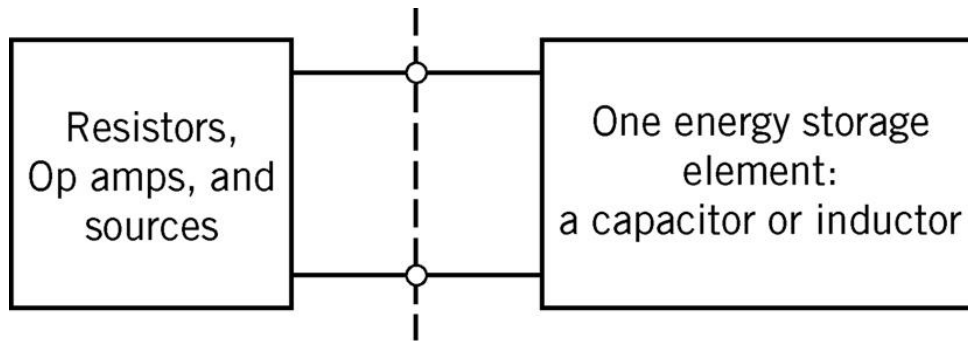


# Chapter 8


## *The Complete Response of RL and RC Circuits*

- Circuits that contain only one inductor and no capacitors or only one capacitor and no inductors can be represented by a first-order differential equation. These circuits are called *first-order circuits*.
- Thévenin's & Norton's equivalent circuits are used to simplify the analysis with one energy storage element.


# First-Order Circuits



(a)

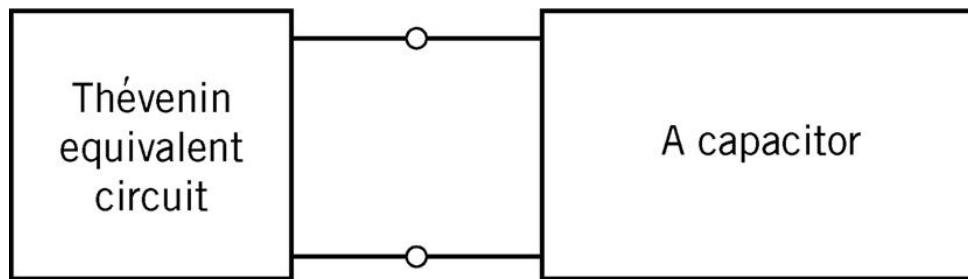

OR

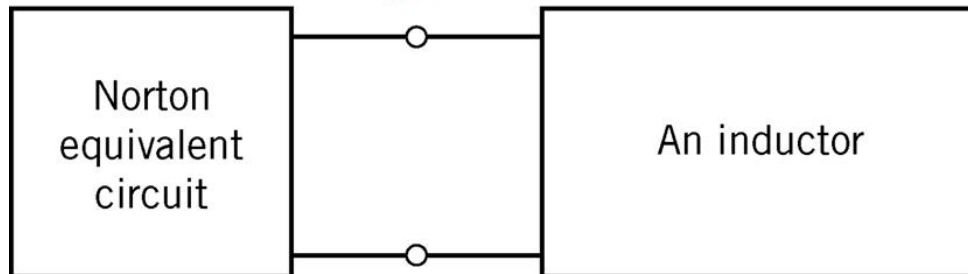


(b)

**FIGURE 8.2-1** A plan for analyzing first-order circuits.

(a) First, separate the energy storage element from the rest of the circuit. (b) Next, replace the circuit connected to a capacitor by its Thévenin equivalent circuit or replace the circuit connected to an inductor by its Norton equivalent circuit.

# FIRST-ORDER RC CIRCUITS

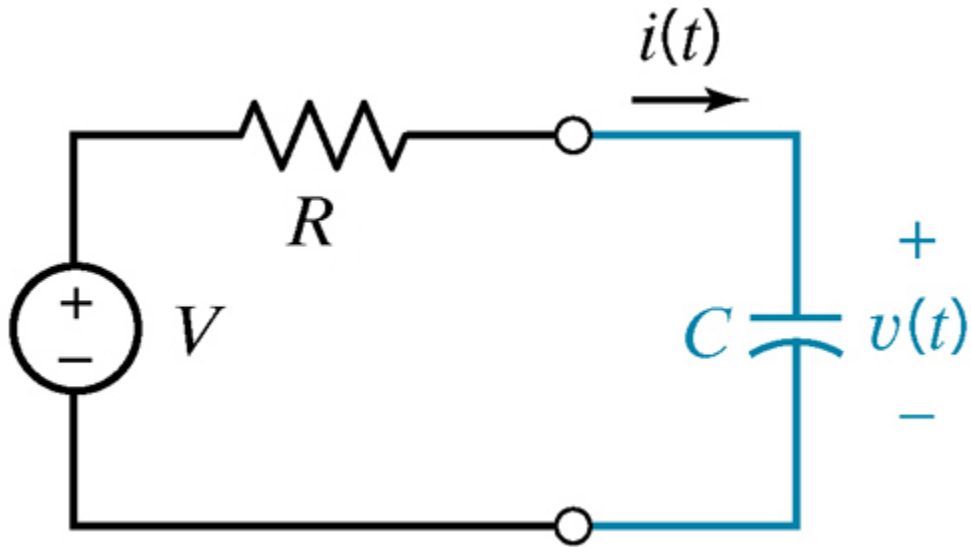

$$\begin{aligned} -V + R \cdot i(t) + v(t) &= 0 \\ \Rightarrow -V + R \cdot C \frac{dv(t)}{dt} + v(t) &= 0 \\ \Rightarrow R \cdot C \frac{dv(t)}{dt} + v(t) &= V \\ \Rightarrow \frac{dv(t)}{dt} + \frac{v(t)}{RC} &= \frac{V}{RC} \end{aligned}$$

# 1<sup>st</sup> Order Differential Equation

- Complete Response of the differential equation =  
Transient Response ( $t$  is small) + Steady State Response ( $t \rightarrow \infty$ )  
(Natural Response) (Forced Response)

$$\int \left( \frac{dv(t)}{dt} + \frac{v(t)}{RC} \right) = \int \frac{V}{RC}$$

- If input voltage  $V$  is constant (DC), the answer will be:

$$v(t) = V + (v(0) - V)e^{-\frac{t}{RC}}$$

# 1<sup>st</sup> Order Differential Equation

- If input voltage  $V$  is constant (DC), the answer will be:

$$v(t) = V + (v(0) - V)e^{-\frac{t}{RC}}$$


Time constant  
 $\tau = RC$

***Transient (Natural) Response:*** The part of the response which disappears after long enough time


$$v(t) = V + (v(0) - V)e^{-\frac{t}{RC}}$$

***Steady State (Forced) Response:*** The part of the response which stays after long enough time passes.

# Transient (Natural) Response

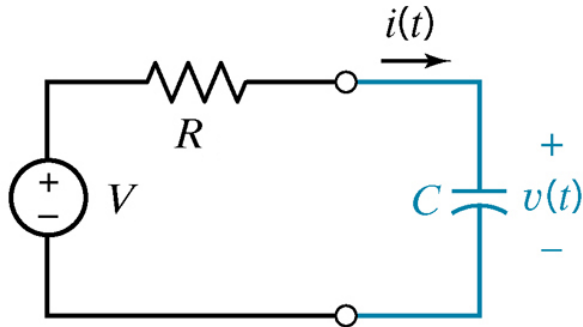


Transient (Natural) response

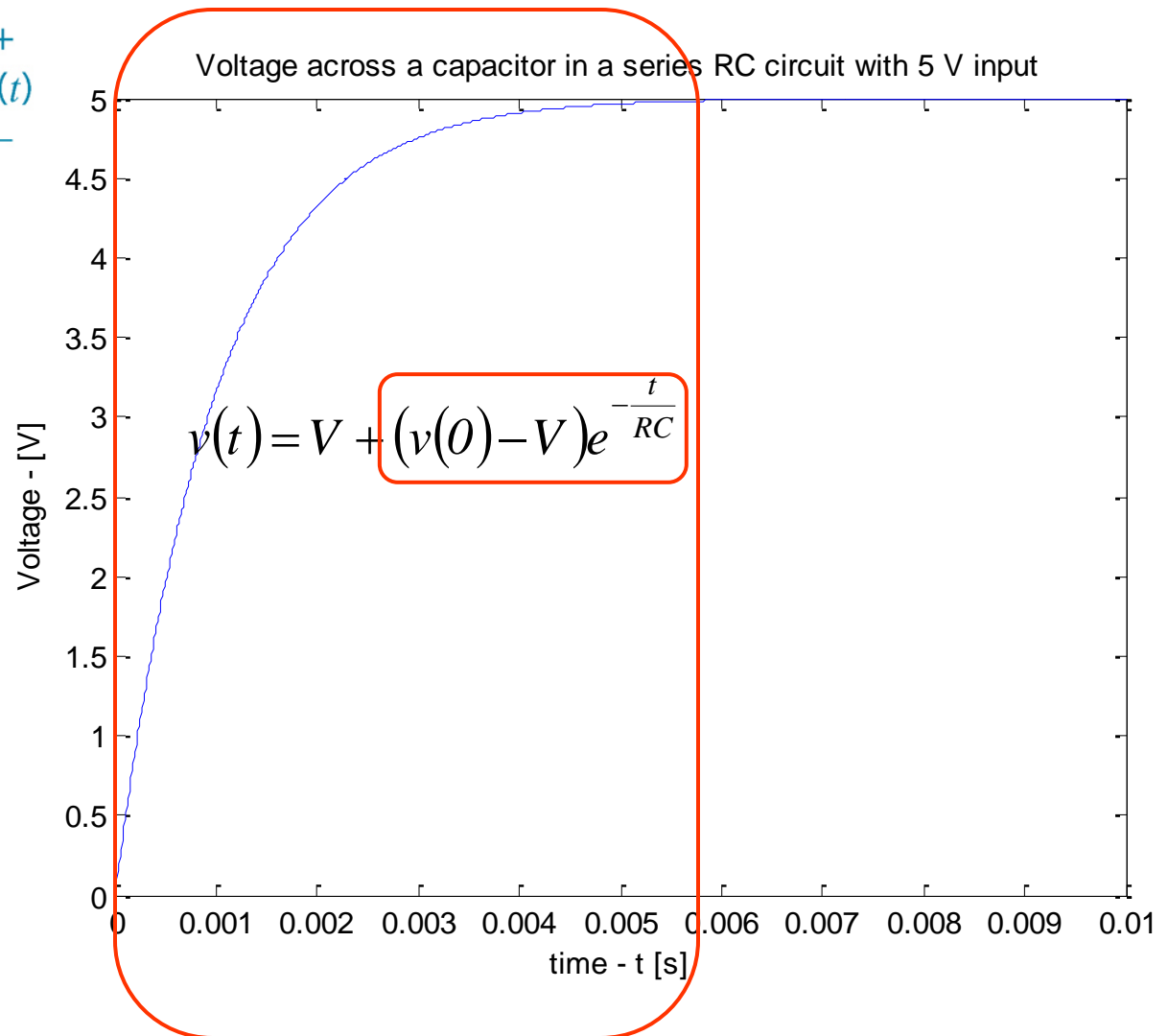




# Steady-State (Forced) Response

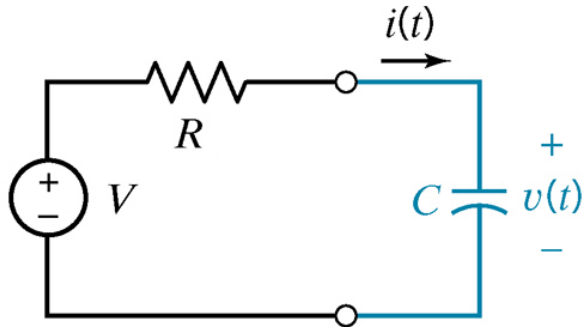


## Steady-State (Forced) Response

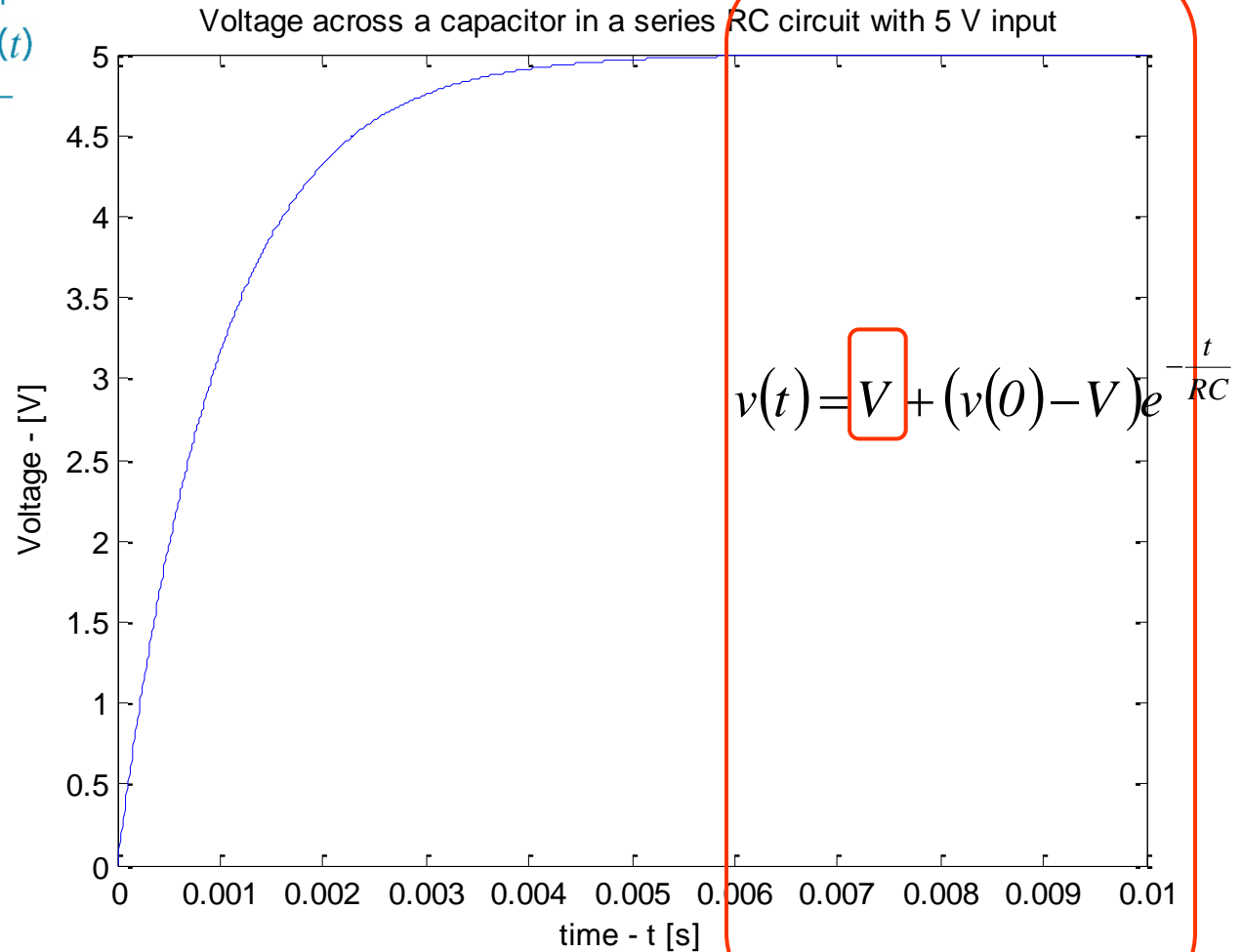


- At  $t = \tau = RC$ ,

$$Ve^{-\frac{\tau}{RC}} = Ve^{-1} = 0.368 \cdot V$$

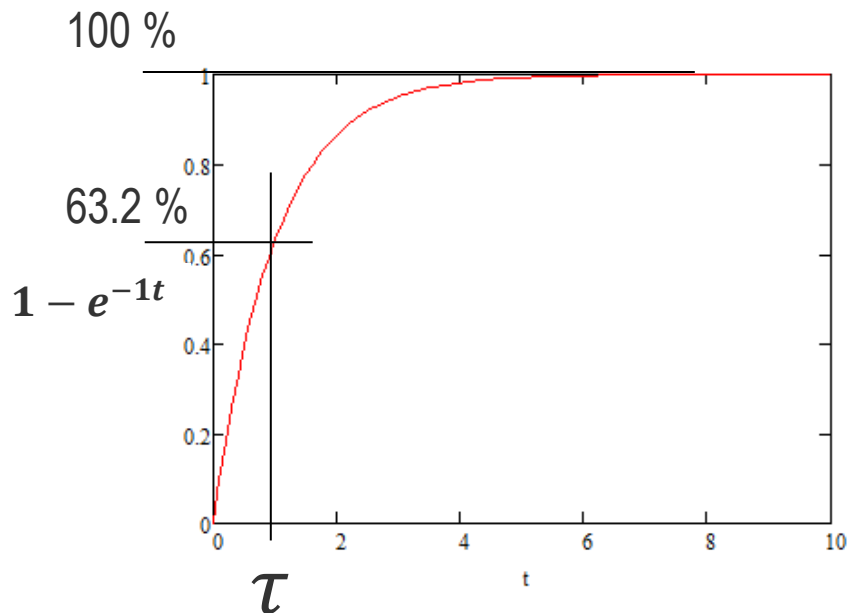Setting for  $t = \tau$  for the rise sets  $V(t)$  equal to  $0.63V_{\max}$ . This means that the time constant is the time elapsed after 63% of  $V_{\max}$  has been reached



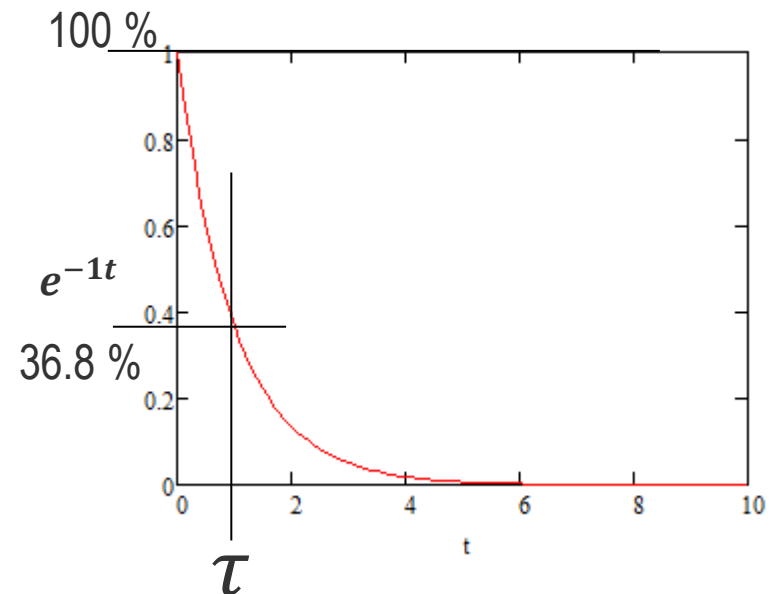Setting for  $t = \tau$  for the fall sets  $V(t)$  equal to  $0.37V_{\max}$ , meaning that the time constant is the time elapsed after it has fallen to 37% of  $V_{\max}$ .





# Example 1

- $R = 1 \, \Omega$ ,  $C = 1 \, \text{F}$ , initial capacitor voltage,  $v(0) = 0.5 \, \text{V}$  DC is applied to an RC circuit. What is the capacitor voltage?

$$v(t) = V + (v(0) - V)e^{-\frac{t}{RC}}$$

$$v(t) = 5 + (0 - 5)e^{-\frac{t}{1 \times 1}}$$

$$= 5(1 - e^{-t})$$

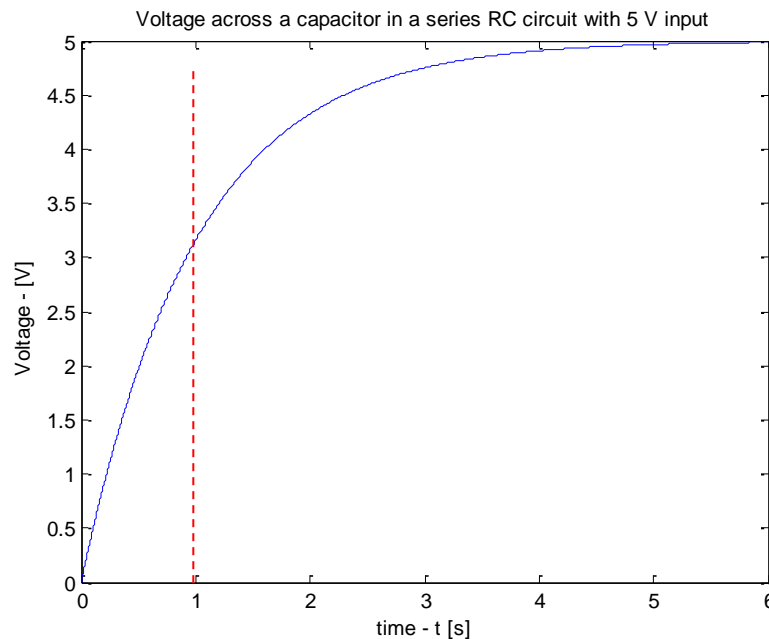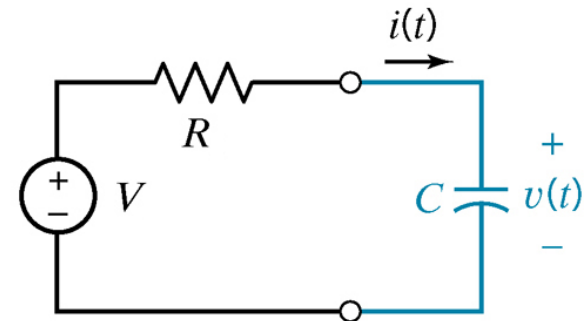


## Example 1

- $R = 1 \, \Omega$ ,  $C = 1 \, \text{mF}$ , initial capacitor voltage,  $v(0) = 0.5 \, \text{V}$  DC is applied to an RC circuit. What is the capacitor voltage?

$$v(t) = V + (v(0) - V)e^{-\frac{t}{RC}}$$


$$v(t) = 5 + (0 - 5)e^{-\frac{t}{1 \times 1 \text{m}}}$$

$$= 5(1 - e^{-10^3 t})$$

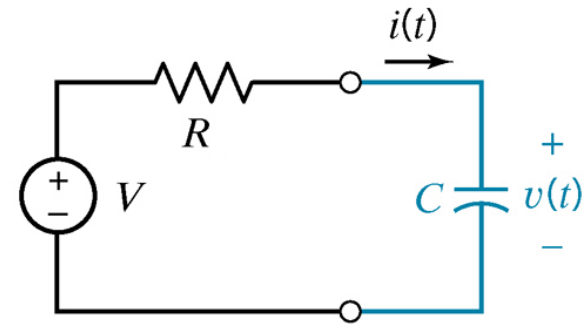


# Example 1


$$R = 1 \, \Omega, C = 1 \, \text{F}$$

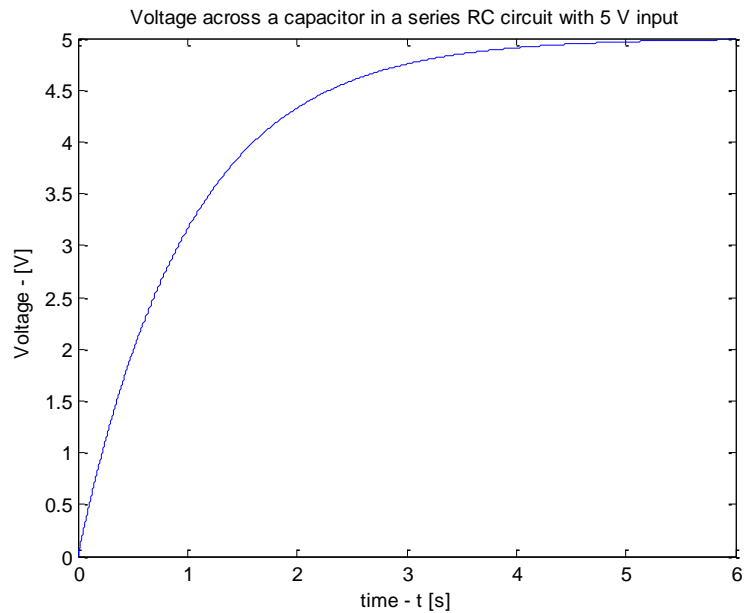

$$R = 1 \, \Omega, C = 1 \, \text{mF}$$

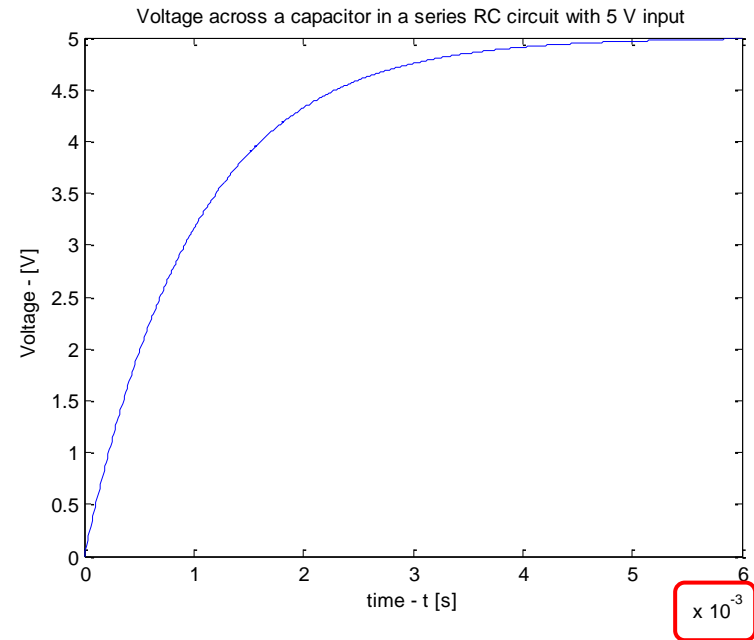

# FIRST-ORDER RL CIRCUITS

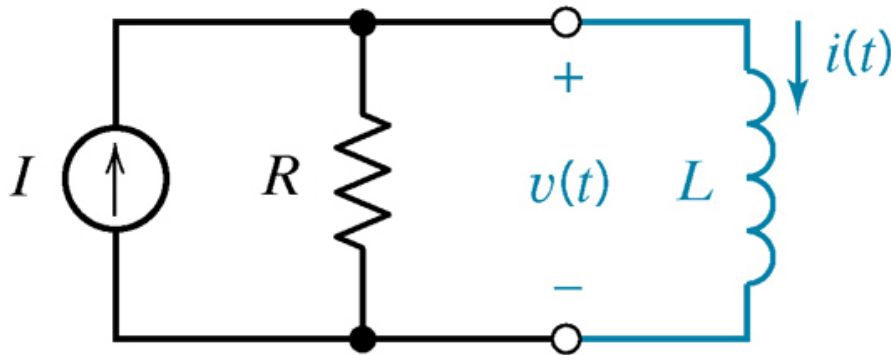

$$I = i_R + i(t)$$

$$\Rightarrow I = \frac{v(t)}{R} + i(t)$$

$$\Rightarrow I = \frac{L \frac{di(t)}{dt}}{R} + i(t)$$

$$\Rightarrow I = \frac{L}{R} \frac{di(t)}{dt} + i(t)$$

$$\Rightarrow \frac{di(t)}{dt} + \frac{R}{L} i(t) = \frac{R}{L} I$$

# 1<sup>st</sup> Order Differential Equation

- Complete Response of the differential equation =  
Transient Response (t is small) + Steady State Response (t → ∞)  
(Natural Response) (Forced Response)

$$\int \left( \frac{di(t)}{dt} + \frac{R}{L} i(t) \right) dt = \int \frac{R}{L} I dt$$

- If input current  $I$  is constant (DC), the answer will be:

$$i(t) = I + (i(0) - I)e^{-\frac{R}{L}t}$$



# 1<sup>st</sup> Order Differential Equation

- If input current  $I$  is constant (DC), the answer will be:

$$i(t) = I + (i(0) - I)e^{-\frac{R}{L}t}$$


**Transient (Natural) Response:** The part of the response which disappears after long enough time

$$i(t) = I + (i(0) - I)e^{-\frac{t}{\tau}}$$


Time constant  
 $\tau = L / R$

**Steady State (Forced) Response:** The part of the response which stays after long enough time passes.


# Transient (Natural) Response

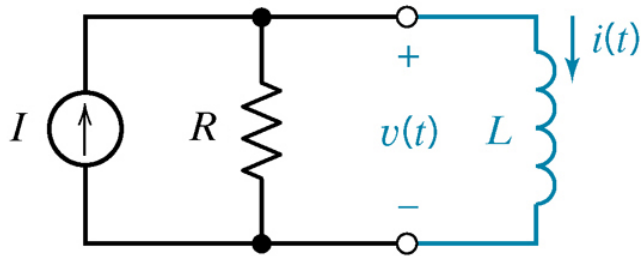


## Transient (Natural) response

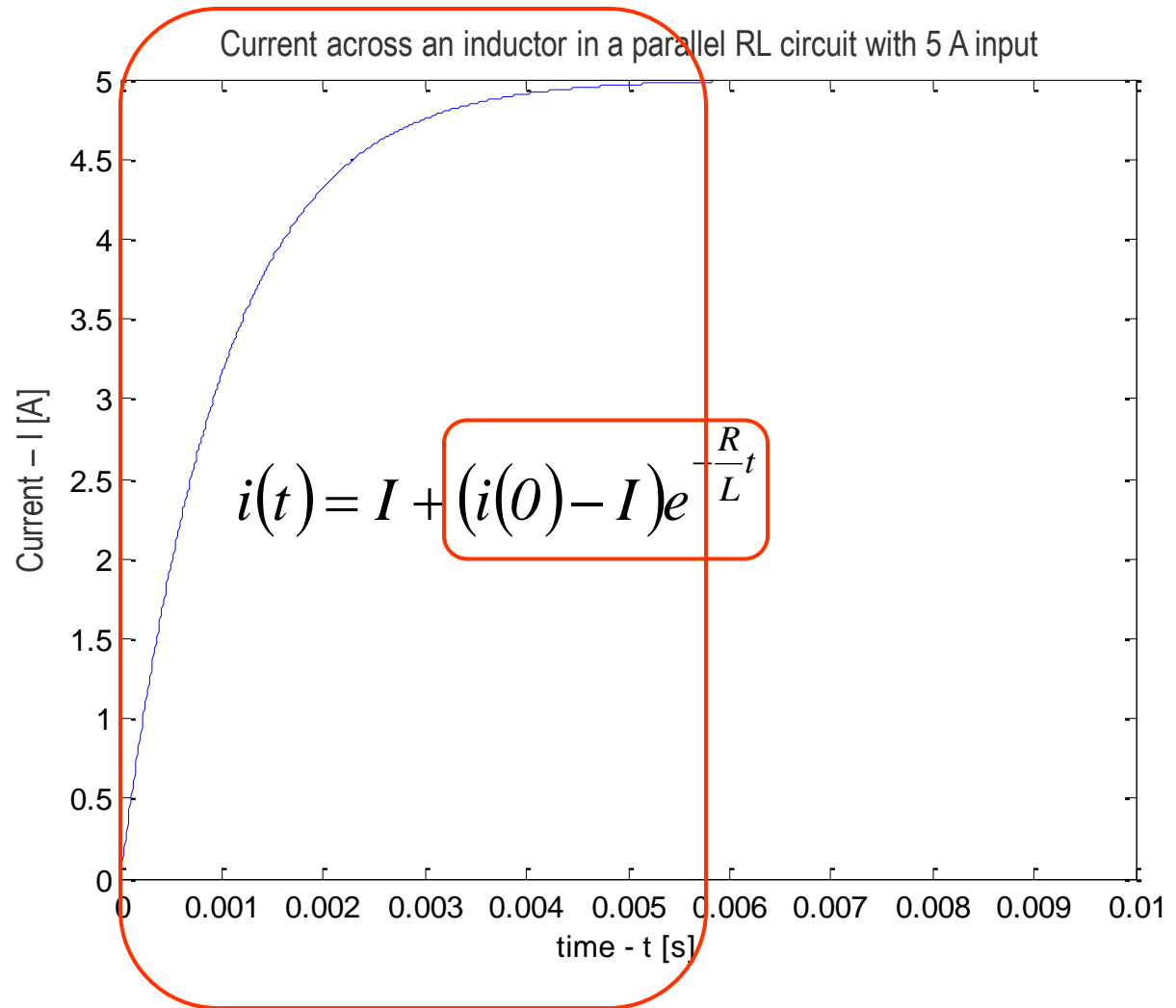

# Steady-State (Forced) Response

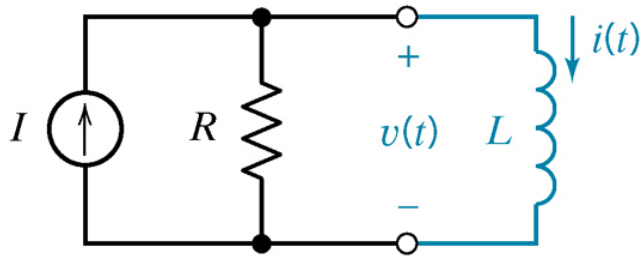

## Steady-State Forced Response

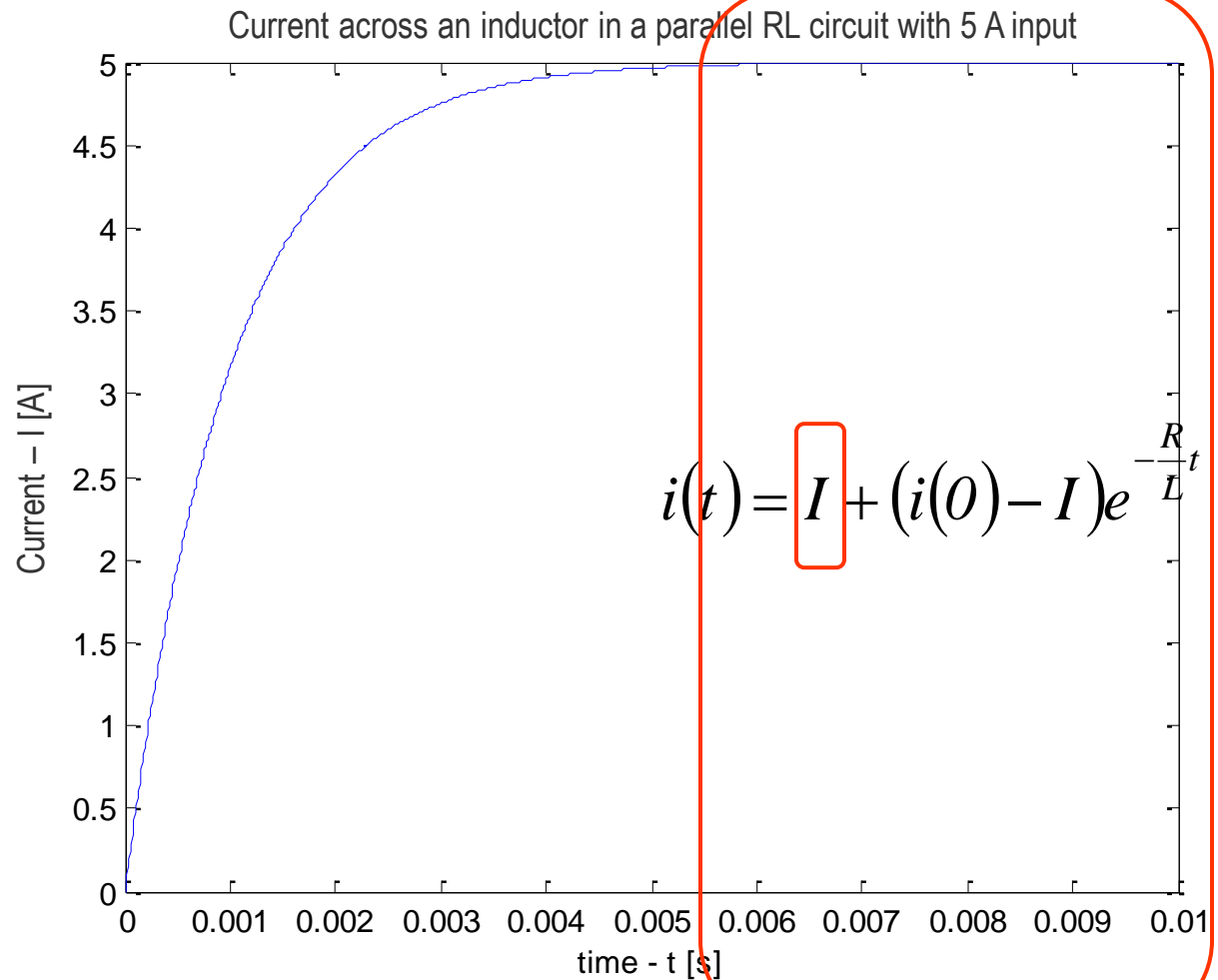

# REMEMBER: Initial Conditions

- **DC circuits**


- Independent voltage and current sources are DC (constant) – They do not change with time.
- The circuit includes at least one capacitor or one inductor (If multiple capacitors/inductors find the equivalent)
- The change in capacitor voltage or in inductor current is NOT instantaneous. It is continuous.
  - We denote the time immediately before the switch opens/closes as  $t_0^-$
  - We denote the time immediately after the switch opens/closes as  $t_0^+$
  - The capacitor voltage or inductor current have the same values right before and right after the switch closes

## REMEMBER: Initial Conditions

- A **capacitor** in a DC circuit behaves like an **open circuit** in steady state.
- An **inductor** in a DC circuit behaves like a **short circuit** in steady state.
- Draw the circuit for before the switch operation and after the switch operation!

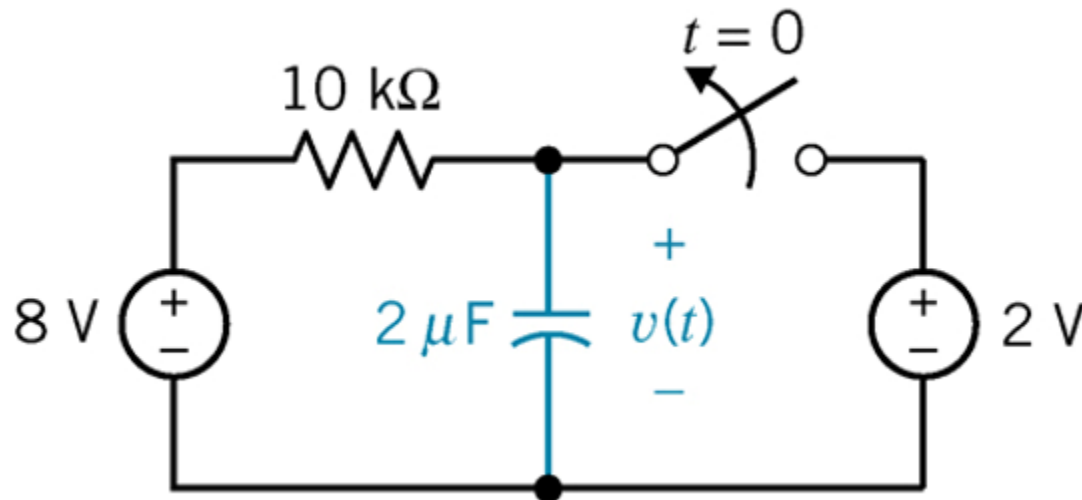
## Example 8.3-1

- What is the value of the capacitor voltage 50 ms after the switch opens?  $t \geq 0$




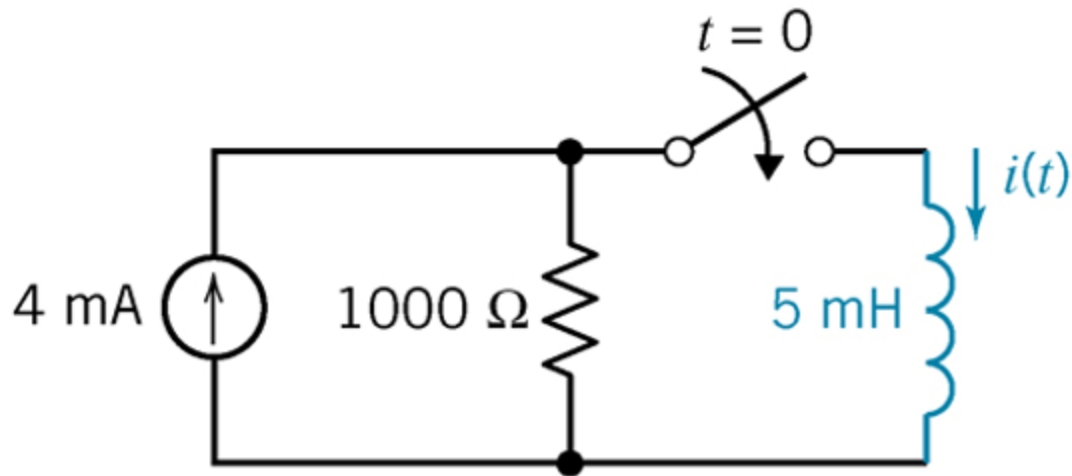
## Example 8.3-2

- Find the inductor current after the switch closes. How long will it take for the inductor current to reach **2 mA**?  $t \geq 0$


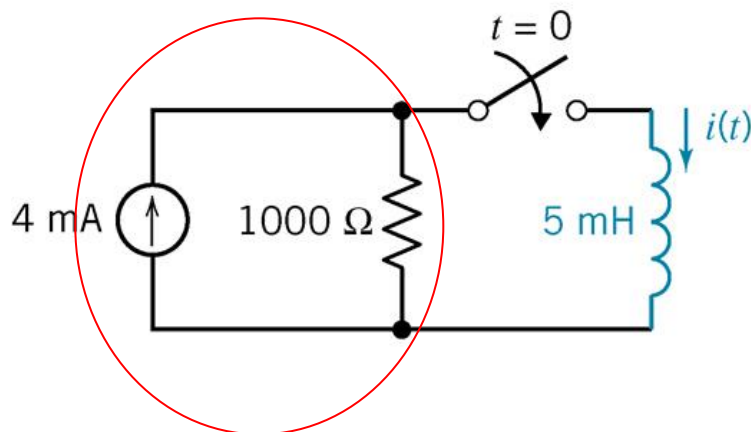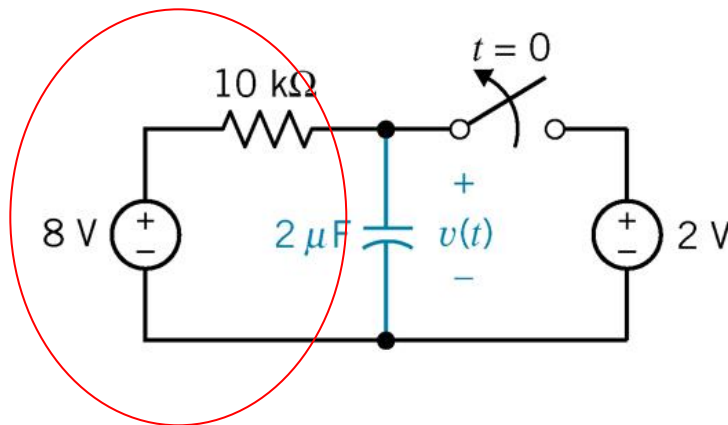
## In the previous problems

- At  $t \geq 0$ , the circuits are already Thévenin or Norton Eq. Circuits




See next problem...



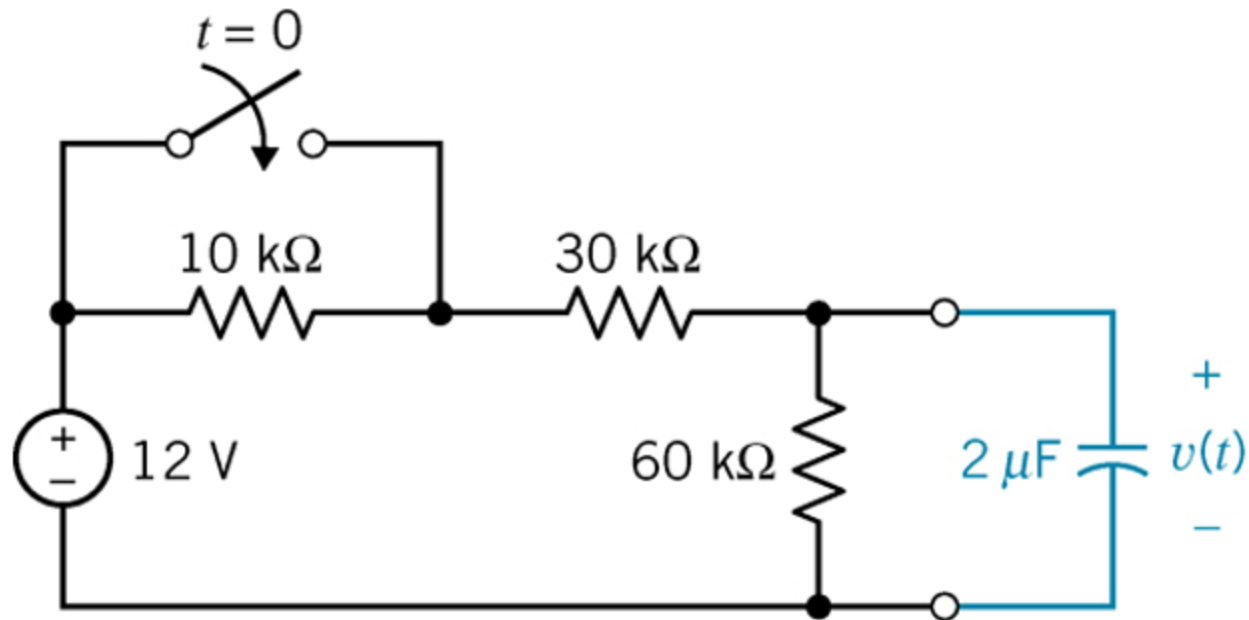
## Example 8.3-3

- The switch has been open for a long time and the circuit has reached steady state before the switch closes at time  $t = 0$ . Find the capacitor voltage for  $t \geq 0$ .



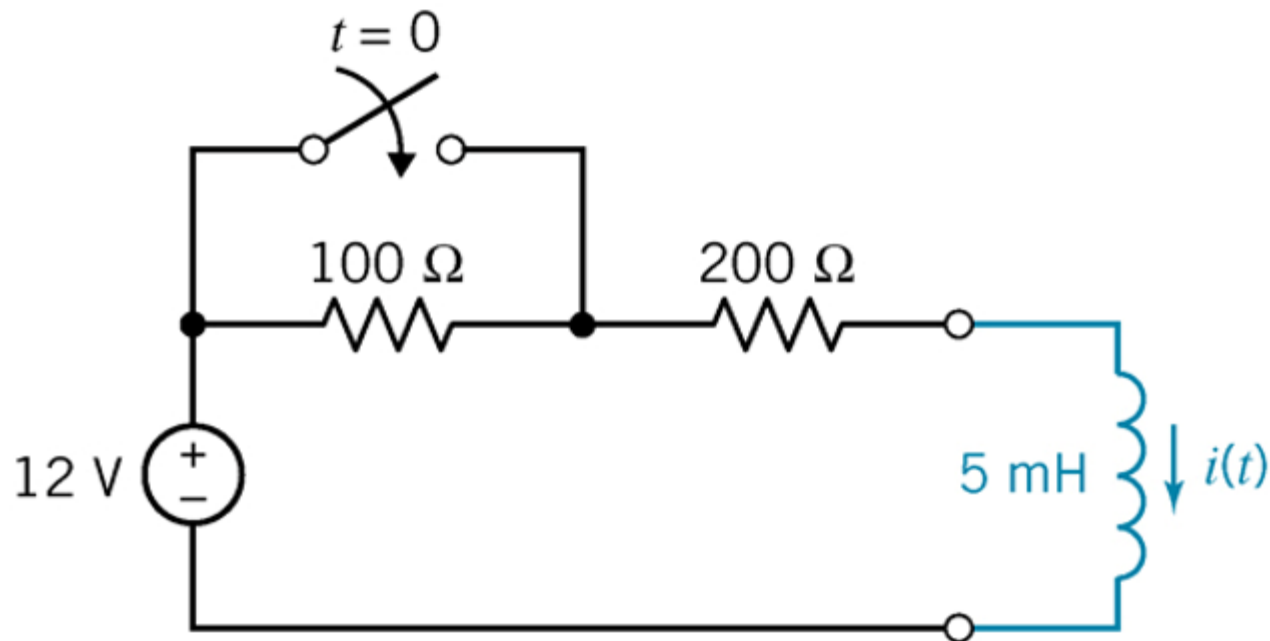
## Example 8.3-4

- The switch has been open for a long time and the circuit has reached steady state before the switch closes at time  $t = 0$ . Find the inductor current for  $t \geq 0$ .



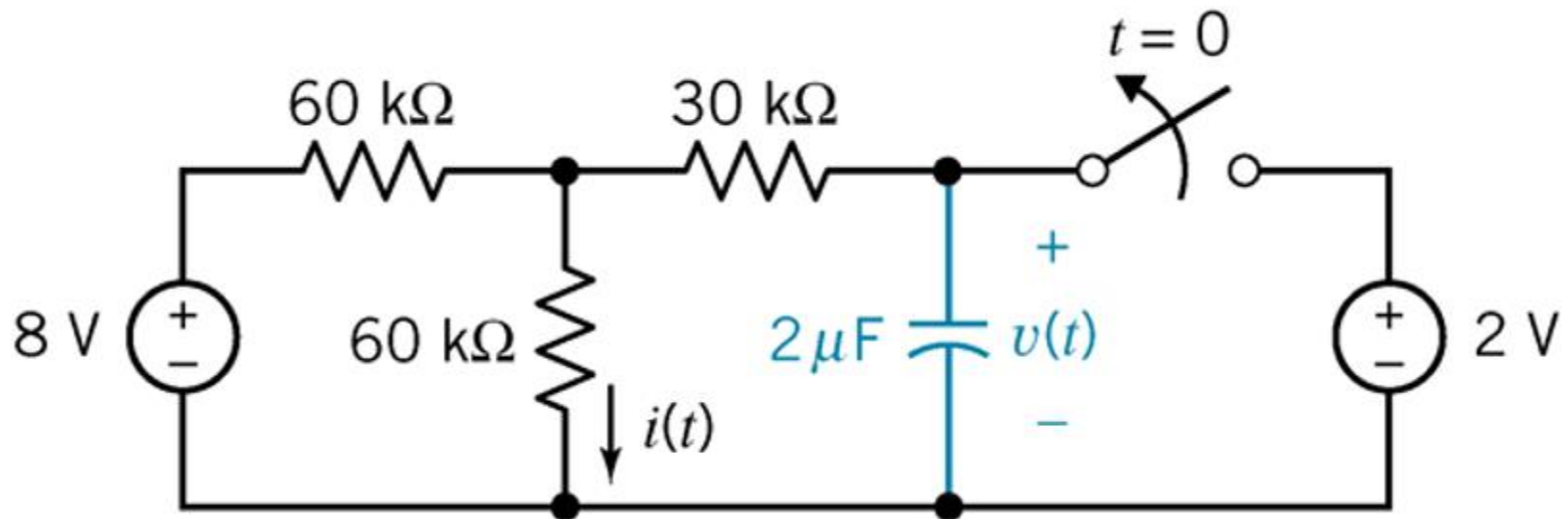
## Example 8.3-5

- The circuit is at steady state before the switch opens. Find the current  $i(t)$  for  $t > 0$ . What is the voltage  $v(t)$  at  $t = 60$  ms?



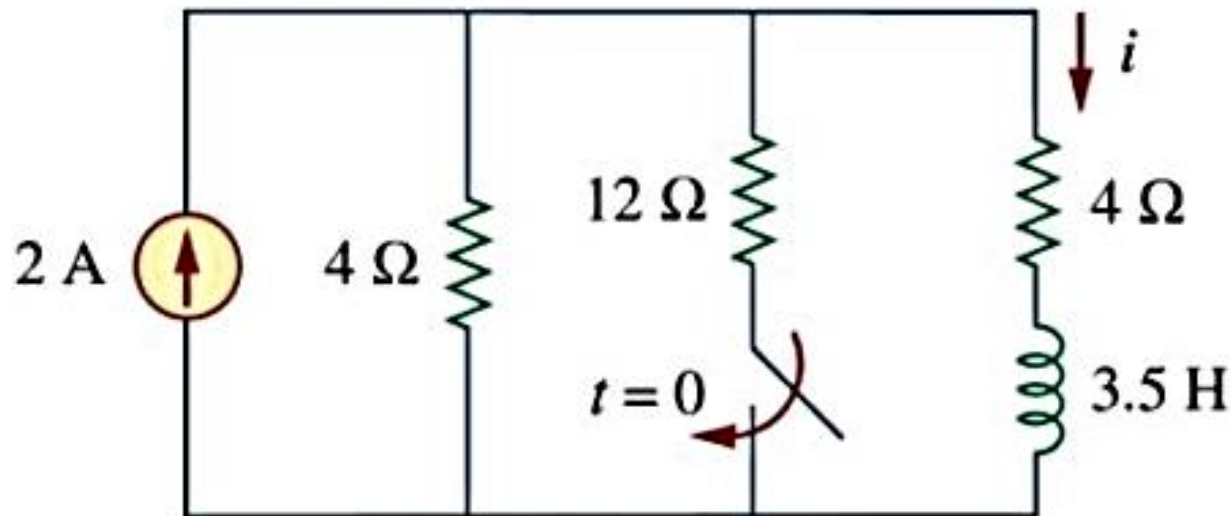
## Example 2

Obtain the inductor current for both  $t < 0$  and  $t > 0$  in each of the circuits in Fig. 7.120.


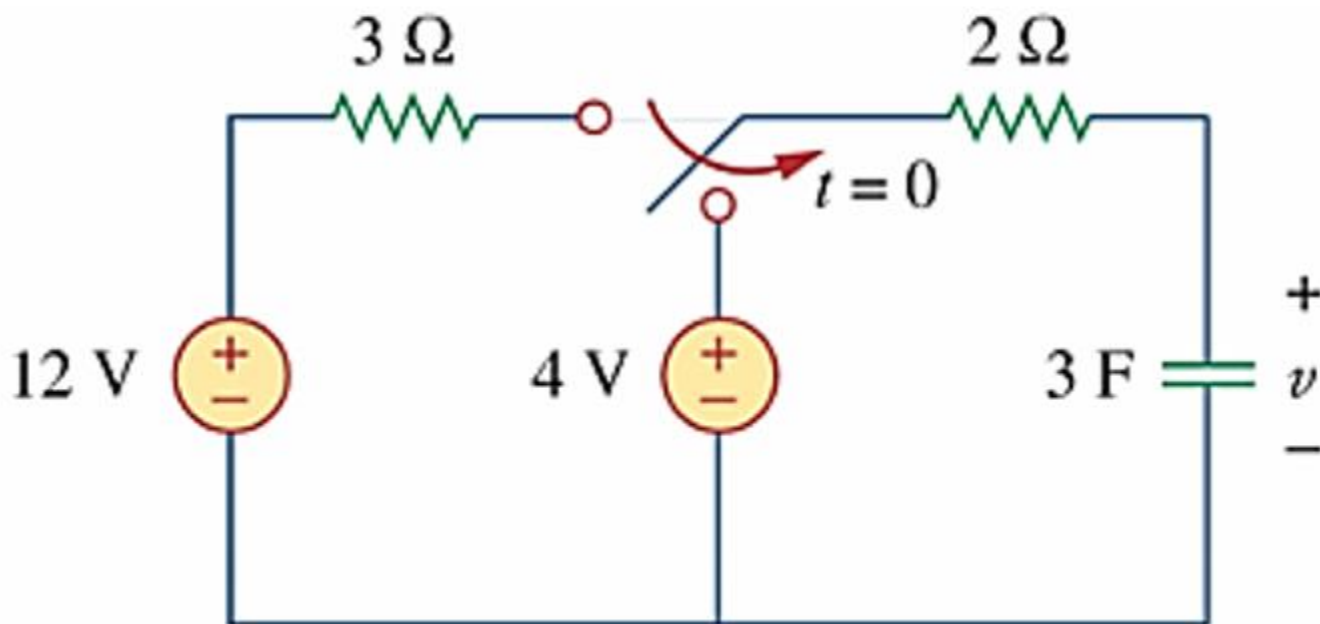
## Example 3

Find the capacitor voltage for  $t < 0$  and  $t > 0$  for each of the circuits in the figure



## Example 8.5-1

- The first order switch is at steady state before the switch closes at  $t = 0$ . Find the capacitor voltage,  $v(t)$ , for  $t > 0$ .

