
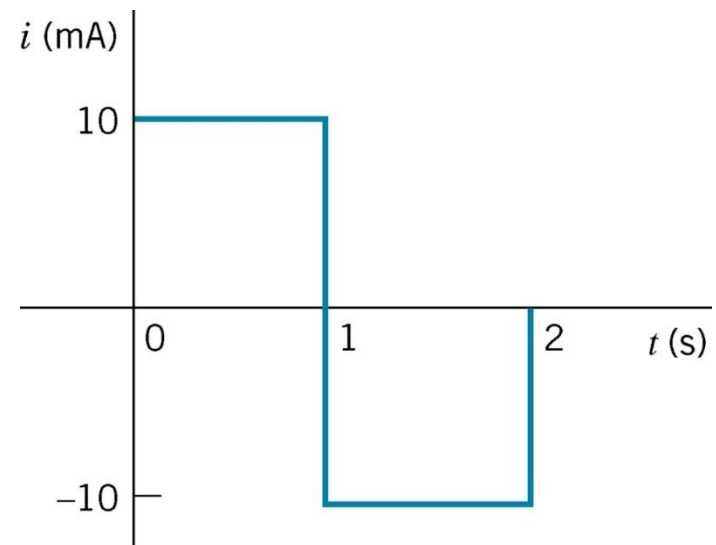


Chapter 7


Energy Storage Elements (Problems)

Example 7.2-1

- $C = 1 \text{ mF}$ and the voltage across the capacitor is given below. Calculate the current $i(t)$ through the capacitor.

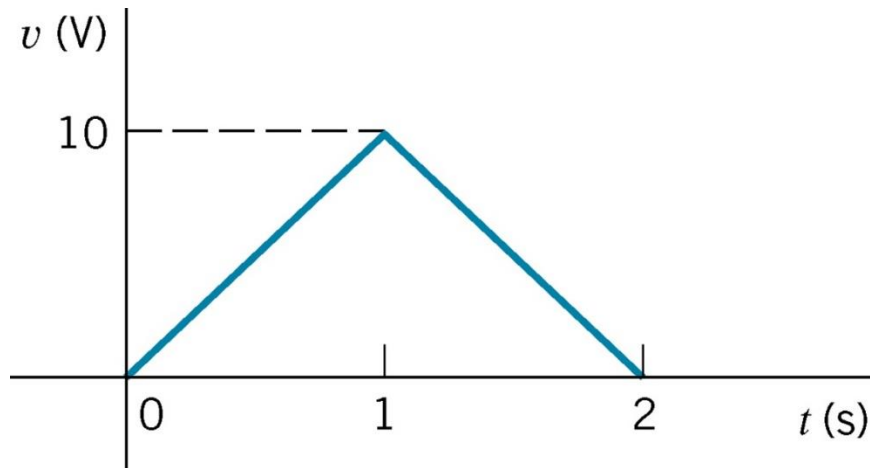

Example 7.2-1 Solution

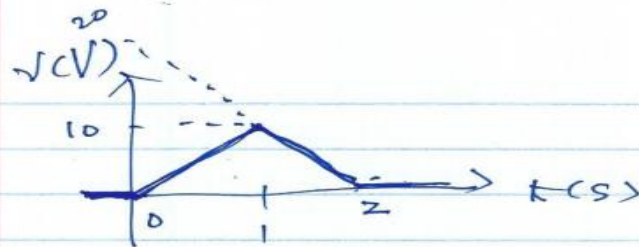


$$C = 1 \text{ mF.}$$

$$v(t) = \begin{cases} 0, & t \leq 0 \\ 10 \cdot t & 0 \leq t < 1 \\ 20 - 10t & 1 \leq t \leq 2 \\ 0 & t \geq 2 \end{cases}$$

$$\begin{aligned} i(t) &= \begin{aligned} & \rightarrow 1 \times 10^{-3} \cdot 0 = 0 \\ & \rightarrow (1 \times 10^{-3}) \cdot \frac{d(10t)}{dt} = 10^{-2} \\ & \rightarrow (1 \times 10^{-3}) \frac{d(20 - 10t)}{dt} = -10^{-2} \\ & \rightarrow (1 \times 10^{-3}) \cdot 0 = 0 \end{aligned} \end{aligned}$$

$$i = C \cdot \frac{dv}{dt}$$

$$i(t) = \begin{cases} 0 & t \leq 0 \\ 10^{-2} & 0 \leq t < 1 \\ -10^{-2} & 1 \leq t \leq 2 \\ 0 & t \geq 2 \end{cases}$$

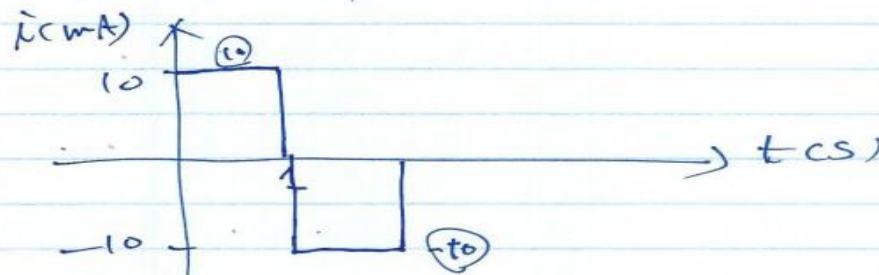

Example 7.2-1 Solution

Find the current for a capacitor $C = 1 \text{ mF}$ when the voltage across the capacitor is represented by the signal shown in Figure 7.2-6.

Solution

The voltage (with units of volts) is given by

$$v(t) = \begin{cases} 0 & t \leq 0 \\ 10t & 0 \leq t \leq 1 \\ 20 - 10t & 1 \leq t \leq 2 \\ 0 & t \geq 2 \end{cases}$$

Then, because $i = C dv/dt$, where $C = 10^{-3} \text{ F}$, we obtain

$$i(t) = \begin{cases} 0 & t < 0 \\ 10^{-2} & 0 < t < 1 \\ -10^{-2} & 1 < t < 2 \\ 0 & t > 2 \end{cases}$$

Therefore, the resulting current is a series of two pulses of magnitudes 10^{-2} A and -10^{-2} A , respectively, as shown in Figure 7.2-7.

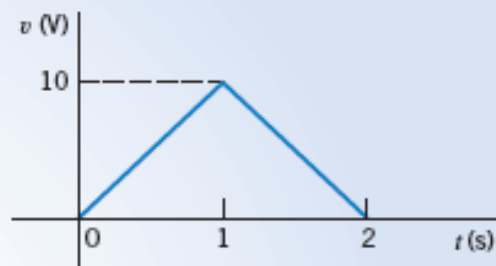


FIGURE 7.2-6 Waveform of the voltage across a capacitor for Example 7.2-1. The units are volts and seconds.

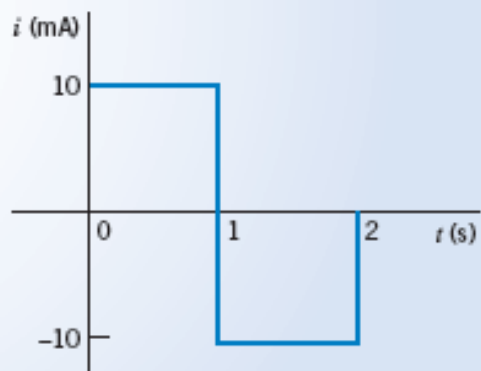


FIGURE 7.2-7 Current for Example 7.2-1.

Example 7.2-5


- The input current is:

$$i(t) = 3.75e^{-1.2t} \text{ A for } t > 0$$

- The output capacitor voltage is:

$$v(t) = 4 - 1.25e^{-1.2t} \text{ V for } t > 0$$


- Find the value of the capacitance, **C**.

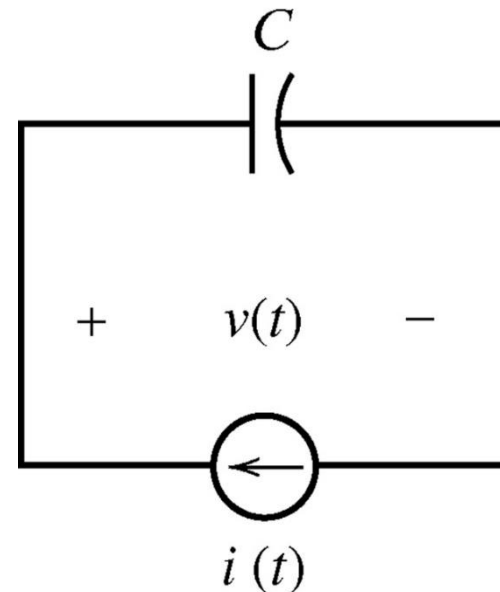

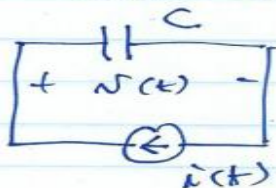Example 7.2-5 Solution

$$i(t) = 3.75 e^{-1.2t} \text{ A for } t > 0$$

$$v(t) = 4 - 1.25 e^{-1.2t} \text{ V for } t > 0.$$



$$v(t) = \frac{1}{C} \int_0^t i(\tau) d\tau + v(0)$$

$$\begin{aligned} 4 - 1.25 e^{-1.2t} &= \frac{1}{C} \int_0^t 3.75 e^{-1.2\tau} d\tau + v(0) \\ &= \frac{3.75}{C(-1.2)} e^{-1.2\tau} \Big|_0^t + v(0) \\ &= -\frac{3.125}{C} (e^{-1.2t} - 1) + v(0) \\ &= \underbrace{-\frac{3.125}{C} e^{-1.2t}}_{-1.25 e^{-1.2t}} + \underbrace{\frac{3.125}{C} + v(0)}_{4} \end{aligned}$$

$$-1.25 e^{-1.2t} = -\frac{3.125}{C} e^{-1.2t} \quad -1.25 = -\frac{3.125}{C}$$

$$\times 4 = \frac{3.125}{C} + v(0)$$

$$\begin{aligned} C &= \frac{3.125}{1.25} \\ &= 2.5 \text{ F} \end{aligned}$$

Example 7.2-5 Solution

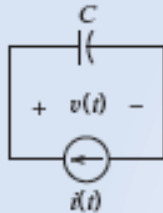


FIGURE 7.2-12

The circuit considered in Example 7.2-5.

The input to the circuit shown in Figure 7.2-12 is the current

$$i(t) = 3.75e^{-1.2t} \text{ A for } t > 0$$

The output is the capacitor voltage

$$v(t) = 4 - 1.25e^{-1.2t} \text{ V for } t > 0$$

Find the value of the capacitance C .

Solution

The capacitor voltage is related to the capacitor current by

$$v(t) = \frac{1}{C} \int_0^t i(\tau) d\tau + v(0)$$

That is,



$$4 - 1.25e^{-1.2t} = \frac{1}{C} \int_0^t 3.75e^{-1.2\tau} d\tau + v(0) = \frac{3.75}{C(-1.2)} e^{-1.2\tau} \Big|_0^t + v(0) = \frac{-3.125}{C} (e^{-1.2t} - 1) + v(0)$$

Equating the coefficients of $e^{-1.2t}$ gives

$$1.25 = \frac{3.125}{C} \Rightarrow C = \frac{3.125}{1.25} = 2.5 \text{ F}$$

Example 7.2-2


- $C = \frac{1}{2} \text{ F}$, the current through the capacitor is given below. Calculate the voltage $v(t)$ across the capacitor.

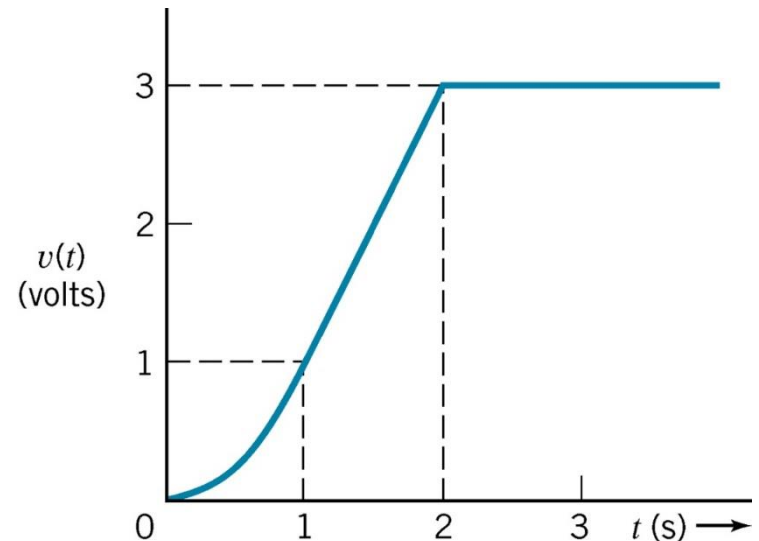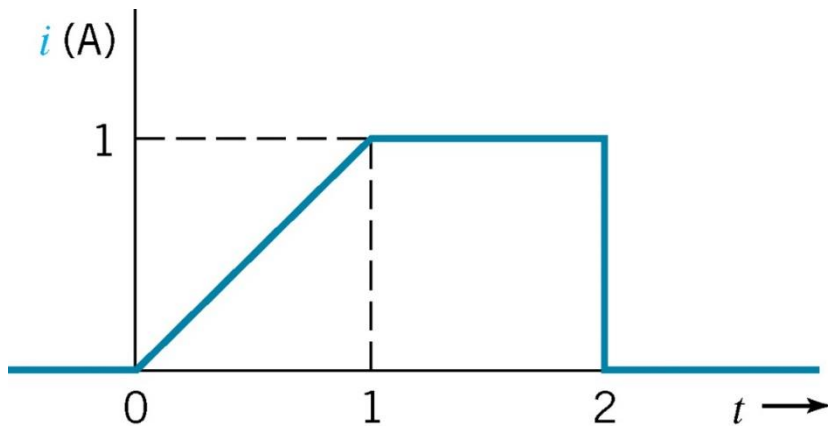

Example 7.2-2 Solution

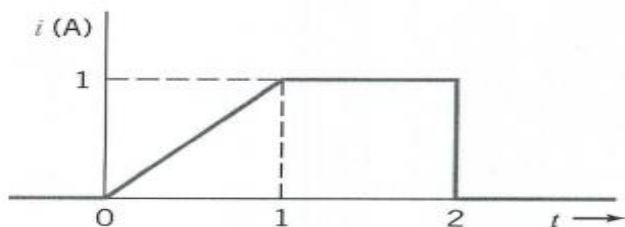Example 7.2 – 2

- $C = \frac{1}{2} \text{ F}$, current through the capacitor is given, voltage across the capacitor, $v(t) = ?$



$$i(t) = \begin{cases} 0 & t \leq 0 \\ t & 0 \leq t \leq 1 \\ 1 & 1 \leq t \leq 2 \\ 0 & 2 < t \end{cases}$$

$$v(t) = \frac{1}{C} \int_0^t i(\tau) d\tau + v(0) = \frac{1}{C} \int_0^t i(\tau) d\tau$$

$$C = \frac{1}{2}$$

$$v(t) = \begin{cases} 0 & t \leq 0 \\ 2 \int_0^t \tau d\tau & 0 \leq t \leq 1, \quad v(t) = t^2, \quad v(1) = 1\text{V} \\ 2 \int_1^t (1) d\tau + v(1) & 1 \leq t \leq 2, \quad 2(t-1) + 1, \quad v(2) = 3\text{V} \\ v(2) & 2 \leq t \end{cases}$$



Example 7.2-2 Solution

Find the voltage $v(t)$ for a capacitor $C = 1/2$ F when the current is as shown in Figure 7.2-8 and $v(t) = 0$ for $t \leq 0$.

Solution

First, we write the equation for $i(t)$ as

$$i(t) = \begin{cases} 0 & t \leq 0 \\ t & 0 \leq t \leq 1 \\ 1 & 1 \leq t \leq 2 \\ 0 & 2 < t \end{cases}$$

Then, because $v(0) = 0$

$$v(t) = \frac{1}{C} \int_0^t i(\tau) d\tau + v(0) = \frac{1}{C} \int_0^t i(\tau) d\tau$$

and $C = 1/2$, we have

$$v(t) = \begin{cases} 0 & t \leq 0 \\ 2 \int_0^t \tau d\tau & 0 \leq t \leq 1 \\ 2 \int_1^t (1) d\tau + v(1) & 1 \leq t \leq 2 \\ v(2) & 2 \leq t \end{cases}$$

with units of volts. Therefore, for $0 < t \leq 1$, we have

$$v(t) = t^2$$

For the period $1 \leq t \leq 2$, we note that $v(1) = 1$ and, therefore, we have

$$v(t) = 2(t - 1) + 1 = (2t - 1) \text{ V}$$

The resulting voltage waveform is shown in Figure 7.2-9. The voltage changes with t^2 during the first 1 s, changes linearly with t during the period from 1 to 2 s, and stays constant equal to 3 V after $t = 2$ s.

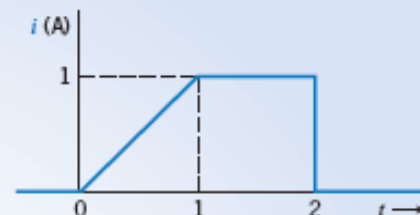


FIGURE 7.2-8 Circuit waveform for Example 7.2-2. The units are in amperes and seconds.


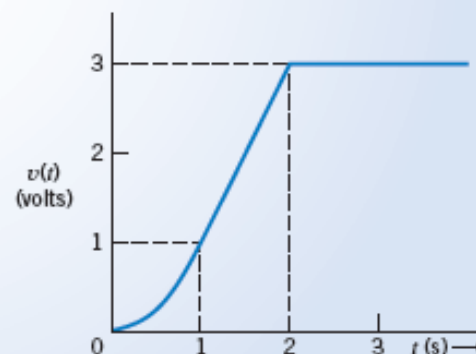


FIGURE 7.2-9 Voltage waveform for Example 7.2-2.

Example 7.3-2


- The voltage across a 5-mF capacitor is shown below. Determine and plot the capacitor current, power and energy.

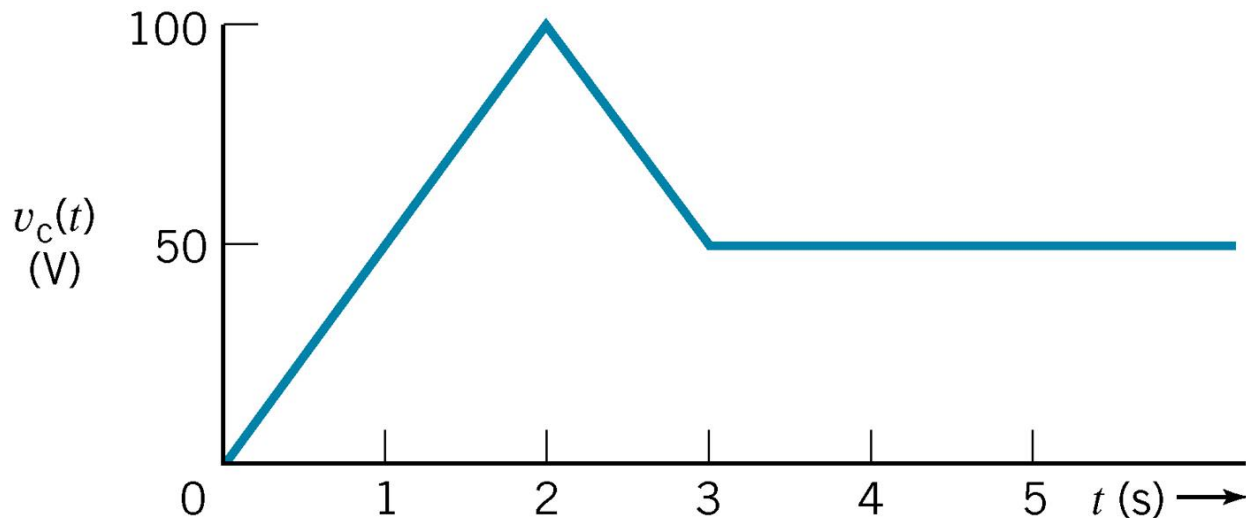

Example 7.3-2 Solution

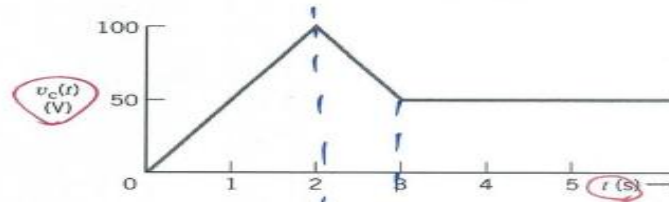Example 7.3 – 2


The voltage across a 5-mF capacitor is shown below. Determine and plot the capacitor current, power and energy.




$$i(t) = C \frac{dv}{dt} \rightarrow \text{slope of } v(t) \text{ graph.}$$


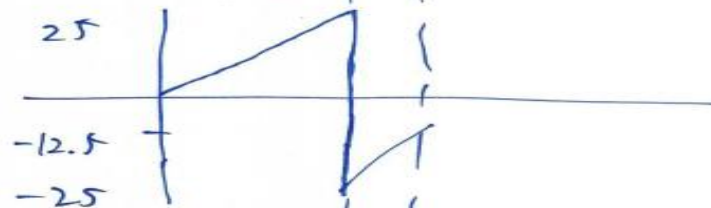
$$p(t) = C \cdot v(t) \frac{dv(t)}{dt} = v(t) \cdot \left(C \frac{dv(t)}{dt} \right)$$





$$w(t) = \frac{1}{2} C v(t)^2$$

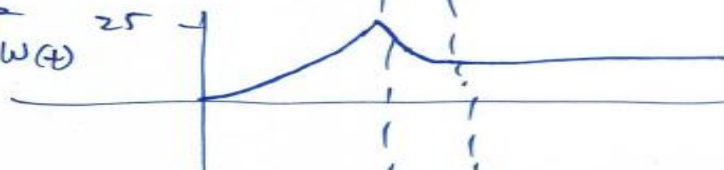


Example 7.3-2 Solution


$$C = 5 \text{ mF}$$

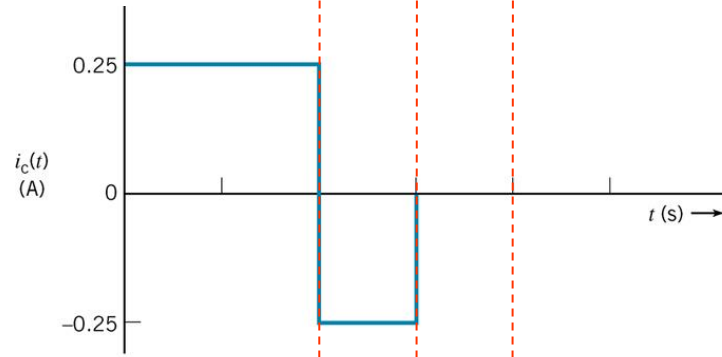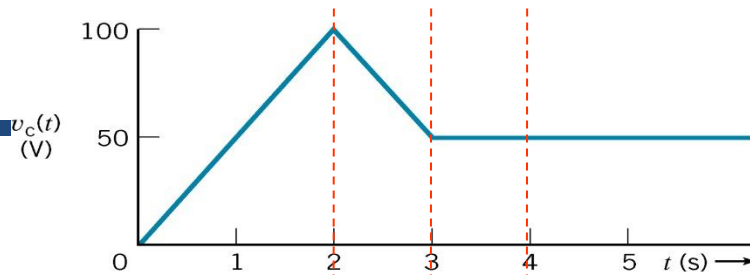

(a)

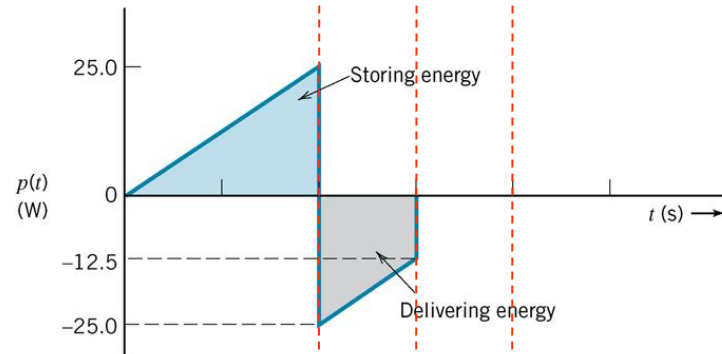

(b)

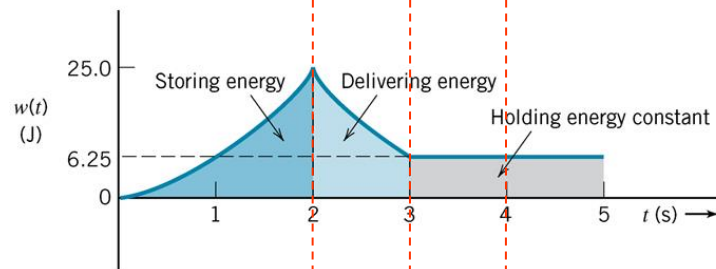

(c)

Example 7.3-2 Solution

The voltage across a 5-mF capacitor varies as shown in Figure 7.3-3. Determine and plot the capacitor current, power, and energy.


Solution

The current is determined from $i_c = C dv/dt$ and is shown in Figure 7.3-4a. The power is $v(t)i(t)$ —the product of the current plot (Figure 7.3-4a) and the voltage plot (Figure 7.3-3)—and is shown in Figure 7.3-4b. The capacitor receives energy during the first two seconds and then delivers energy for the period $2 < t < 3$.


The energy is $w = \int p dt$ and can be found as the area under the $p(t)$ plot. The plot for the energy is shown in Figure 7.3-4c. Note that the capacitor increasingly stores energy from $t = 0$ s to $t = 2$ s, reaching a maximum energy of 25 J. Then the capacitor delivers a total energy of 18.75 J to the external circuit from $t = 2$ s to $t = 3$ s. Finally, the capacitor holds a constant energy of 6.25 J after $t = 3$ s.




FIGURE 7.3-3 The voltage across a capacitor.

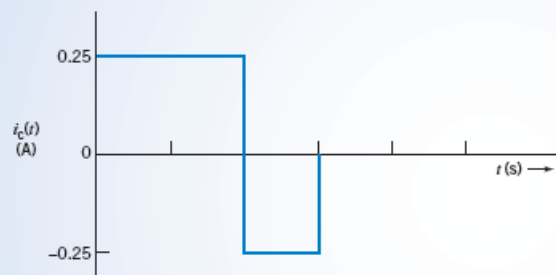

(a)

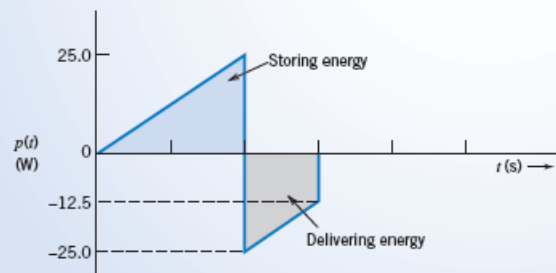

(b)

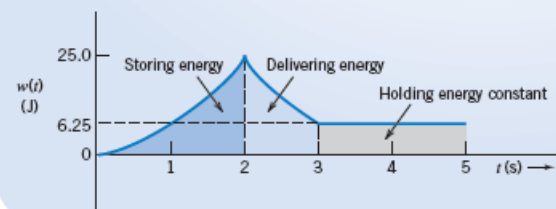


(c)

FIGURE 7.3-4 The current, power, and energy of the capacitor of Example 7.3-2.

Example 7.4-1




- Find the equivalent capacitance C_{eq} when $C_1 = C_2 = C_3 = 2 \text{ mF}$, $v_1(0) = 10 \text{ V}$ and $v_2(0) = v_3(0) = 20 \text{ V}$.

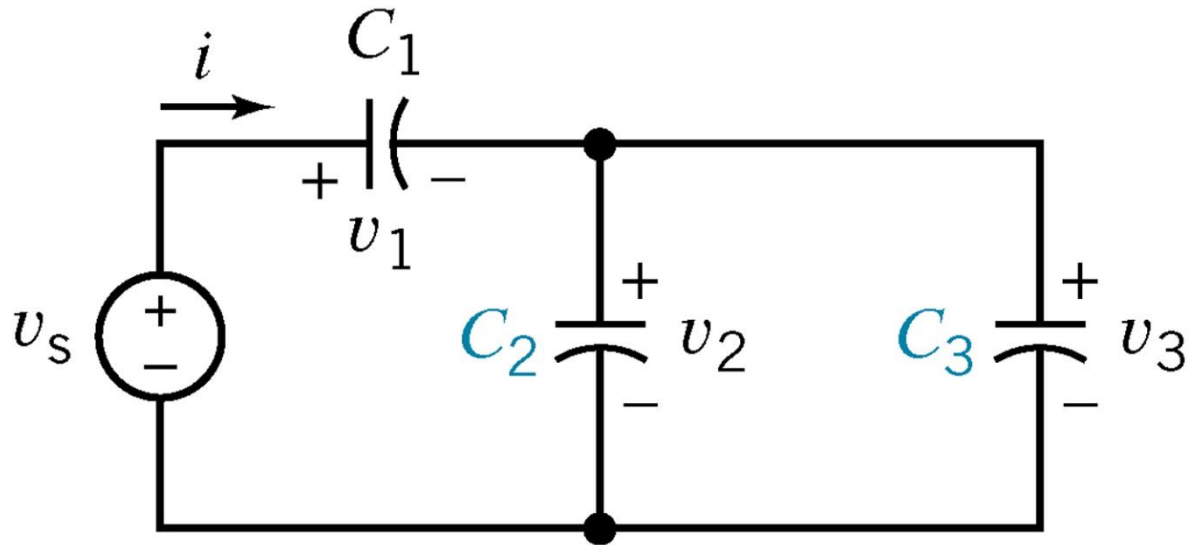

Example 7.4-1 Solution

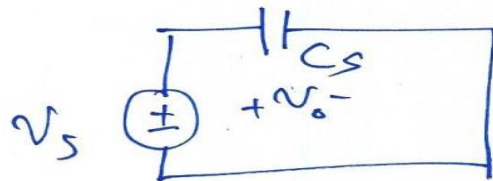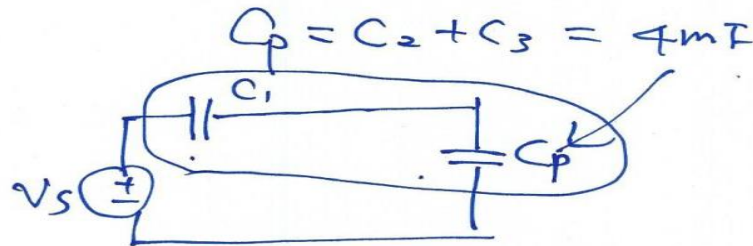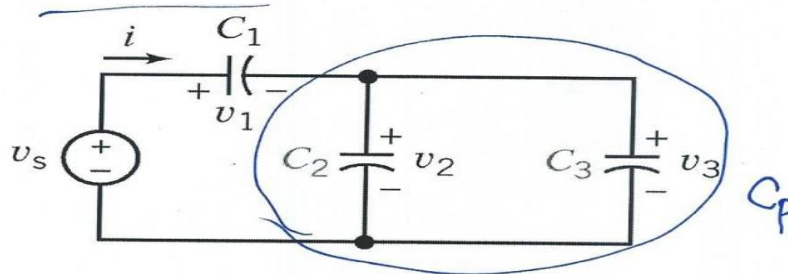Example 7.4 – 1

- Find the C_{eq} when $C_1 = C_2 = C_3 = \underline{2 \text{ mF}}$, $\underline{v_1(0) = 10 \text{ V}}$ and $\underline{v_2(0) = 20 \text{ V}}$



$C_s = C_1 \text{ \& } C_p \text{ in series}$

$$C_s = \frac{C_1 C_p}{C_1 + C_p} = \frac{2 \times 10^{-3} \cdot 4 \times 10^{-3}}{2 \times 10^{-3} + 4 \times 10^{-3}} = \frac{8}{6} \text{ mF}.$$

$v_o = ?$ $v_o = 10 + 20 = 30 \text{ V}$

Example 7.4-1 Solution

Find the equivalent capacitance for the circuit of Figure 7.4-5 when $C_1 = C_2 = C_3 = 2 \text{ mF}$, $v_1(0) = 10 \text{ V}$, and $v_2(0) = v_3(0) = 20 \text{ V}$.

Solution

Because C_2 and C_3 are in parallel, we replace them with C_p , where

$$C_p = C_2 + C_3 = 4 \text{ mF}$$

The voltage at $t = 0$ across the equivalent capacitance C_p is equal to the voltage across C_2 or C_3 , which is $v_2(0) = v_3(0) = 20 \text{ V}$. As a result of replacing C_2 and C_3 with C_p , we obtain the circuit shown in Figure 7.4-6.

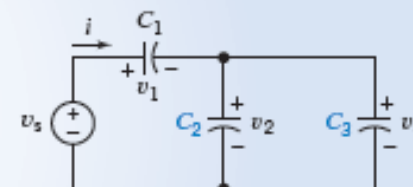


FIGURE 7.4-5 Circuit for Example 7.4-1.

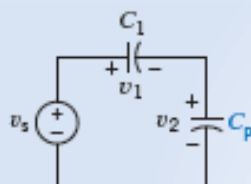


FIGURE 7.4-6

Circuit resulting from Figure 7.4-5 by replacing C_2 and C_3 with C_p .

We now want to replace the series of two capacitors C_1 and C_p with one equivalent capacitor. Using the relationship of Eq. 7.4-9, we obtain

$$C_s = \frac{C_1 C_p}{C_1 + C_p} = \frac{(2 \times 10^{-3})(4 \times 10^{-3})}{(2 \times 10^{-3}) + (4 \times 10^{-3})} = \frac{8}{6} \text{ mF}$$

The voltage at $t = 0$ across C_s is

$$v(0) = v_1(0) + v_p(0)$$

where $v_p(0) = 20 \text{ V}$, the voltage across the capacitance C_p at $t = 0$. Therefore, we obtain

$$v(0) = 10 + 20 = 30 \text{ V}$$

Thus, we obtain the equivalent circuit shown in Figure 7.4-7.

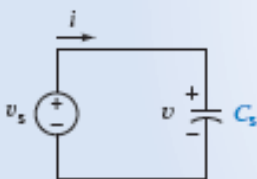



FIGURE 7.4-7

Equivalent circuit for the circuit of Example 7.4-1.

Example 7.5-1

- Find the voltage across an inductor, $L=0.1$ H, when the current in the inductor is:

$$i(t) = 20 \cdot t \cdot e^{-2t} \text{ A}, \quad t > 0, i(0) = 0$$

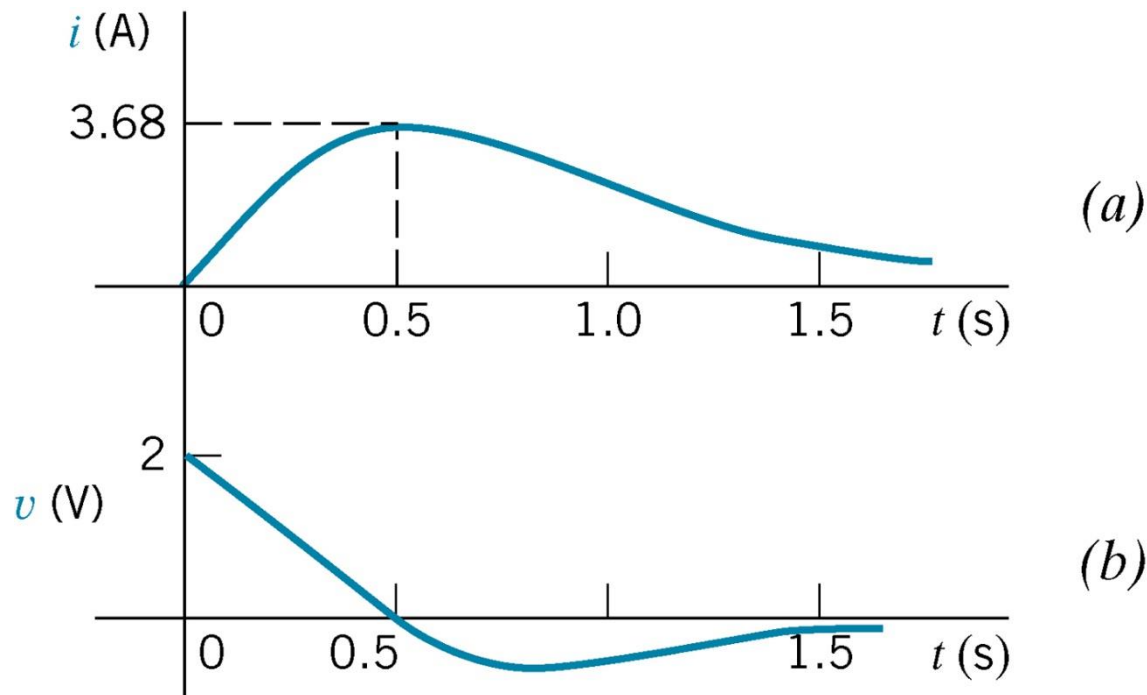

Example 7.5-1 Solution

Ex 7.5-1

 $L = 0.1 \text{ H}$

$$i(t) = 20 \cdot t e^{-2t} \text{ A}, \quad t \geq 0, \quad i(0) = 0.$$

for $t \geq 0$.

$$\begin{aligned} v(t) &= L \frac{di}{dt} = (0.1) \frac{d(20 \cdot t e^{-2t})}{dt} \\ &= (0.1) \cdot (20) (t e^{-2t}' + t' e^{-2t}) \\ &= 2 \cdot (-2t e^{-2t} + e^{-2t}) \\ &= \underline{2 \cdot e^{-2t} (1 - 2t) \text{ V}}. \end{aligned}$$

Example 7.5-1 Solution

Find the voltage across an inductor, $L = 0.1$ H, when the current in the inductor is

$$i(t) = 20te^{-2t} \text{ A}$$

for $t > 0$ and $i(0) = 0$.

Solution

The voltage for $t < 0$ is

$$v(t) = L \frac{di}{dt} = (0.1) \frac{d}{dt} (20te^{-2t}) = 2(-2te^{-2t} + e^{-2t}) = 2e^{-2t}(1 - 2t) \text{ V}$$

The voltage is equal to 2 V when $t = 0$, as shown in Figure 7.5-6b. The current waveform is shown in Figure 7.5-6a.


Example 7.5-3

- Calculate R and L if $i_L(0) = -3.5$ A, the input to the circuit is the voltage:

$$v(t) = 4 \cdot e^{-20t} \text{ V}, \quad t > 0$$

and the output is the current:

$$i(t) = -1.2 \cdot e^{-20t} - 1.5 \text{ A}, \quad t > 0$$

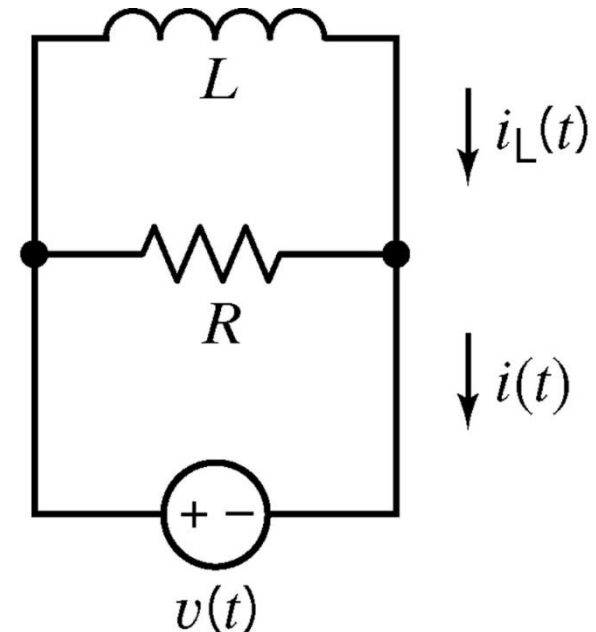

Example 7.5-3 Solution


- the input to the circuit is the voltage;

$$v(t) = 4 \cdot e^{-20t} \text{ V}, \quad t > 0 \quad \text{--- (1)}$$

- the output is the current

$$i(t) = -1.2 \cdot e^{-20t} - 1.5 \text{ A}, \quad t > 0 \quad \text{--- (2)}$$
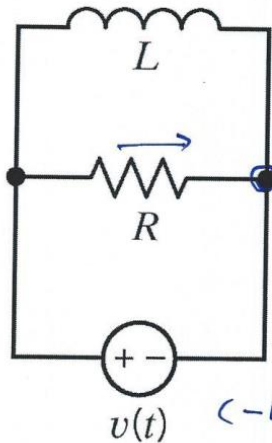
$$i_L(0) = -3.5 \text{ A} \quad \text{--- (3)}$$



$i_L(t)$ KCL

$$i(t) = \frac{v(t)}{R} + i_L(t)$$

$$i(t) = \frac{v(t)}{R} + \left[i(t_0) + \frac{1}{L} \int_{t_0}^t v(\tau) d\tau \right]$$

$$(-1.2 e^{-20t} - 1.5) = \frac{4 e^{-20t}}{R} - 3.5 + \frac{1}{L} \int_0^t 4 e^{-20\tau} d\tau$$

$$= \frac{4 e^{-20t}}{R} - 3.5 + \frac{4}{L(-20)} (e^{-20t} - 1)$$

$$= e^{-20t} \left(\frac{4}{R} - \frac{1}{5L} \right) - 3.5 + \frac{1}{5L}$$

$$-1.5 = -3.5 + \frac{1}{5L}, \quad L = 0.1 \text{ H}$$

$$-1.2 = \frac{4}{R} - \frac{1}{5L}, \quad R = 5 \Omega$$

$$v(t) = L \frac{di(t)}{dt}$$

$$i(t) = i(t_0) + \frac{1}{L} \int_{t_0}^t v(\tau) \cdot d\tau$$

Example 7.5-3 Solution

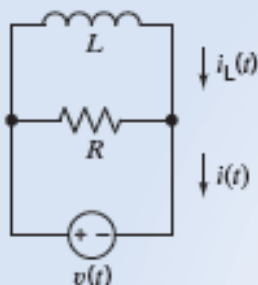


FIGURE 7.5-8 The circuit considered in Example 7.5-3.

The input to the circuit shown in Figure 7.5-8 is the voltage

$$v(t) = 4e^{-20t} \text{ V for } t > 0$$

The output is the current

$$i(t) = -1.2e^{-20t} - 1.5 \text{ A for } t > 0$$

The initial inductor current is $i_L(0) = -3.5 \text{ A}$. Determine the values of the inductance L and resistance R .

Solution

Apply KCL at either node to get

$$i(t) = \frac{v(t)}{R} + i_L(t) = \frac{v(t)}{R} + \left[\frac{1}{L} \int_0^t v(\tau) d\tau + i(0) \right]$$

That is

$$\begin{aligned} -1.2e^{-20t} - 1.5 &= \frac{4e^{-20t}}{R} + \frac{1}{L} \int_0^t 4e^{-20\tau} d\tau - 3.5 = \frac{4e^{-20t}}{R} + \frac{4}{L(-20)}(e^{-20t} - 1) - 3.5 \\ &= \left(\frac{4}{R} - \frac{1}{5L} \right) e^{-20t} + \frac{1}{5L} - 3.5 \end{aligned}$$

Equating coefficients gives


$$-1.5 = \frac{1}{5L} - 3.5 \Rightarrow L = 0.1 \text{ H}$$

and

$$-1.2 = \frac{4}{R} - \frac{1}{5L} = \frac{4}{R} - \frac{1}{5(0.1)} = \frac{4}{R} - 2 \Rightarrow R = 5 \Omega$$


Example 7.7-1

- Find L_{eq} assuming that $i(0) = 0$ A.

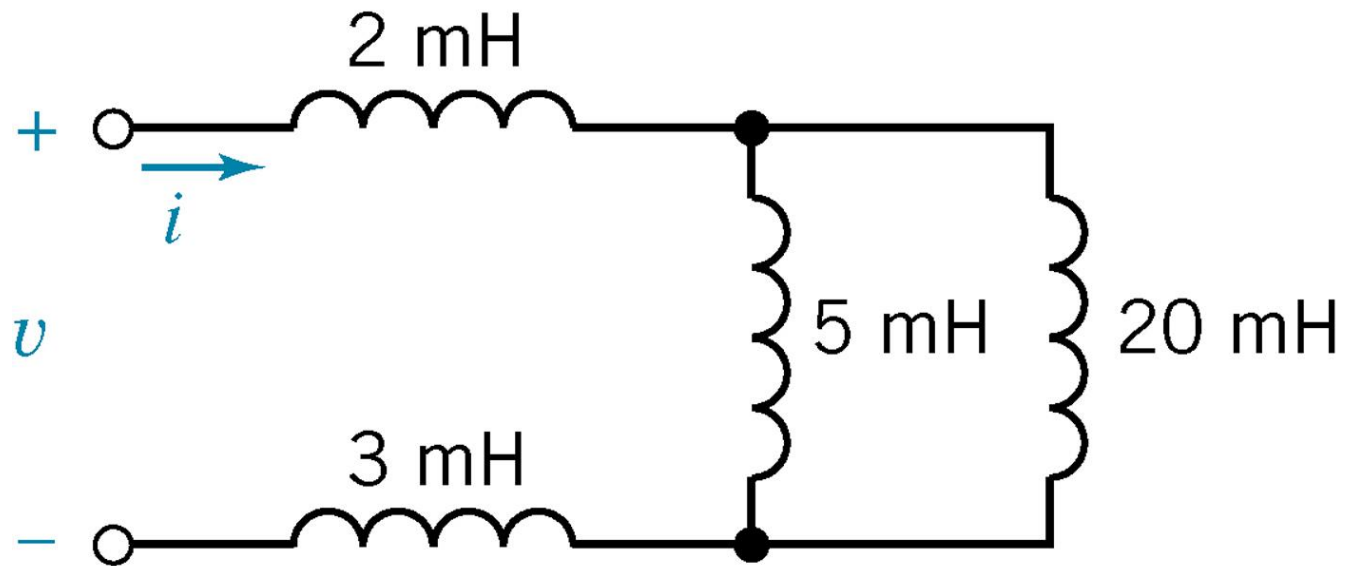


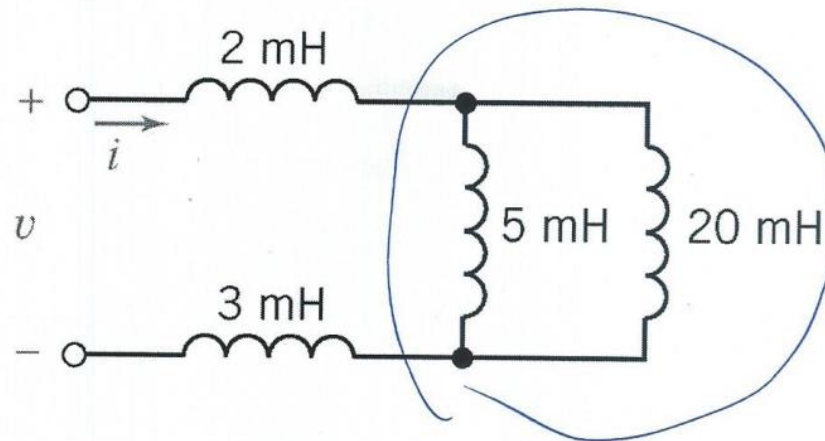Example 7.7-1 Solution

Find the L_{eq} where $i(0) = 0 \text{ A}$


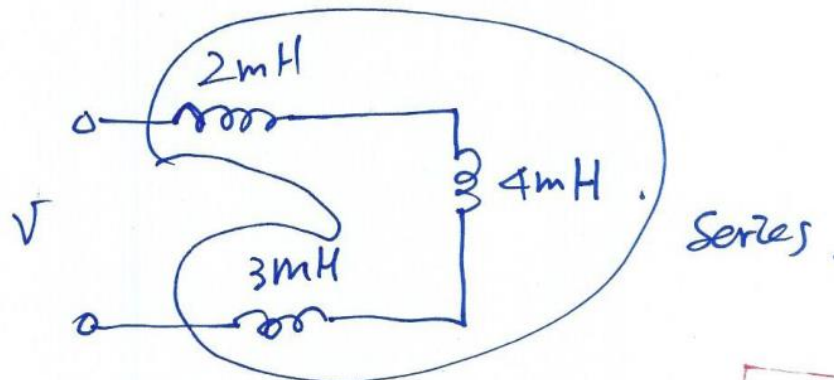
$$L_{eq} = \frac{5 \text{ m} \cdot 20 \text{ m}}{5 \text{ m} + 20 \text{ m}} = 4 \text{ mH}.$$



Series.

$$L_{eq} = 2 \text{ mH} + 4 \text{ mH} + 3 \text{ mH} = \boxed{9 \text{ mH}}$$

Example 7.7-1 Solution

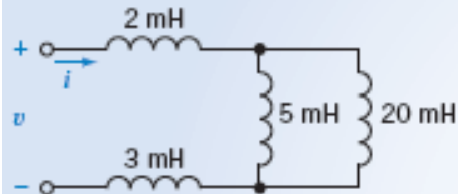


FIGURE 7.7-5 The circuit of Example 7.7-1.

Find the equivalent inductance for the circuit of Figure 7.7-5. All the inductor currents are zero at t_0 .

Solution

First, we find the equivalent inductance for the 5-mH and 20-mH inductors in parallel.

From Eq. 7.7-4, we obtain

$$\frac{1}{L_p} = \frac{1}{L_1} + \frac{1}{L_2}$$

or

$$L_p = \frac{L_1 L_2}{L_1 + L_2} = \frac{5 \times 20}{5 + 20} = 4 \text{ mH}$$

This equivalent inductor is in series with the 2-mH and 3-mH inductors. Therefore, using Eq. 7.7-1, we obtain

$$L_{eq} = \sum_{n=1}^N L_n = 2 + 3 + 4 = 9 \text{ mH}$$