

# CPE201

# Digital Design

By Benjamin Haas

Class 6: More Gates, Timing, and Chips




# NOT Timing

Truth tables:

a	b	AND
0	0	0
0	1	0
1	0	0
1	1	1


a	b	OR
0	0	0
0	1	1
1	0	1
1	1	1

a	NOT
0	1
1	0

 

 
# Example

- If  $C = 1$ , what is the value at the other



# AND Timing

 

Truth tables:

a	b	AND
0	0	0
0	1	0
1	0	0
1	1	1



a	b	OR
0	0	0
0	1	1
1	0	1
1	1	1

a	NOT
0	1
1	0



# Example

- Draw the output waveform.

  


# OR Timing

Truth tables:

a	b	AND
0	0	0
0	1	0
1	0	0
1	1	1

a	b	OR
0	0	0
0	1	1
1	0	1
1	1	1


a	NOT
0	1
1	0

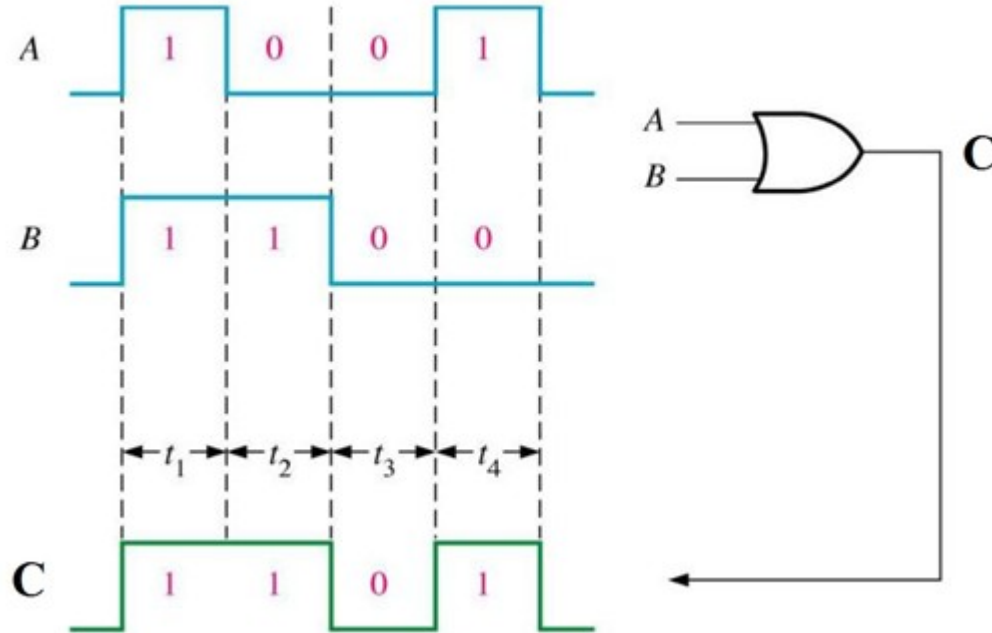


# NAND Gates

- NAND = NOT AND
- AND with inverted output
- $C = \overline{AB} = (AB)'$


A	B	A <b>NAND</b> B
0	0	1
0	1	1
1	0	1
1	1	0

 

# NAND Timing

 


 
*A and B are both HIGH during these four time intervals. Therefore X is LOW.*





# Example

- Draw the output waveform.

  



# NOR Gates

- NOR NOT OR
- OR with inverted output
- $C = \overline{A+B} = (A+B)'$

A	B	A <b>NOR</b> B
0	0	1
0	1	0
1	0	0
1	1	0





# NOR Timing

  

# Example

- Draw the output waveform

  


# Why NAND and NOR?


- Universal gates (to be discussed later)
  - Any of the other gates (and more) can be built from NAND, NOR, and NOT
- Smaller sized implementations
- Faster logic



# NAND and NOR Equivalents

 

A	B	A <b>NAND</b> B
0	0	1
0	1	1
1	0	1
1	1	0

 

A	B	A <b>NOR</b> B
0	0	1
0	1	0
1	0	0
1	1	0


- Foreshadowing...



# XOR and XNOR

- Exclusive-OR and Exclusive-NOR
  - A combination of the logic already discussed

Given their own unique

 

# XOR


- Outputs a 1 when either of the inputs is 1 (exclusively one of the inputs is 1)
- Outputs a 0 otherwise
- $C = B$
- Example application: addit

A	B	A XOR B
0	0	0
0	1	1
1	0	1
1	1	0





# XOR Timing

 



# XNOR

- Invert the output of XOR
- $C = \overline{A \oplus B} = (A \oplus B)'$



A	B	A <b>XNOR</b> B
0	0	1
0	1	0
1	0	0
1	1	1




# XNOR Timing

  



# Breadboards vs PCBs

  


# PCBs

 


# Through hole vs Surface Mount

  


# IC Packages

 


Dual in-line package (DIP)

 



SSOP ( $153 \times 193$  mils)

 

LQFP ( $7 \times 7$  mm)

 

QFN

  




FBGA bottom view  
( $4 \times 4$  mm)



# Packages


Metric code	Imperial code
0402	01005
0603	0201
1005	0402
1608	0603
2012	0805
2520	1008
3216	1206
3225	1210
4516	1806
4532	1812
5025	2010
6332	2512

Actual size

  
 




# Tape and Reel

 


# Pick and Place/Wave Solder

  


# Pins

- Check the datasheet!

 

DIP or SSOP

 

PLCC or LCC



# Example

Figure 5-1. LQFP64 package outline

 


Table 5-1. LQFP64 package dimensions

Symbol	Min	Typ	Max
A	—	—	1.60
A1	0.05	—	0.15
A2	1.35	1.40	1.45
A3	0.59	0.64	0.69
b	0.18	—	0.26
b1	0.17	0.20	0.23
c	0.13	—	0.17
c1	0.12	0.13	0.14
D	11.80	12.00	12.20
D1	9.90	10.00	10.10
E	11.80	12.00	12.20
E1	9.90	10.00	10.10
e	—	0.50	—
eB	11.25	—	11.45
L	0.45	—	0.75
L1	—	1.00	—
$\theta$	0°	—	7°



# Reading

- This lecture
  - Sections 3.4-3.6, 1.6
- Next lecture
  - Sections 3.7, 1.7, 4.1-4.2

