

# CPE201

# Digital Design


By Benjamin Haas

Class 16: Multiplexers and Parity



 
# Multiplexer

- Usually called a MUX
- Has both encoder and decoder inputs
  - $n$  selection inputs and  $2^n$  data inputs
  - One output
  - $n$  selects which of  $2^n$  is on the output



# MUX

Data-Select Inputs		Input Selected
$S_1$	$S_0$	
0	0	$D_0$
0	1	$D_1$
1	0	$D_2$
1	1	$D_3$

 

# MUX

The data output is equal to  $D_0$  only if  $S_1 = 0$  and  $S_0 = 0$ :  $Y = D_0\bar{S}_1\bar{S}_0$ .

The data output is equal to  $D_1$  only if  $S_1 = 0$  and  $S_0 = 1$ :  $Y = D_1\bar{S}_1S_0$ .

The data output is equal to  $D_2$  only if  $S_1 = 1$  and  $S_0 = 0$ :  $Y = D_2S_1\bar{S}_0$ .


The data output is equal to  $D_3$  only if  $S_1 = 1$  and  $S_0 = 1$ :  $Y = D_3S_1S_0$ .

$$Y = D_0\bar{S}_1\bar{S}_0 + D_1\bar{S}_1S_0 + D_2S_1\bar{S}_0 + D_3S_1S_0$$




# MUX


Data-Select Inputs		Input Selected
$S_1$	$S_0$	
0	0	$D_0$
0	1	$D_1$
1	0	$D_2$
1	1	$D_3$

 

# Example

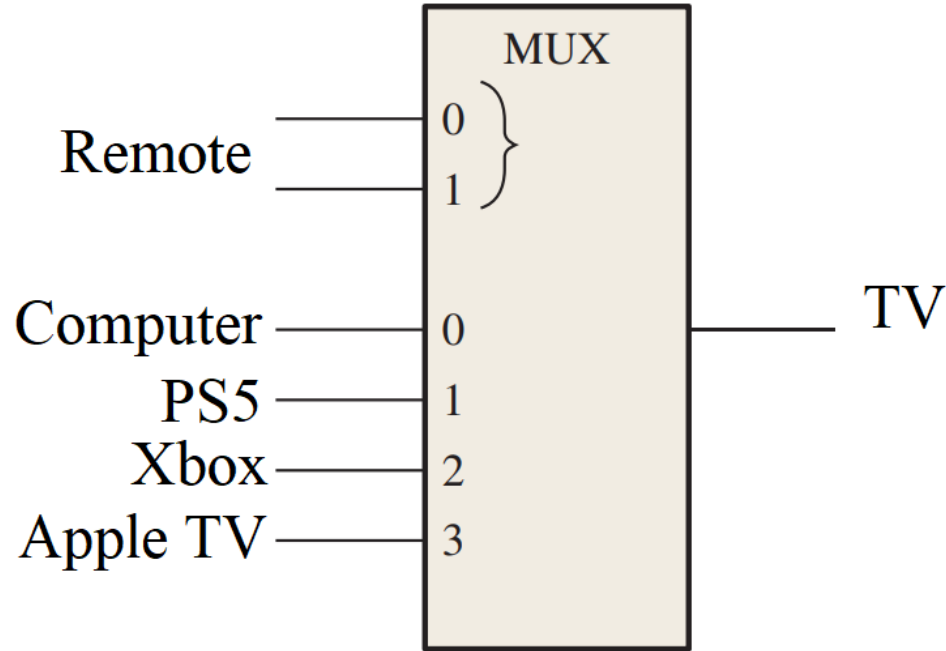

# Example

 

# Transmission Modes


- Simplex Transmission Mode
  - Television, radio, above MUX circuit
- Half Duplex Transmission Mode
  - Walkie-talkie
- Full Duplex Transmission Mode
  - Phones





# Half Duplex Example


- Not really a MUX, but a MUX switch

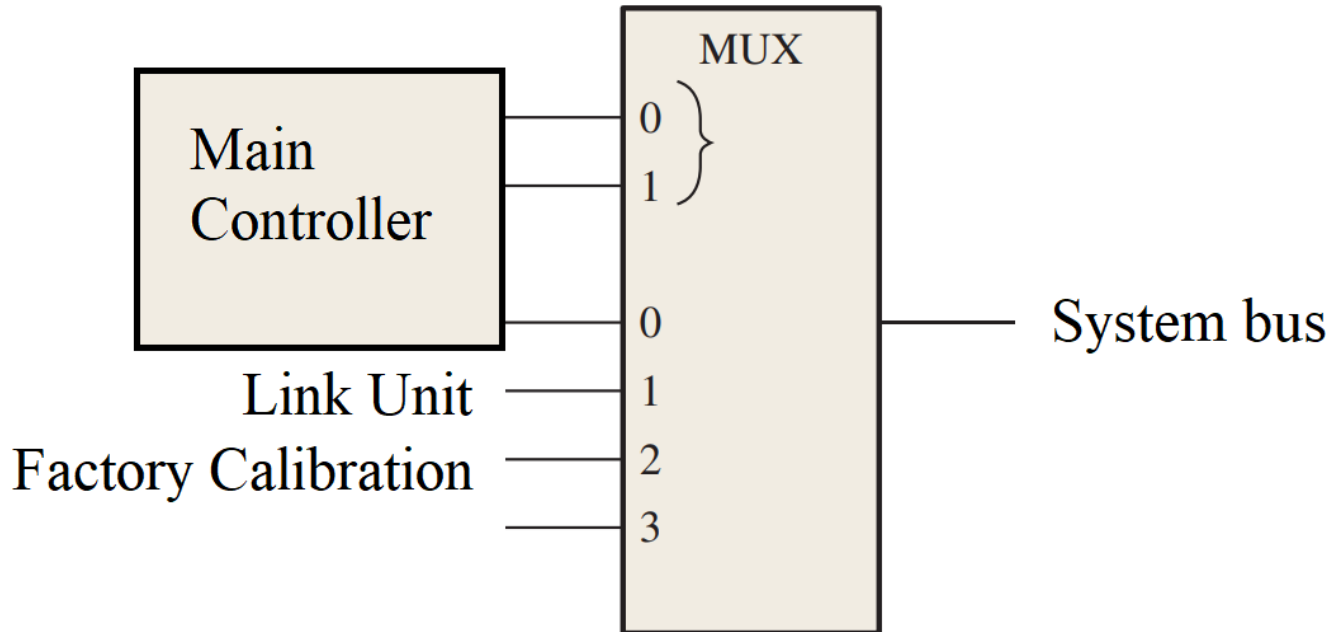


TMUX1247 Block Diagram

# Real Chips – 74HC153

- Dual 4-input MUX
- Now with enable

 

(a) Pin diagram

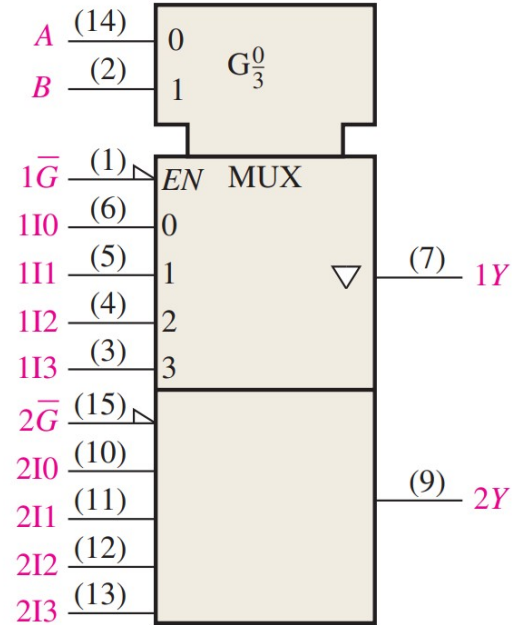


(b) Logic symbol


The 74HC153 dual four-input data selector/multiplexer.

# Real Chips – 74HC151

- 8-input MUX

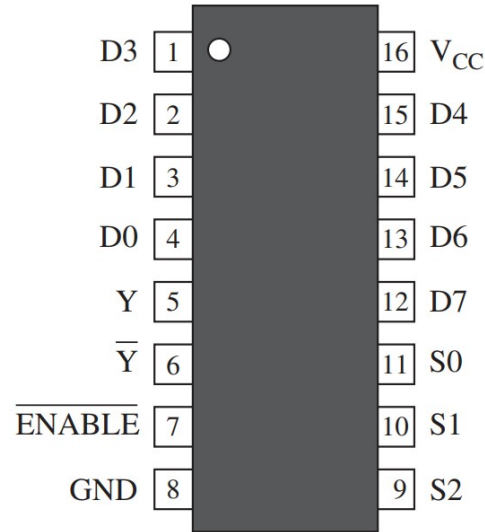

(a) Pin diagram

 

(b) Logic symbol

The 74HC151 eight-input data selector/multiplexer.


# Demultiplexer (DEMUX)

- Reverse of MUX
  - $n$  selection inputs and one data input
  - $2^n$  data outputs
  - $n$  selects pins tell which of  $2^n$  the input goes onto



# DEMUX


S1	S0	D3	D2	D1	D0
0	0	0	0	0	Input
0	1	0	0	Input	0
1	0	0	Input	0	0
1	1	Input	0	0	0

 

# Decoder as DEMUX

- One CS line becomes data input

Active low example

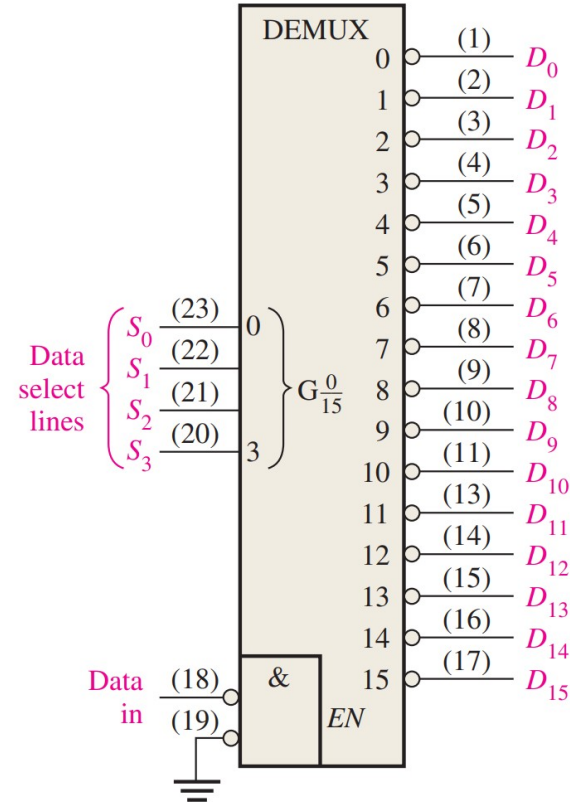

# DEMUX Applications

- Like a chip select to pick what subsystem to communicate with
  - Computer to projector or monitor
- Memory addressing and comms
- Serial to parallel conversion



# Parity

- A form of error checking
- Even parity - # of 1's in a transmission is even
  - Sum of all bits is 0
- Odd parity - # of 1's in a transmission is odd
  - Sum of all bits is 1





# Examples

- Even or odd parity?
- 1000 0100
- 1010 0101
- 1110 0000
- 0110 0100
- 0110 1010



# Parity for Error Checking

- One less data bit than packet size
  - Replaced with parity bit
  - Packets without parity are discarded
    - Packet can be any size
    - Larger packets should have more robust error checking



# Communication w/Parity

- One form of parity must be chosen
- Generate parity bits to ensure the chosen form
- Parity check passes if received data has the chosen form, otherwise error occurred



# Examples

- Assume even parity communication
  - Find the parity bit x
- 1000 010x
- 1010 010x
- 1110 000x
- 0110 010x
- 0110 101x




# Examples

- Assume even parity communication
  - Is there a packet error?
- 1000 0101
- 1010 0100
- 1110 0001
- 0110 0101
- 0110 1011



 
# Generating Parity


- Sum all bits to get even parity bit
- Sum and NOT to get odd parity



Summing of two bits

 

Summing of four bits

 

# Checking Parity


- Same as generating, but with an extra bit
  - Use opposite parity to indicate an error



# Real Chips – 74HC280


- 9-bit parity generator/chec

Number of Inputs <i>A–I</i> that Are High	Outputs	
	$\Sigma$ Even	$\Sigma$ Odd
0, 2, 4, 6, 8	H	L
1, 3, 5, 7, 9	L	H

 



# Use

 

# Reading

- This lecture
  - Sections 6.8-6.10
- Next lecture
  - Sections 5.7, 6.11, 7.1

