

Chapter 7


Energy Storage Elements

- This chapter introduces two more circuit elements, the capacitor (C) and the inductor (L). The constitutive equations for the devices involve either integration or differentiation.
 - Electric circuits that contain capacitors and/or inductors are represented by differential equations. We say that circuits containing capacitors and/or inductors are dynamic circuits.
 - Circuits that contain capacitors and/or inductors are able to store energy.
 - Capacitor voltages and inductor currents are **continuous** functions of time.
 - Series or parallel capacitors can be reduced to an equivalent capacitor. Series or parallel inductors can be reduced to an equivalent inductor.


The Impact of “Time”

- Up to this point we have assumed that everything happens **instantaneously**
- We will now discuss elements that have input-output relationships depending on time
- These elements can “**store**” energy
- At different times they may either produce or absorb energy
- These elements are called “**energy storage elements**”


Example of Energy Storing Systems

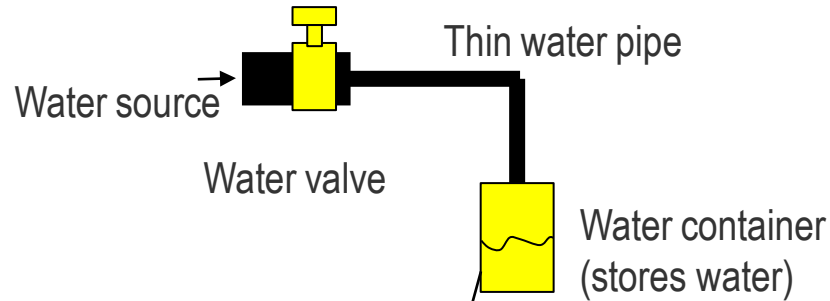


Amount of
Water
in the Tank

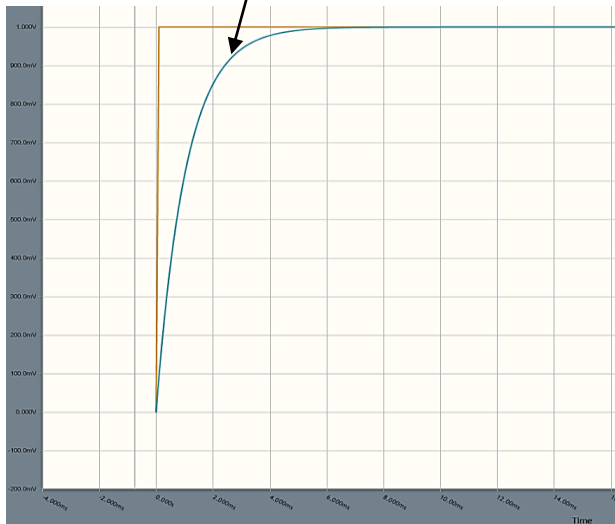

Time

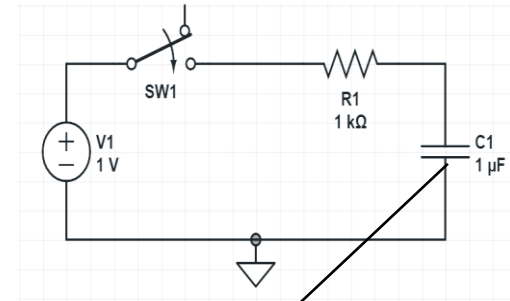

Amount of
Charge in
the
Capacitor

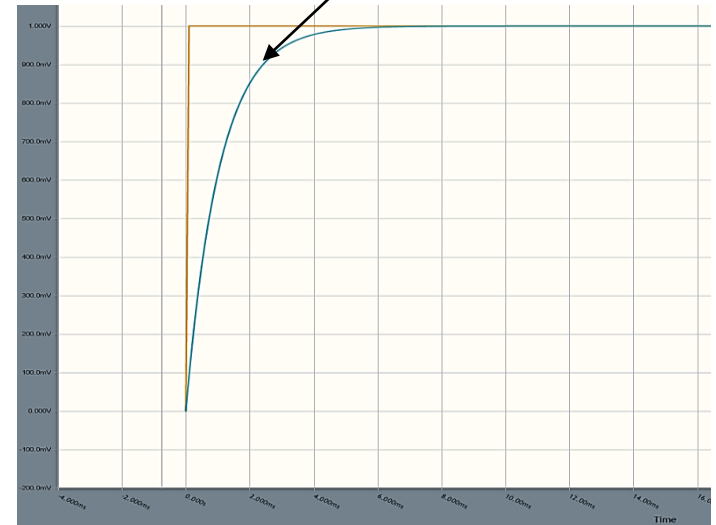

Time

Energy Storage Elements

- **Capacitors** store energy in an electric field
- **Inductors** store energy in a magnetic field
- Capacitors and inductors are passive elements:
 - Can store energy supplied by a circuit
 - Can return stored energy to a circuit
 - Cannot supply more energy to a circuit than the energy it stored

- **Capacitors** and **Inductors** are used to model electrical power transmission lines along with resistors
- Energy storage elements are used to model electrical loads:
 - **Capacitors** model computers and other electronics (power supplies)
 - **Inductors** model (large/small) motors

CAPACITORS

<https://www.youtube.com/watch?v=X4EUwTwZ110>



Capacitance

- Capacitors are represented by a parameter called *capacitance*.
- Capacitance occurs when two **conductors** (plates) are separated by a **dielectric** (insulator)
- Capacitance is a measure of the ability of a device to store energy in the form of a separated charge or an electric field



- Charge builds up on each of the plates when a voltage is applied
- Charge on the two conductors creates an electric field
- A capacitor is a circuit element that stores energy in an electric field

Symbol

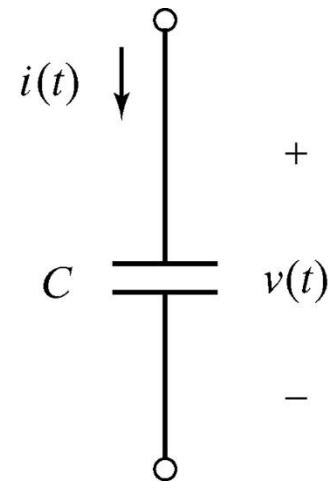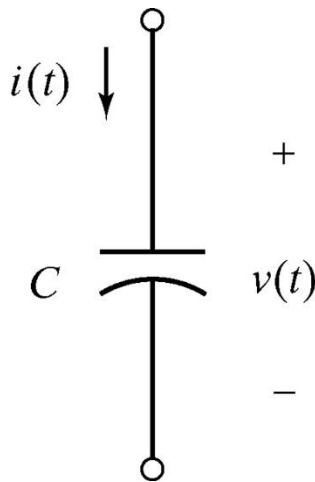

Capacitance

- The voltage difference between the two conductors is proportional to the charge:

$$q = C \cdot v$$

- The proportionality constant C is called *capacitance*.
- Units: **Farads** ($F = \text{Coulomb/Volt}$)

$$C = \frac{\varepsilon \cdot A}{d}$$


$$q = \frac{\varepsilon \cdot A}{d} \cdot v$$

C : capacitance in Farads (F)


ε : permittivity in F/m ($8.854 \cdot 10^{-12} \cdot \varepsilon_r$)

A : area in m^2


d : length in m

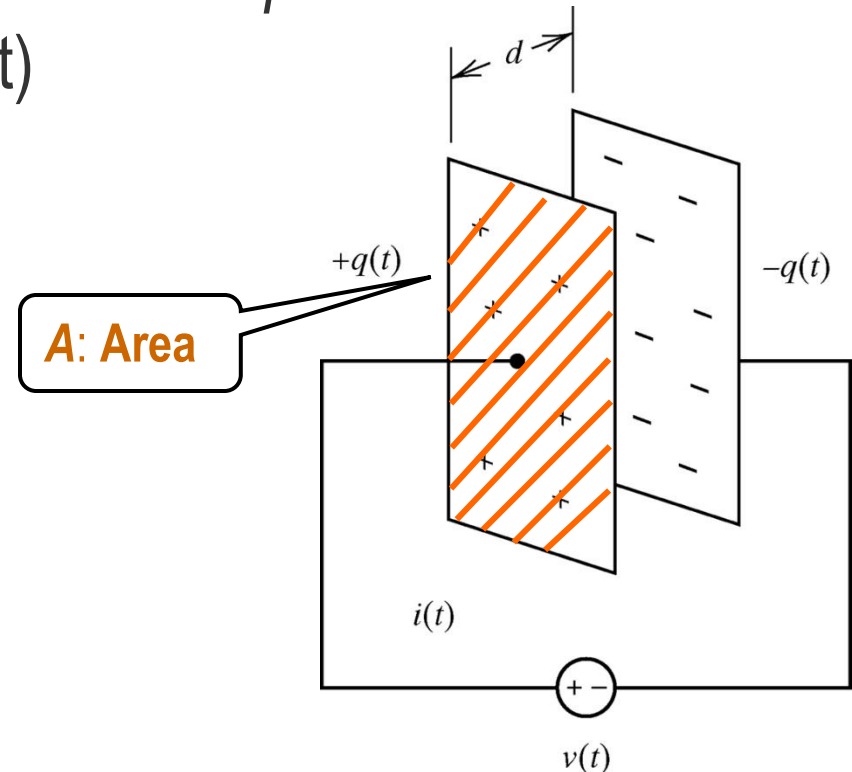

Capacitor (DC)

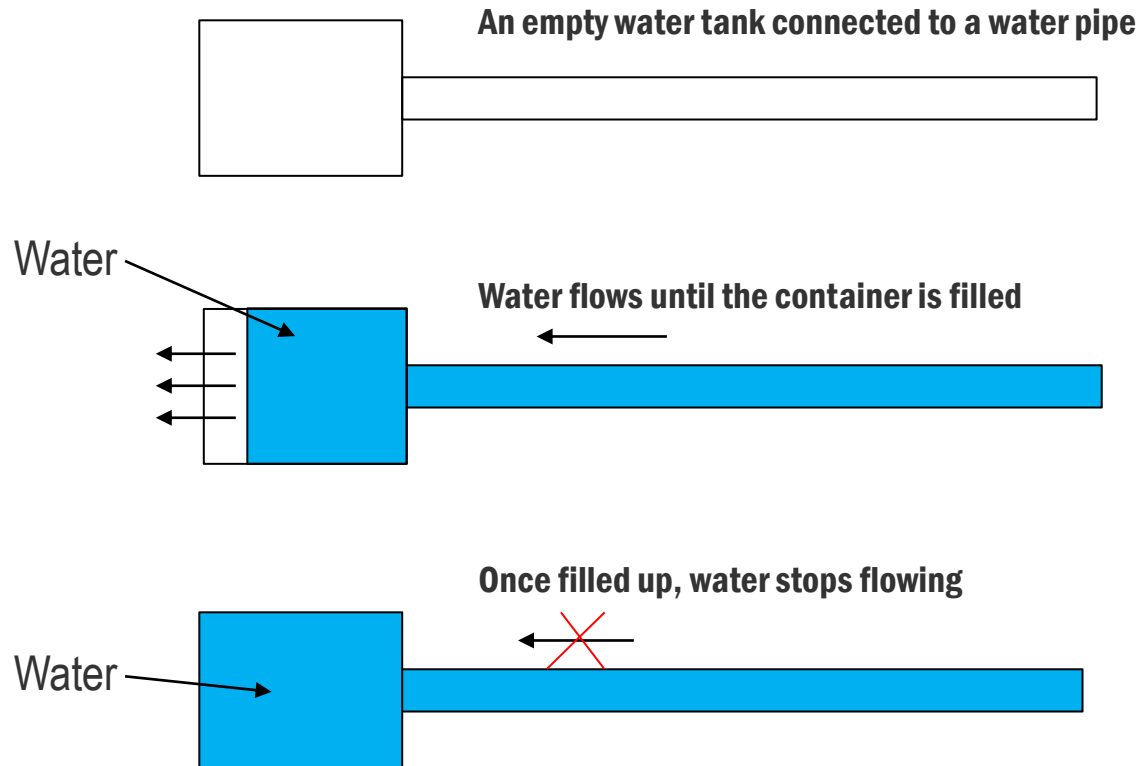

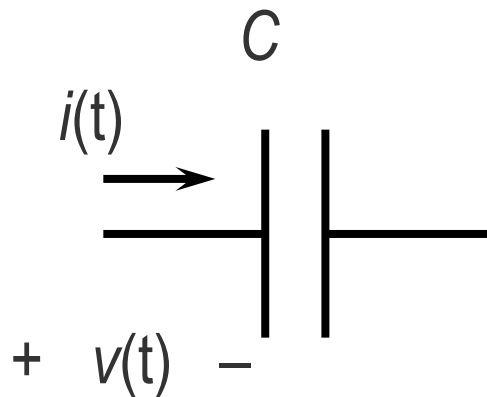DC current flowing into the water will be eventually stopped
Likewise, DC current flowing into a capacitor will be eventually stopped
A capacitor is a DC blocking element




$$q(t) = C \cdot v(t)$$

$$\frac{d}{dt}[q(t)] = \frac{d}{dt}[C \cdot v(t)]$$

$$\frac{dq(t)}{dt} = C \frac{dv(t)}{dt}$$

$$i(t) = C \frac{dv(t)}{dt}$$

I-V Relationship

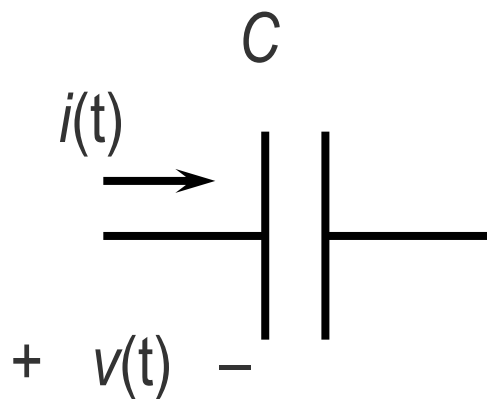

$$i(t) = C \frac{dv(t)}{dt}$$

$$\Rightarrow i(\tau) \cdot d\tau = C \cdot dv(\tau)$$

$$\Rightarrow \int_{t_0}^t i(\tau) \cdot d\tau = \int_{v(t_0)}^{v(t)} C \cdot dv(\tau)$$


Initial time

$$\Rightarrow \int_{t_0}^t i(\tau) \cdot d\tau = C[v(t) - v(t_0)]$$

$$\Rightarrow v(t) = v(t_0) + \frac{1}{C} \int_{t_0}^t i(\tau) \cdot d\tau$$

Initial condition

I-V Relationship

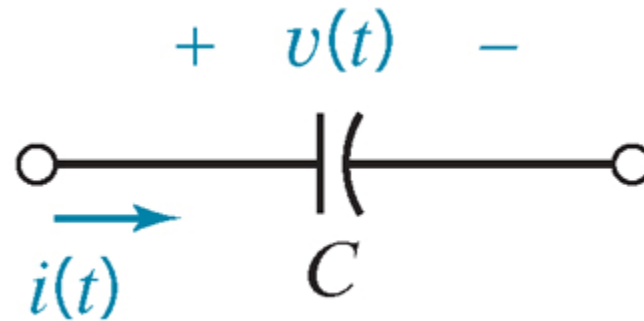

$$i(t) = C \frac{d}{dt} v(t)$$



$$v(t) = \frac{1}{C} \int_{t_0}^t i(\tau) d\tau + v(t_0)$$

Voltage across a capacitor **CANNOT** change instantaneously

These equations define the behavior of the **capacitors**

Example 7.2-1

- $C = 1 \text{ mF}$ and the voltage across the capacitor is given below. Calculate the current $i(t)$ through the capacitor.

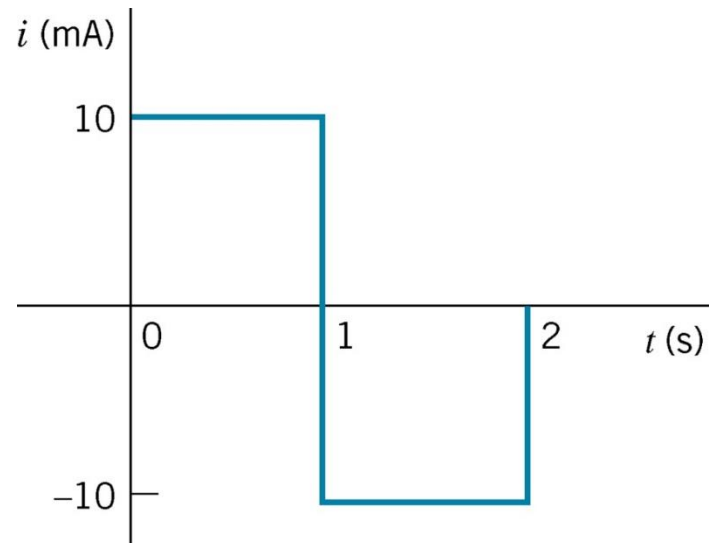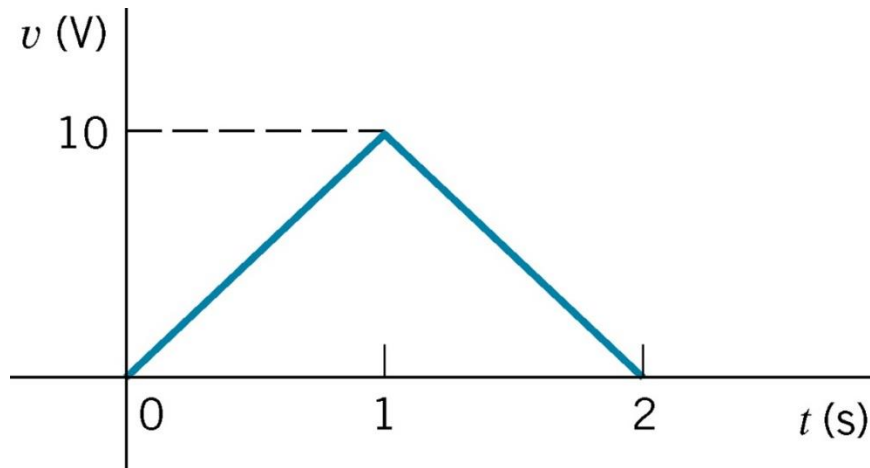

Example 7.2-5


- The input current is:

$$i(t) = 3.75e^{-1.2t} \text{ A for } t > 0$$

- The output capacitor voltage is:



$$v(t) = 4 - 1.25e^{-1.2t} \text{ V for } t > 0$$

- Find the value of the capacitance, **C**.

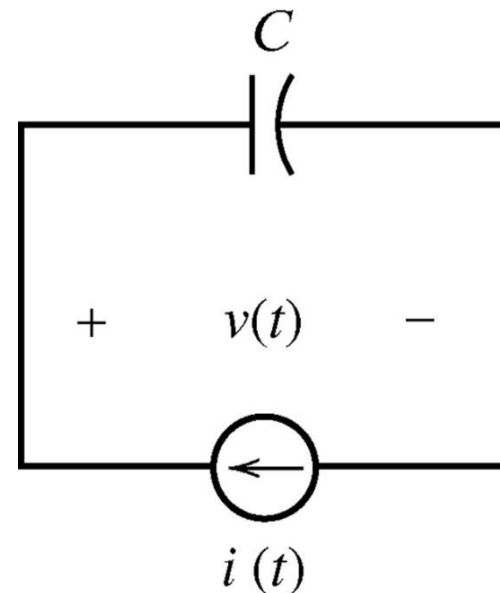


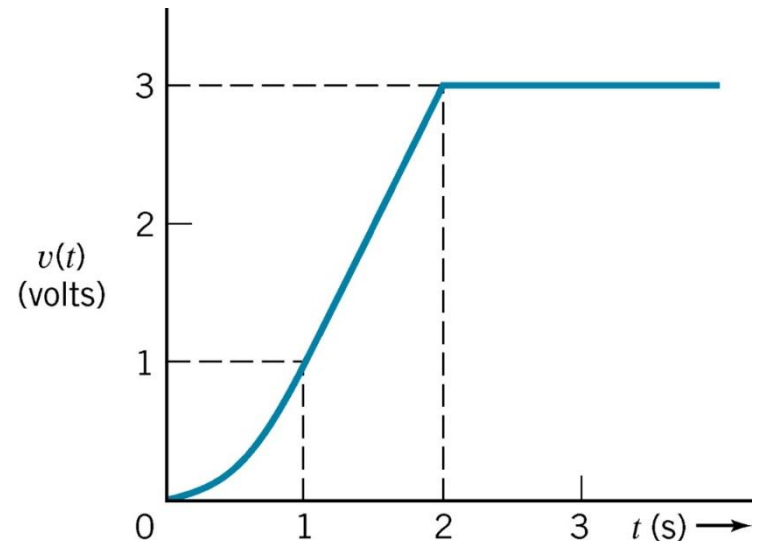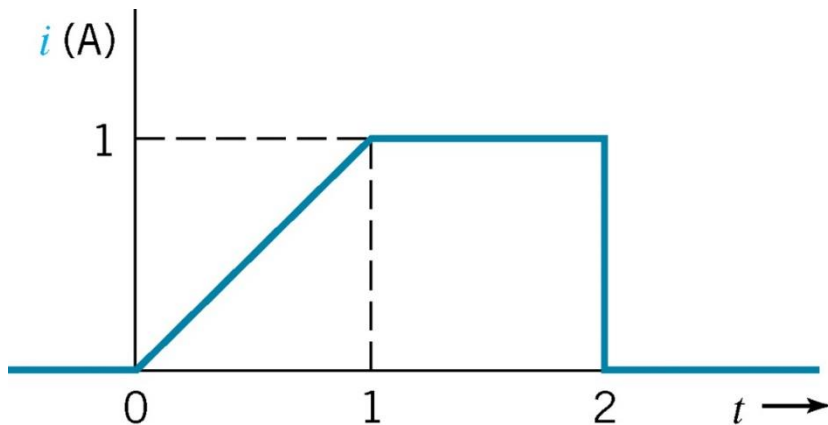Example 7.2-2

- $C = \frac{1}{2} \text{ F}$, the current through the capacitor is given below. Calculate the voltage $v(t)$ across the capacitor.



Power Stored in a Capacitor

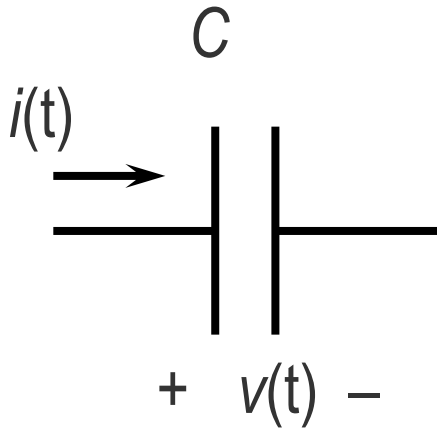


$$i(t) = C \frac{dv(t)}{dt}$$

$$p(t) = v(t) \cdot i(t)$$

$$= v(t) \cdot C \frac{dv(t)}{dt}$$

$$p(t) = C \cdot v(t) \frac{dv(t)}{dt}$$

Energy Stored in a Capacitor

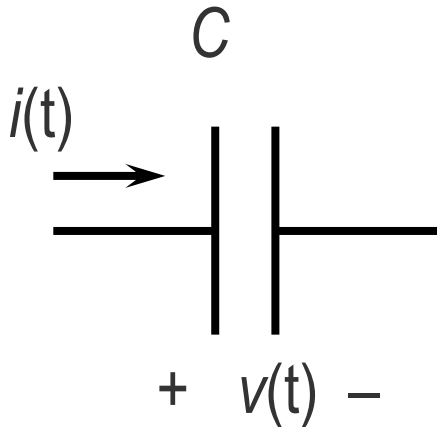


$$\begin{aligned}
 w(t) &= \int_{-\infty}^t p(t) dt = \int_{-\infty}^t C \cdot v(t) \frac{dv(t)}{dt} dt \\
 &= \int_{-\infty}^{v(t)} C \cdot v \cdot dv = C \int_{-\infty}^{v(t)} v \cdot dv \\
 &= \frac{1}{2} C \cdot v^2 \Big|_{v(-\infty)}^{v(t)} \\
 w(t) &= \frac{1}{2} C \cdot [v(t)^2 - v(-\infty)^2]
 \end{aligned}$$



Because the capacitor is uncharged at $t = -\infty$

$$w(t) = \frac{1}{2} C \cdot v(t)^2$$

Energy Stored in a Capacitor

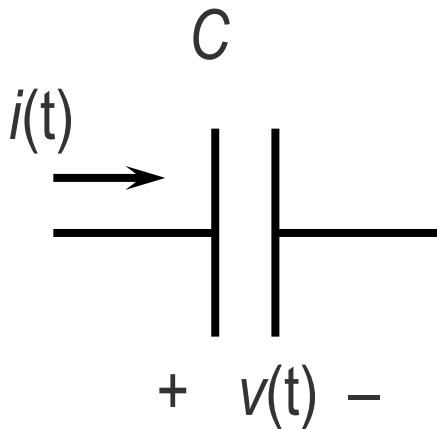

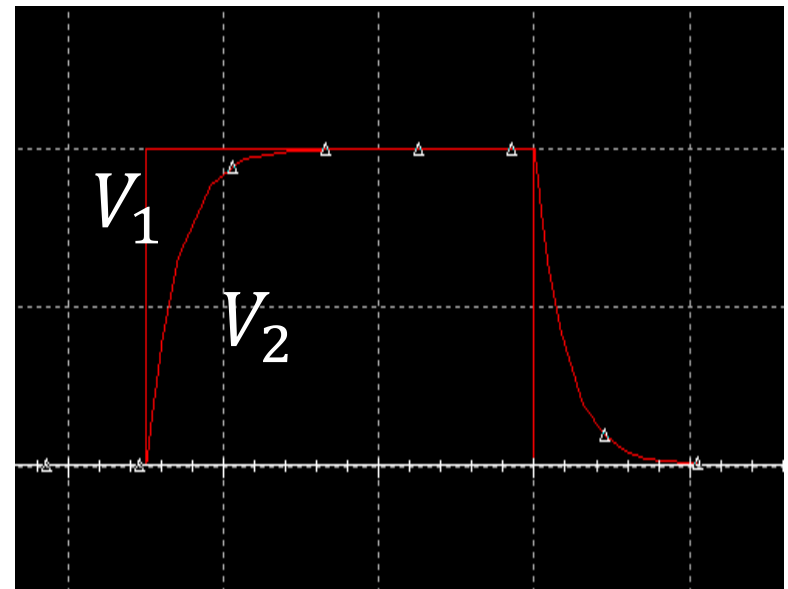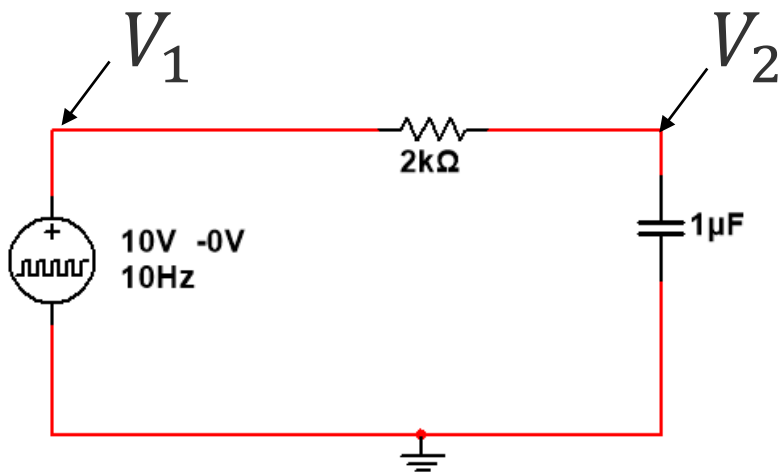
Voltage & Charge on a capacitor **CANNOT** change instantaneously. It takes time to charge the capacitor.



Multisim simulation result

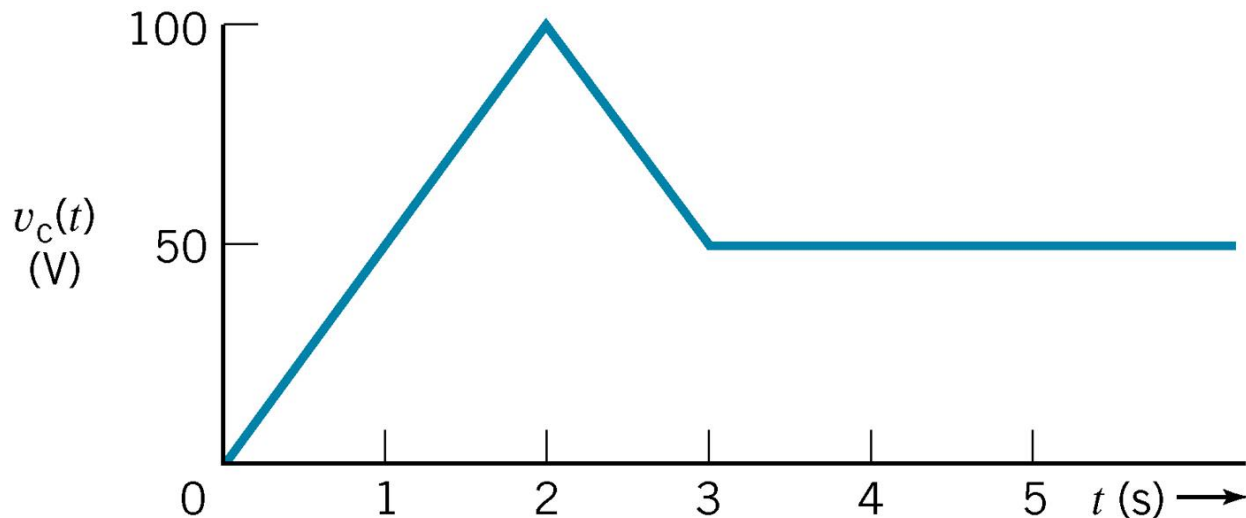Example 7.3-2

- The voltage across a 5-mF capacitor is shown below. Determine and plot the capacitor current, power and energy.



Series & Parallel Capacitors


- **Series capacitors** combine like **parallel resistors**

$$1/C_{eq-series} = 1/C_1 + 1/C_2 + 1/C_3 + \dots$$



- **Parallel capacitors** combine like **series resistors**

$$C_{eq-parallel} = C_1 + C_2 + C_3 + \dots$$


Series & Parallel Capacitors

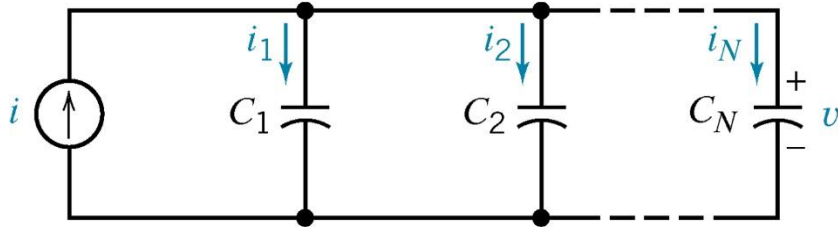

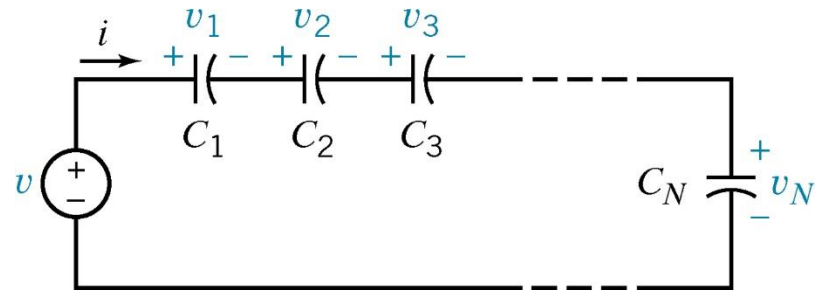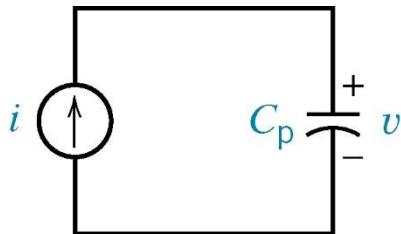
$$\begin{aligned}
 i &= i_1 + i_2 + i_3 + \dots + i_N \\
 &= C_1 \frac{dv}{dt} + C_2 \frac{dv}{dt} + \dots + C_N \frac{dv}{dt} \\
 &= (C_1 + C_2 + \dots + C_N) \frac{dv}{dt} \\
 i &= C_p \frac{dv}{dt}
 \end{aligned}$$


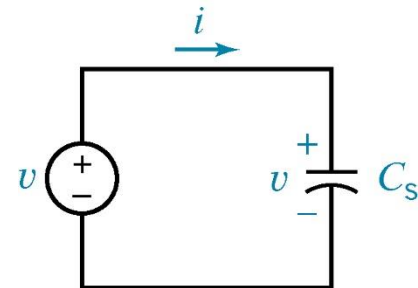
$$\begin{aligned}
 v &= v_1 + v_2 + v_3 + \dots + v_N \\
 &= \frac{1}{C_1} \int_{t_0}^t i \cdot d\tau + \frac{1}{C_2} \int_{t_0}^t i \cdot d\tau + \dots + \frac{1}{C_N} \int_{t_0}^t i \cdot d\tau \\
 &= \left(\frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_N} \right) \int_{t_0}^t i \cdot d\tau \\
 v &= \frac{1}{C_s} \int_{t_0}^t i \cdot d\tau
 \end{aligned}$$



Capacitors in Parallel

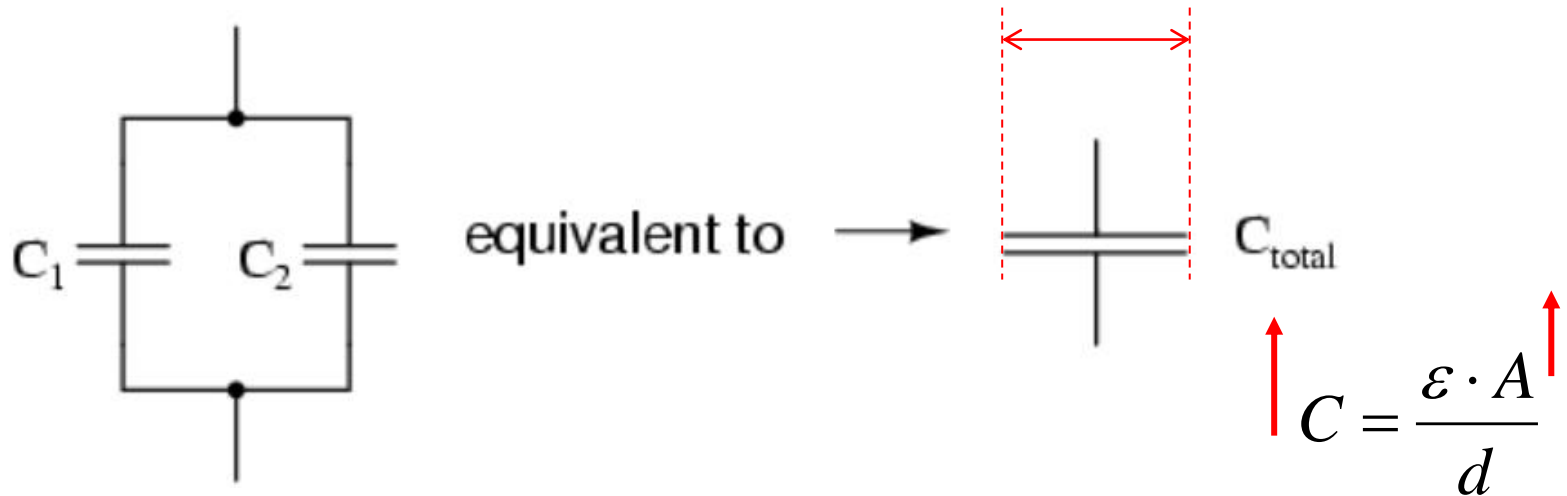


The overall effect is that of a single equivalent capacitor having the sum total of the plate areas of the individual capacitors.

The total capacitance is the sum of the individual capacitors' capacitances.

Parallel Capacitances

$$C_{eq} = C_1 + C_2 + \dots C_n$$

Capacitors in Series

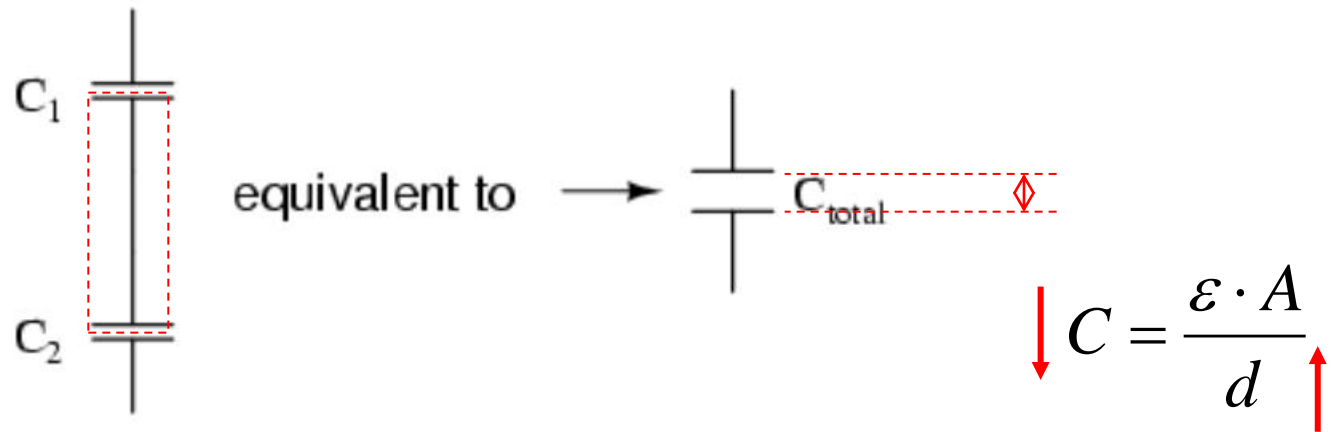

The overall effect is that of a single (equivalent) capacitor having the sum total of the plate spacings of the individual capacitors.


The total capacitance is less than any of the individual capacitors' capacitance.

Series Capacitances

$$C_{eq} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n}}$$

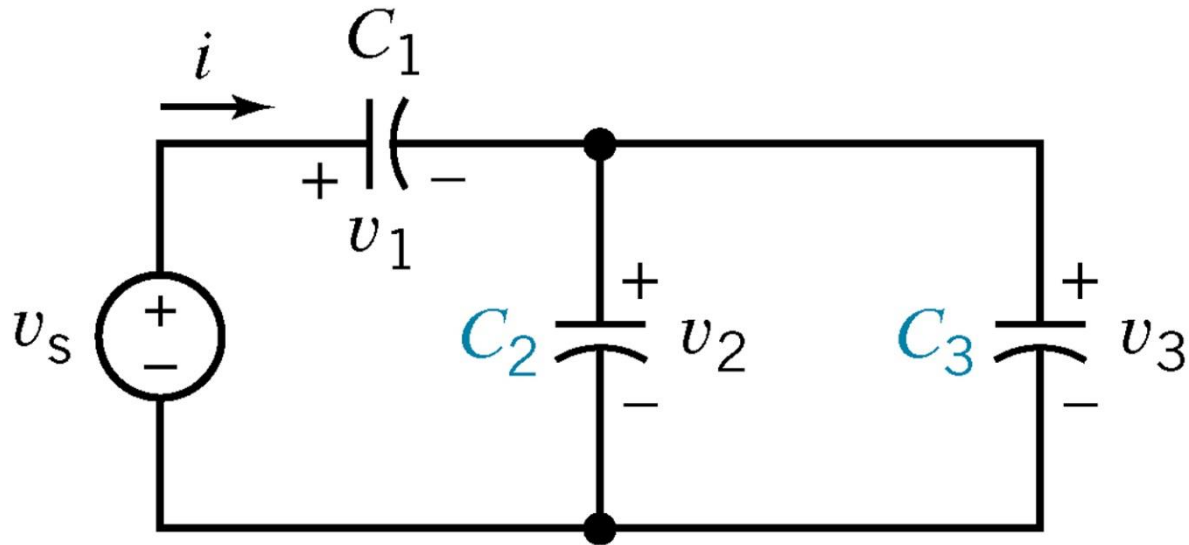Example 7.4-1

- Find the equivalent capacitance C_{eq} when $C_1 = C_2 = C_3 = 2 \text{ mF}$, $v_1(0) = 10 \text{ V}$ and $v_2(0) = v_3(0) = 20 \text{ V}$.







INDUCTANCE

<https://www.youtube.com/watch?v=KSylo01n5FY>

Inductance is a measure of the ability of a device to store energy the form of a magnetic field

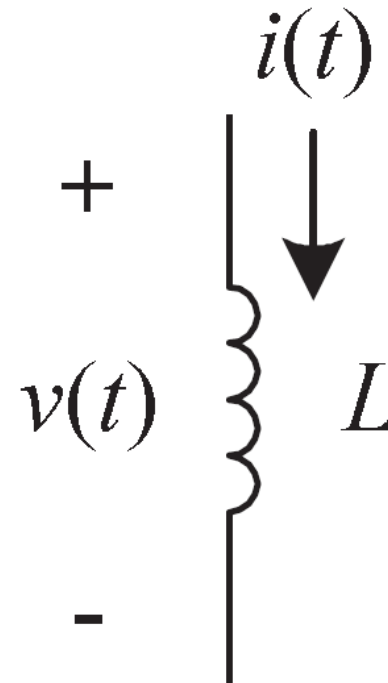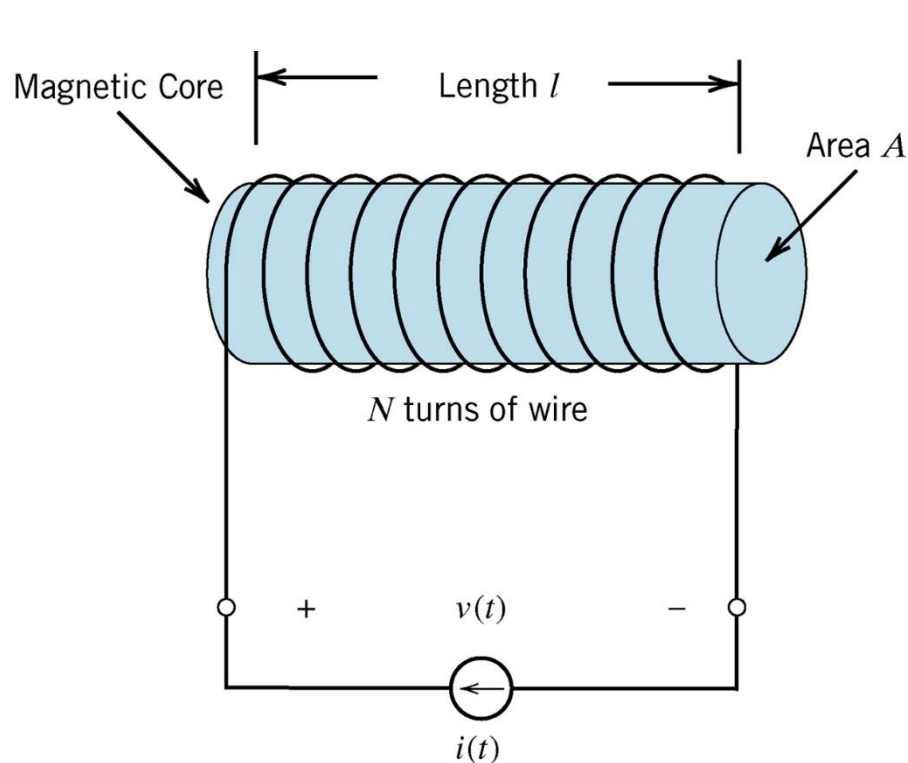- An inductor can be constructed by winding a coil of wire around a magnetic core (any magnetic material)
- Energy stored in the magnetic field created by current flowing through the wire



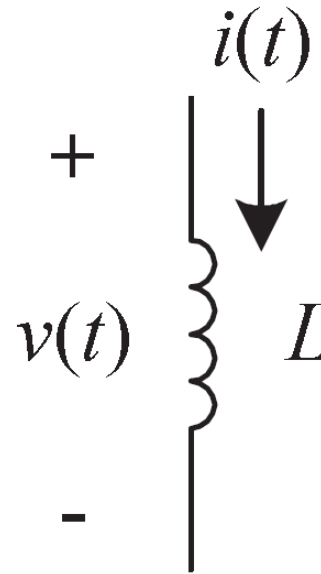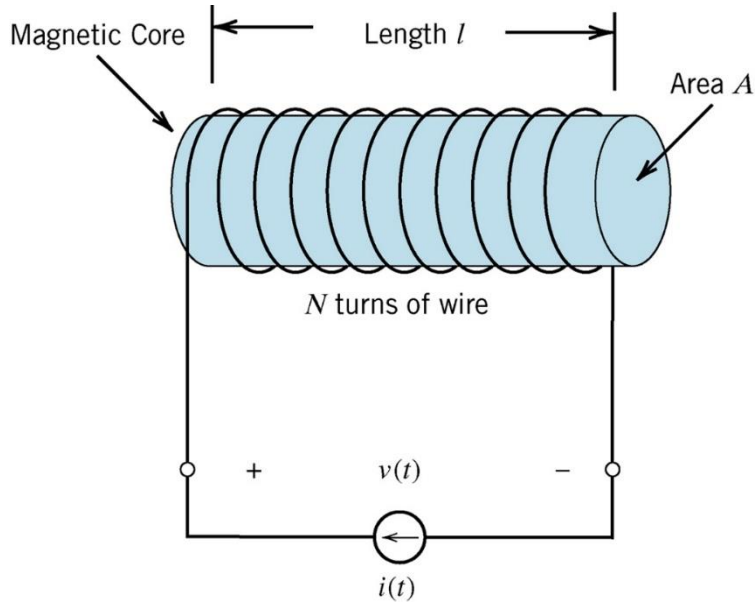

$$L = \frac{\mu N^2 A}{l}$$

L = Inductance in Henrys (H)

N = Number of turns


μ = Magnetic permeability of the core

A = Cross-sectional area (m^2)

l = Length (m)



Faraday's Law:

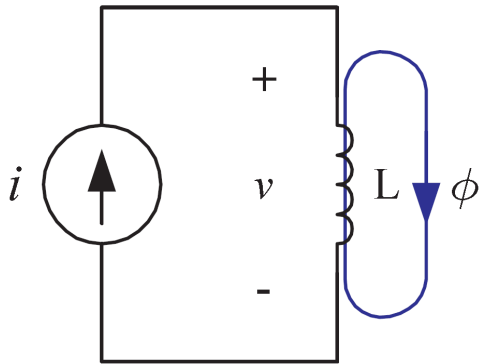

$$e = -\frac{d\psi}{dt}$$

$$\psi = N \cdot \phi$$

$$\phi = N \cdot \frac{\mu \cdot A}{l} \cdot i$$

$$\psi = N \cdot N \cdot \frac{\mu \cdot A}{l} \cdot i$$

$$= N^2 \frac{\mu \cdot A}{l} \cdot i$$


$$e = -\frac{d\left(N^2 \frac{\mu \cdot A}{l} \cdot i\right)}{dt}$$

$$= -N^2 \frac{\mu \cdot A}{l} \frac{di}{dt} = -L \frac{di}{dt}$$



$$v = L \frac{di}{dt}$$

I-V Relationship

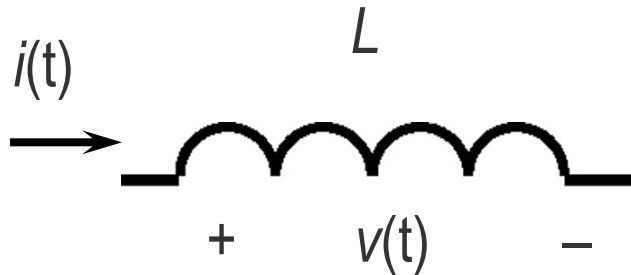

$$v(t) = L \frac{di(t)}{dt}$$

$$\Rightarrow v(\tau) \cdot d\tau = L \cdot di(\tau)$$

$$\Rightarrow \int_{t_0}^t v(\tau) \cdot d\tau = \int_{i(t_0)}^{i(t)} L \cdot di(\tau)$$

Initial time

$$\Rightarrow \int_{t_0}^t v(\tau) \cdot d\tau = L[i(t) - i(t_0)]$$

$$\Rightarrow i(t) = i(t_0) + \frac{1}{L} \int_{t_0}^t v(\tau) \cdot d\tau$$


Initial condition

Current in an inductor **CANNOT** change instantaneously

Example 7.5-1

- Find the voltage across an inductor, $L=0.1$ H, when the current in the inductor is:

$$i(t) = 20 \cdot t \cdot e^{-2t} \text{ A}, \quad t > 0, i(0) = 0$$

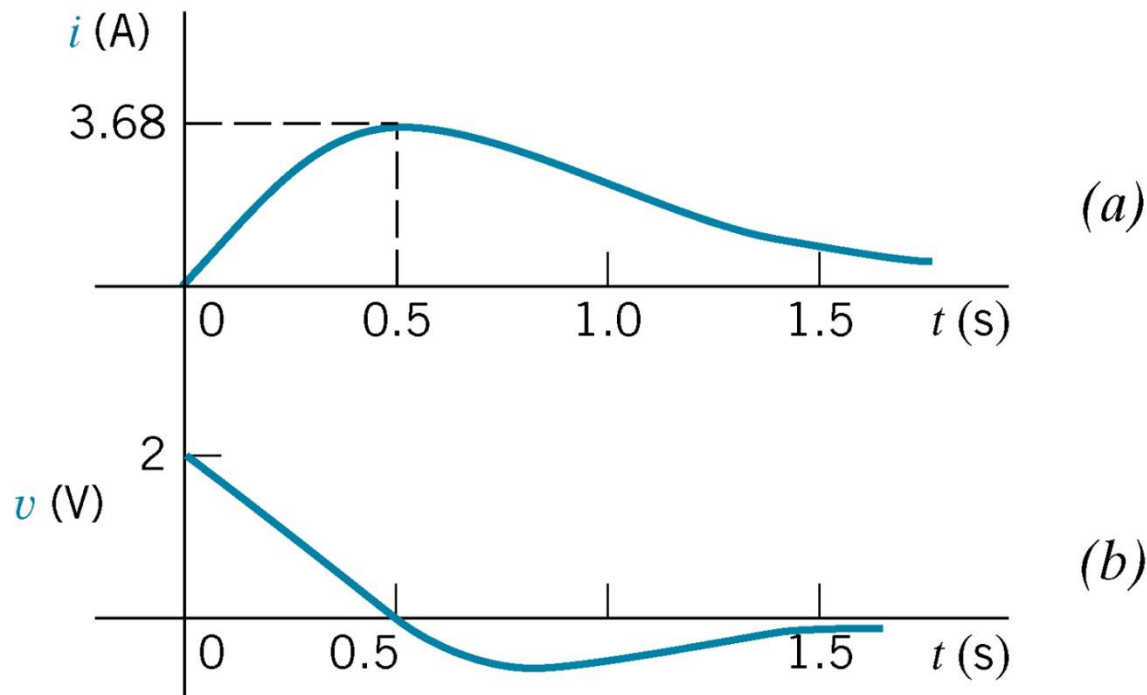


Example 7.5-3

- Calculate R and L if $i_L(0) = -3.5$ A, the input to the circuit is the voltage:


$$v(t) = 4 \cdot e^{-20t} \text{ V}, \quad t > 0$$

and the output is the current:
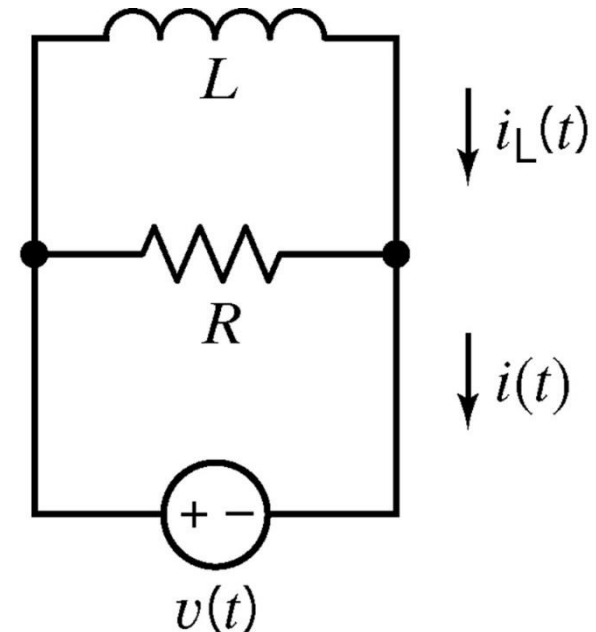
$$i(t) = -1.2 \cdot e^{-20t} - 1.5 \text{ A}, \quad t > 0$$



Power Stored in an Inductor

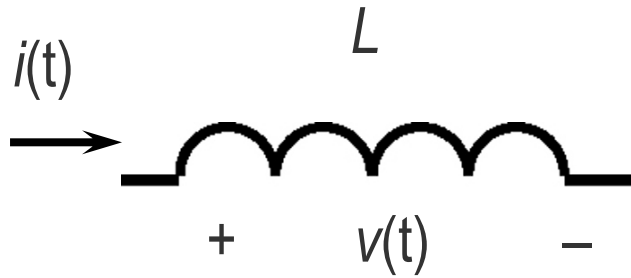


$$v(t) = L \frac{di(t)}{dt}$$

$$p(t) = v(t) \cdot i(t)$$
$$= L \frac{di(t)}{dt} \cdot i(t)$$

$$p(t) = L \cdot i(t) \frac{di(t)}{dt}$$

Energy Stored in an Inductor

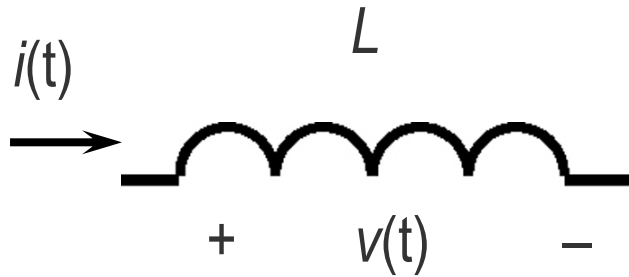

$$w(t) = \int_{-\infty}^t p(t) dt = \int_{-\infty}^t L \cdot i(t) \frac{di(t)}{dt} dt$$

$$= \int_{-\infty}^{i(t)} L \cdot i \cdot di = L \int_{-\infty}^{i(t)} i \cdot di$$


$$= \frac{1}{2} L \cdot i^2 \Big|_{i(-\infty)}^{i(t)}$$

$$= \frac{1}{2} L \cdot [i(t)^2 - i(-\infty)^2]$$



If the inductor is initially not magnetized: $i(-\infty) = 0$

$$w(t) = \frac{1}{2} L \cdot i(t)^2$$


Series & Parallel Inductors

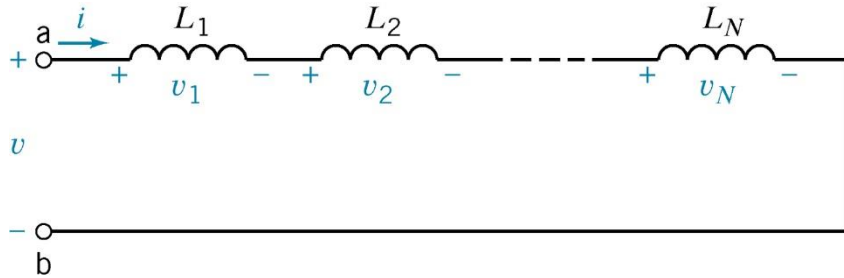
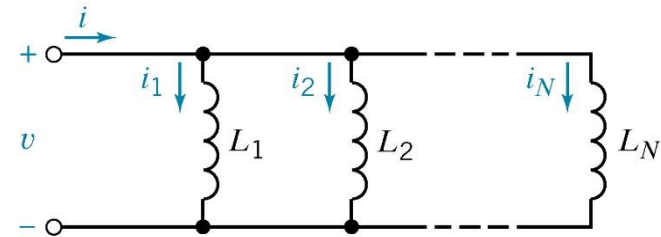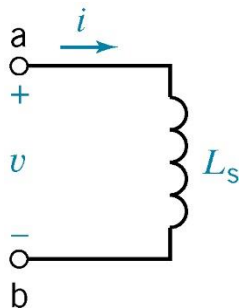
$$\begin{aligned}
 v &= v_1 + v_2 + v_3 + \dots + v_N \\
 &= L_1 \frac{di}{dt} + L_2 \frac{di}{dt} + \dots + L_N \frac{di}{dt} \\
 &= (L_1 + L_2 + \dots + L_N) \frac{di}{dt} \\
 v &= L_s \frac{di}{dt}
 \end{aligned}$$



$$\begin{aligned}
 i &= i_1 + i_2 + i_3 + \dots + i_N \\
 &= \frac{1}{L_1} \int_{t_0}^t v \cdot d\tau + \frac{1}{L_2} \int_{t_0}^t v \cdot d\tau + \dots + \frac{1}{L_N} \int_{t_0}^t v \cdot d\tau \\
 &= \left(\frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_N} \right) \int_{t_0}^t v \cdot d\tau \\
 i &= \frac{1}{L_p} \int_{t_0}^t v \cdot d\tau
 \end{aligned}$$

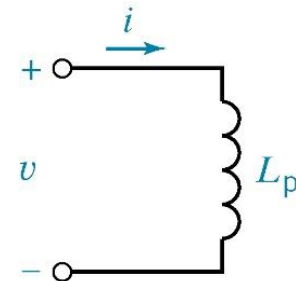

Example 7.7-1

- Find L_{eq} assuming that $i(0) = 0$ A.

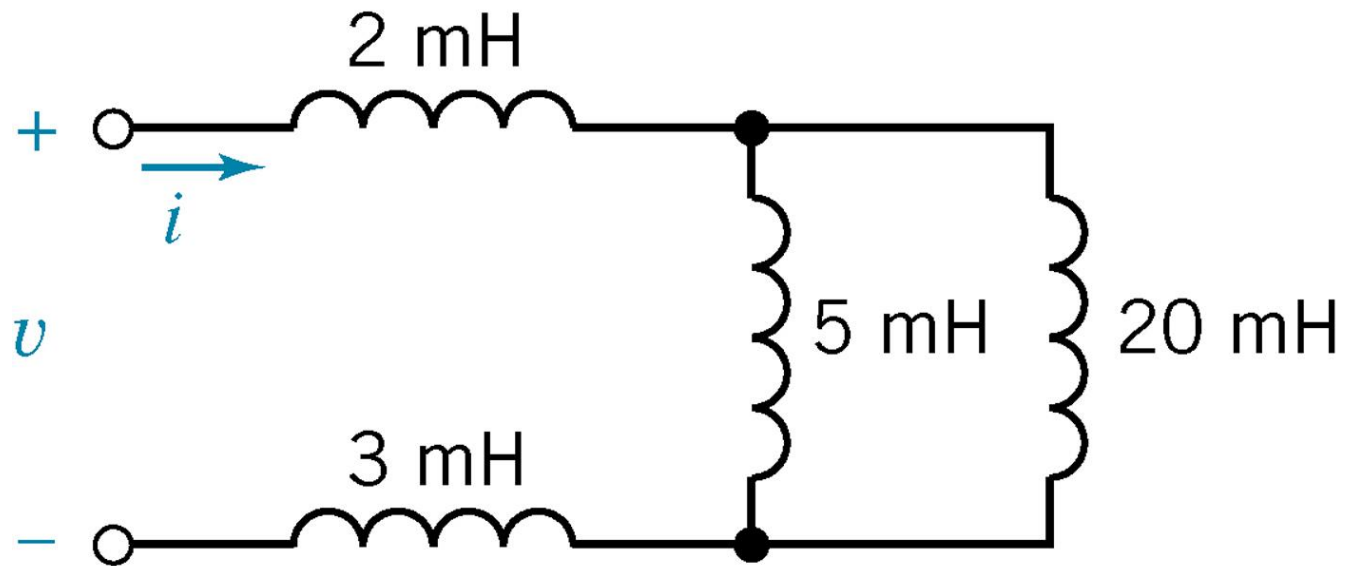
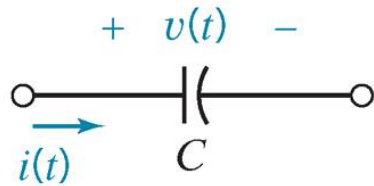
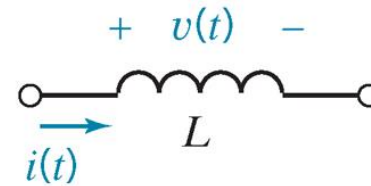


Table 7.13-1 Element Equations for Capacitors and Inductors**CAPACITOR**

$$i(t) = C \frac{d}{dt} v(t)$$

$$v(t) = \frac{1}{C} \int_{t_0}^t i(\tau) d\tau + v(t_0)$$









INDUCTOR

$$i(t) = \frac{1}{L} \int_{t_0}^t v(\tau) d\tau + i(t_0)$$

$$v(t) = L \frac{d}{dt} i(t)$$

Summary

Table 7.13-2 Parallel and Series Capacitors and Inductors

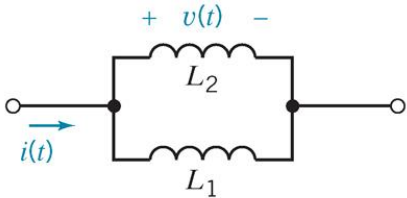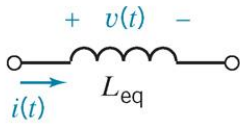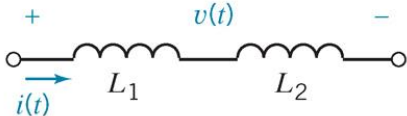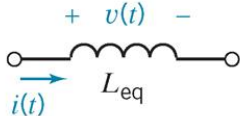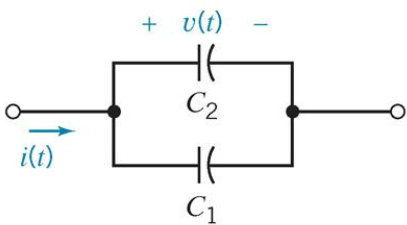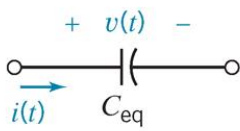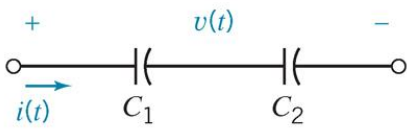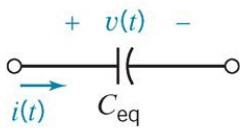SERIES OR PARALLEL CIRCUIT	EQUIVALENT CIRCUIT	EQUATION
		$L_{eq} = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2}}$
		$L_{eq} = L_1 + L_2$
		$C_{eq} = C_1 + C_2$
		$C_{eq} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2}}$