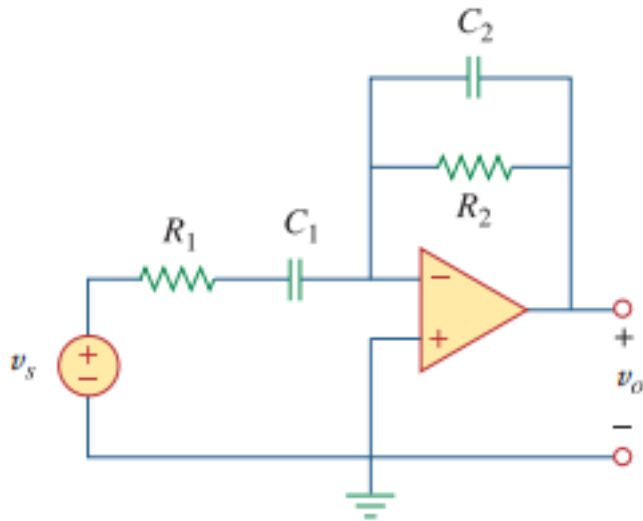


# Final Exam – Review

Spring 2018


# Problem 1

Compute the closed-loop gain and phase shift for the circuit in Fig. 10.33. Assume that  $R_1 = R_2 = 10 \text{ k}\Omega$ ,  $C_1 = 2 \text{ }\mu\text{F}$ ,  $C_2 = 1 \text{ }\mu\text{F}$ , and  $\omega = 200 \text{ rad/s}$ .




# Problem 2

Calculate  $i(t)$

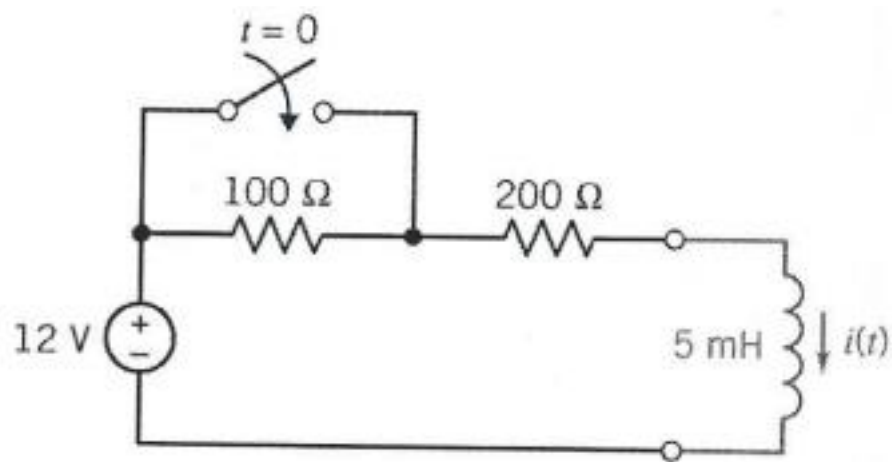


# Problem 3

Find the Thévenin equivalent circuit

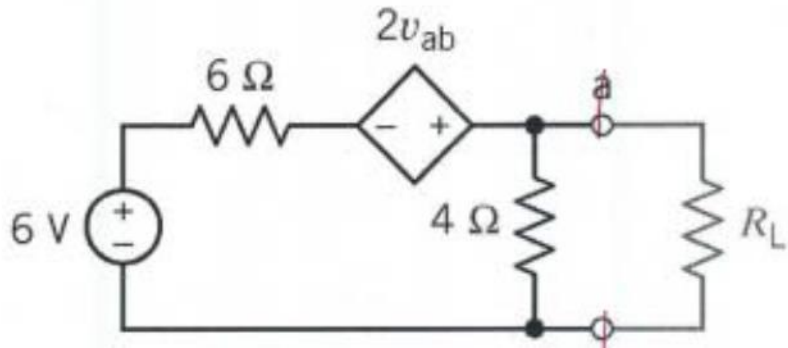


# Problem 4

Calculate node voltages

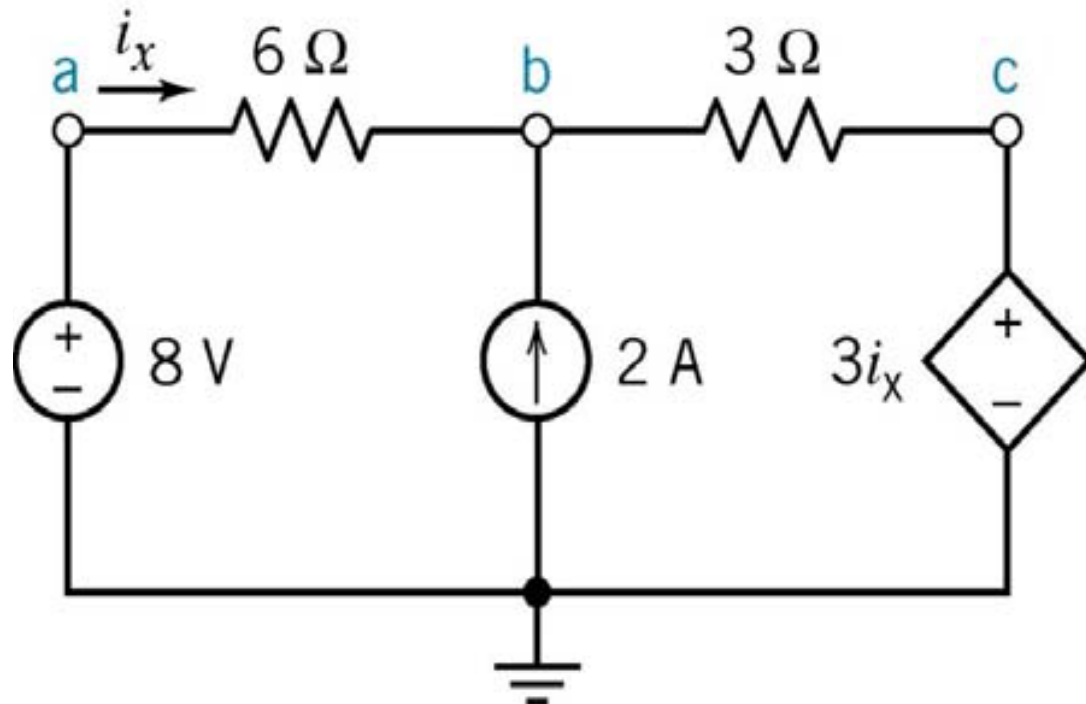

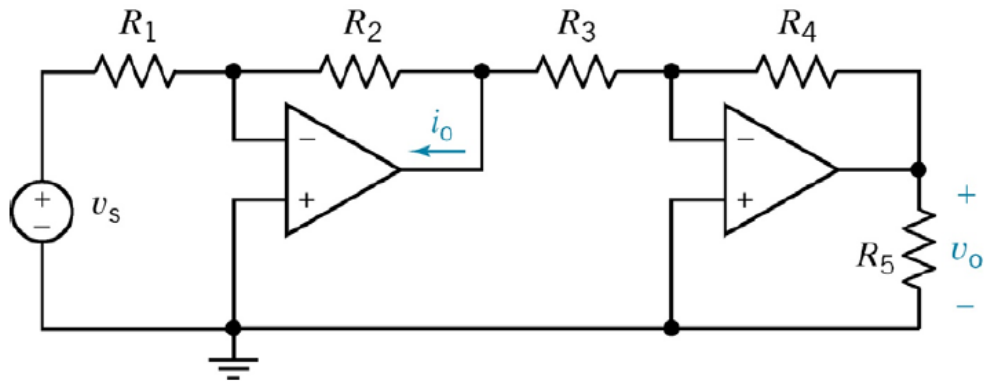
# Problem 5

Find  $i_o$  and  $v_o$  if  $v_s = 1\text{ V}$ ,  $R_1 = 10\ \Omega$ ,  $R_2 = 50\ \Omega$ ,  $R_3 = 20\ \Omega$  and  $R_4 = 80\ \Omega$



# Problem 6

Obtain the Norton equivalent circuit

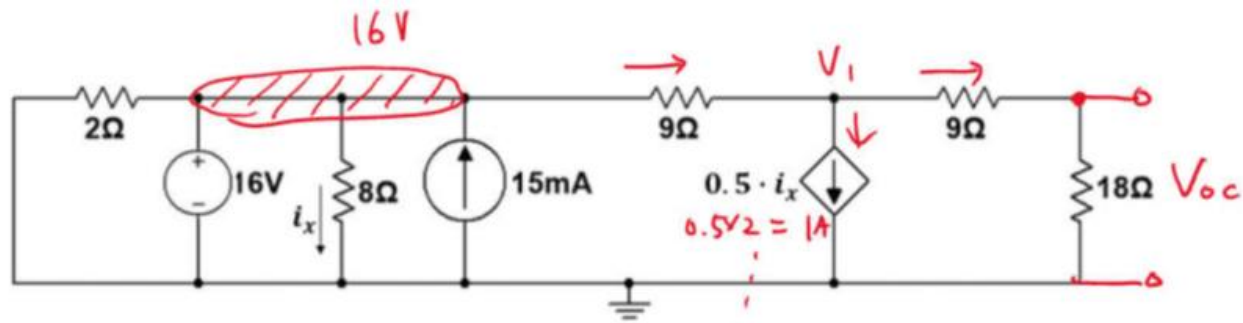

# Problem 7

Determine the steady-state voltage  $v(t)$  and current  $i(t)$  for the circuit below

