

# CPE201

# Digital Design

By Benjamin Haas

Class 21: Shift Registers



# Outline

- Flip-Flop Review
- Shift Register Intro
- 5 Types of shift register configurations
- Notes on real chips




# Flip-Flop Applications


- Data Storage
  - Ch8
- Frequency Division
- Counting
  - Ch9



# D Flip-Flop

 

 (a)  $D = 1$  flip-flop SETS on positive clock edge. (If already SET, it remains SET.)



(b)  $D = 0$  flip-flop RESETS on positive clock edge. (If already RESET, it remains RESET.)

Truth table for a positive edge-triggered D flip-flop.

Inputs		Outputs		Comments
$D$	CLK	$Q$	$\bar{Q}$	
0	↑	0	1	RESET
1	↑	1	0	SET

↑ = clock transition LOW to HIGH



# Shift Registers

- No set state machine
- Shift data in from external sources
- A series of flip-flops



  
# Register

- A digital circuit with 2 functions
  - Data storage



# Register

## – Data movement (4-bit examples)

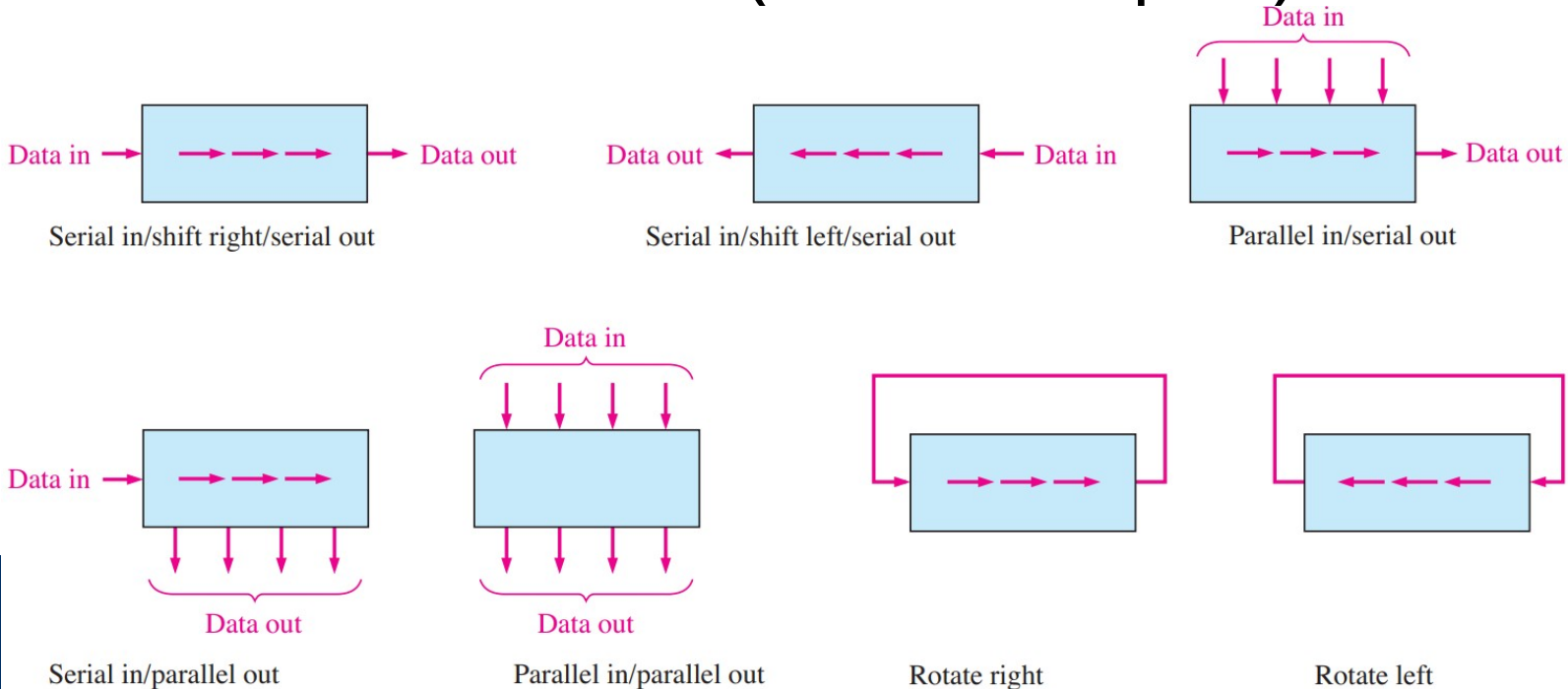

# Serial vs. Parallel

- Serial is one line
  - Connection count is small and takes little space
  - Used in long distance comms
- Parallel is one line per bit
  - Very fast because all bits are xferred at once
  - Takes up much more space than serial
  - Used in short distance comms (moving variables)





# Serial in / Serial out (SISO)

- Like a queue or buffer
  - Buffering in a long xfer line
- Destructive readout (all these regs do this)



Serial in/shift right/serial out




Serial in/shift left/serial out



# SISO Circuit

- Simplest version

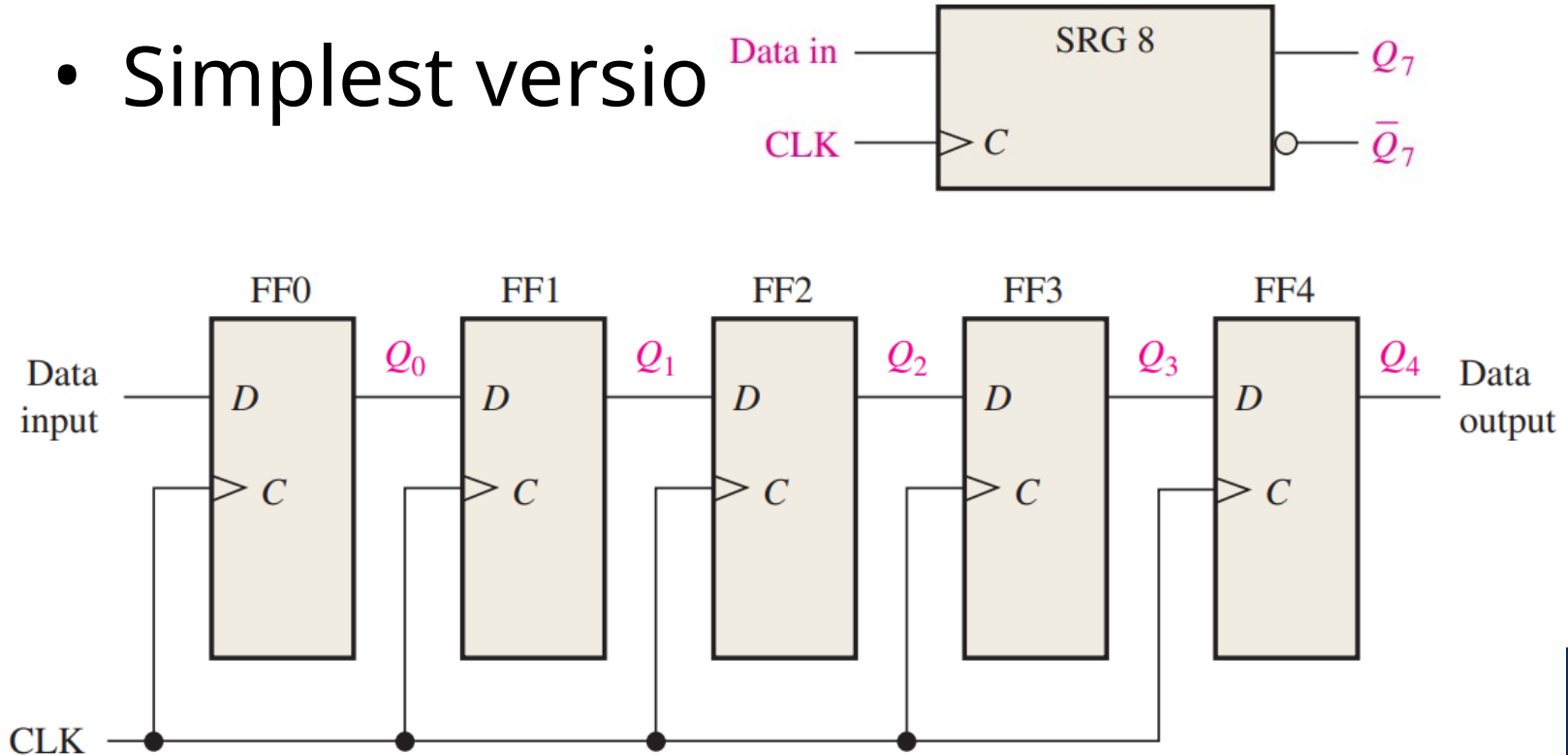

# SISO Data Table Example

Shifting a 4-bit code into the shift register  
Data bits are indicated by a beige screen.


CLK	FF0 ( $Q_0$ )	FF1 ( $Q_1$ )	FF2 ( $Q_2$ )	FF3 ( $Q_3$ )
Initial	0	0	0	0
1	0	0	0	0
2	1	0	0	0
3	0	1	0	0
4	1	0	1	0

Shifting a 4-bit code out of the shift register  
Data bits are indicated by a beige screen.

CLK	FF0 ( $Q_0$ )	FF1 ( $Q_1$ )	FF2 ( $Q_2$ )	FF3 ( $Q_3$ )
Initial	1	0	1	0
5	0	1	0	1
6	0	0	1	0
7	0	0	0	1
8	0	0	0	0




# SISO Signal Example

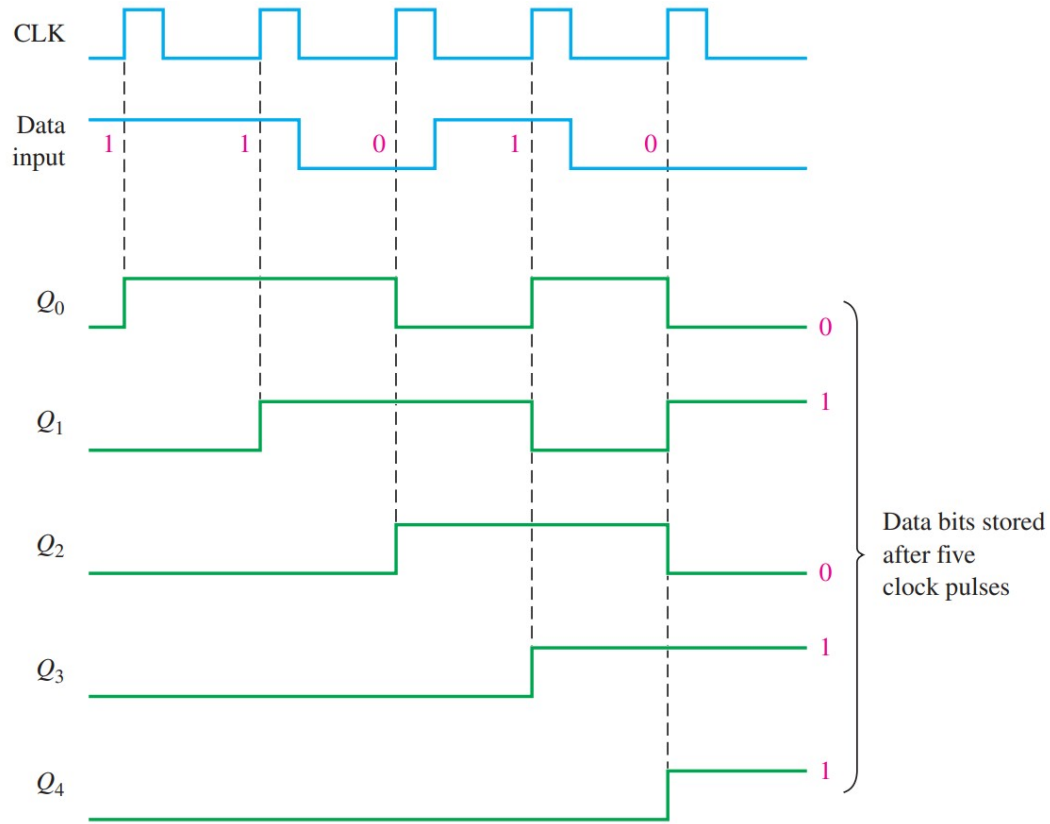
 
# Serial in / Parallel out (SIPO)



- Converts data format
- Receives data from serial bus and stores into variable




Serial in/parallel out

# SIPO Circuit

- Read all outputs at any time

  


# SIPO Signal Example

 
 
# Parallel in / Serial out (PISO)


- Converts data format
- Gets data ready to be xferred on serial bus



Parallel in/serial out




# PISO Circuit

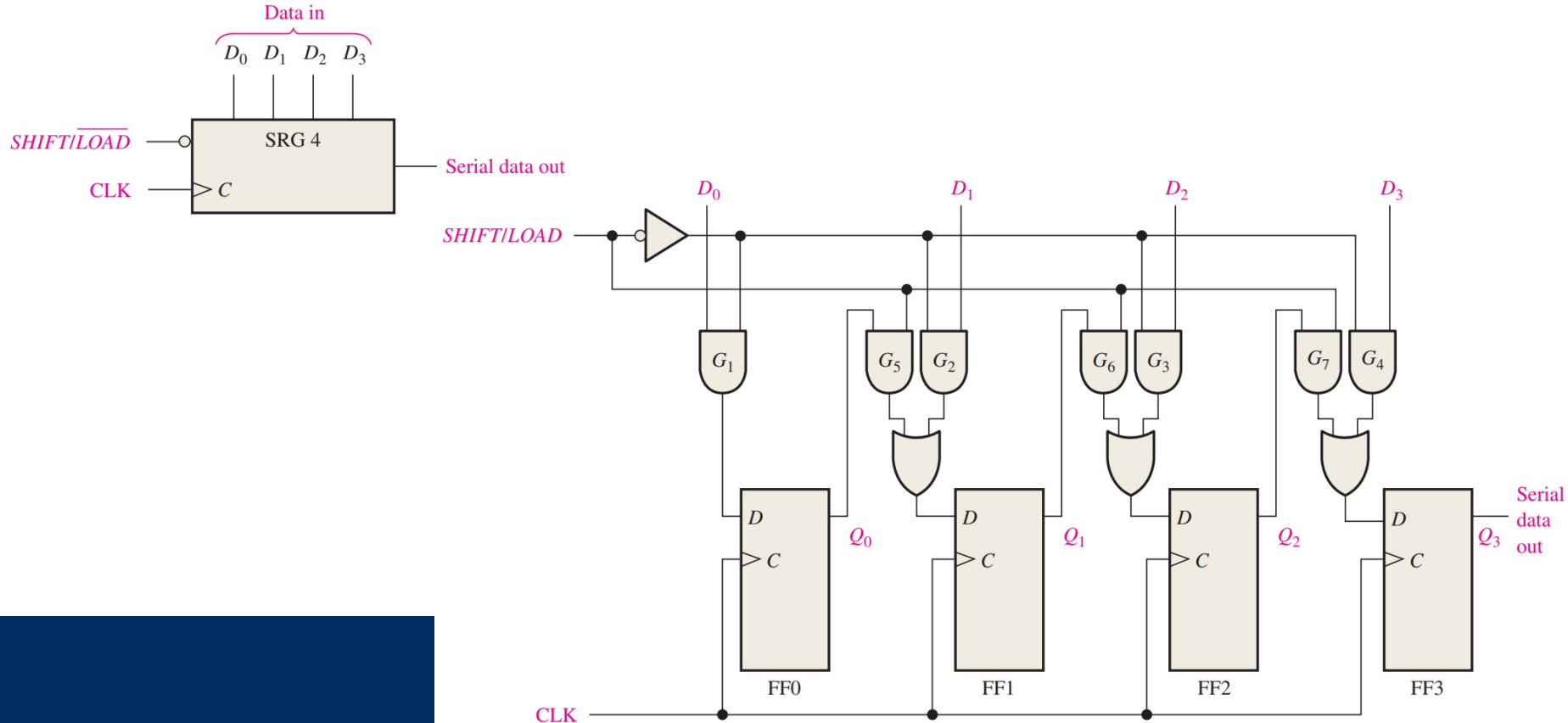


# PISO Signal Example

- || data is 0101

 
 
# Parallel in / Parallel out (PIPO)


- Move variables around
  - Between registers
  - Into/out of memory




Parallel in/parallel out



# PIPO Circuit

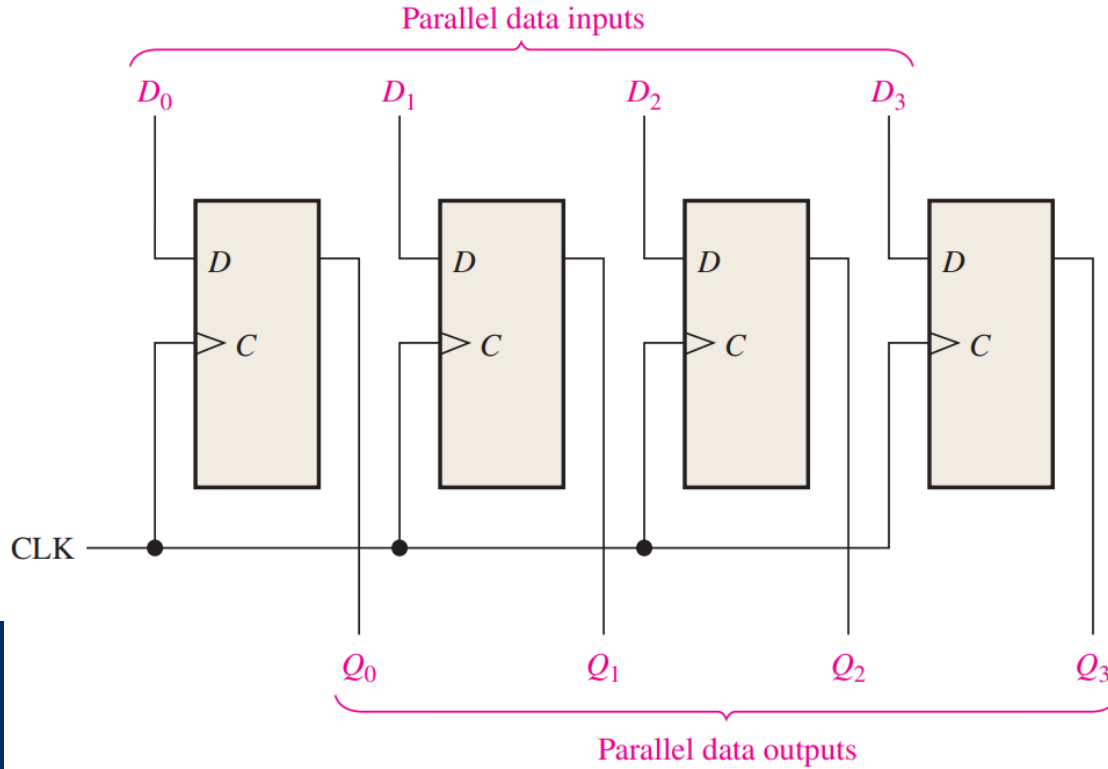

# PIPO Signal Example

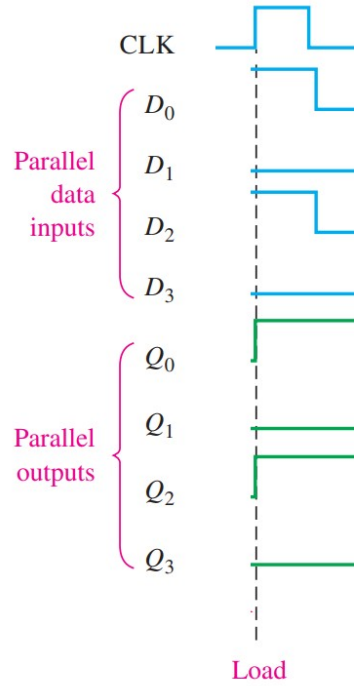


# Bit Rotation

- Usually bidirectional (data can go both directions)
  - Using direction input line



Rotate right

 


Rotate left

# Bit Rotation

- Shift 0100 to the left, get 1000 ( $0100 \ll 1$ )
  - What is that equivalent to?
- Shift 0100 to the right, get 0010 ( $0100 \gg 1$ )
  - What is that equivalent to?
- What is  $5 \ll 1$ ?  $7 \gg 1$ ?  $9 \gg 2$ ?  $1 \ll 4$ ?  $3 \gg 3$ ?




# Signal Example

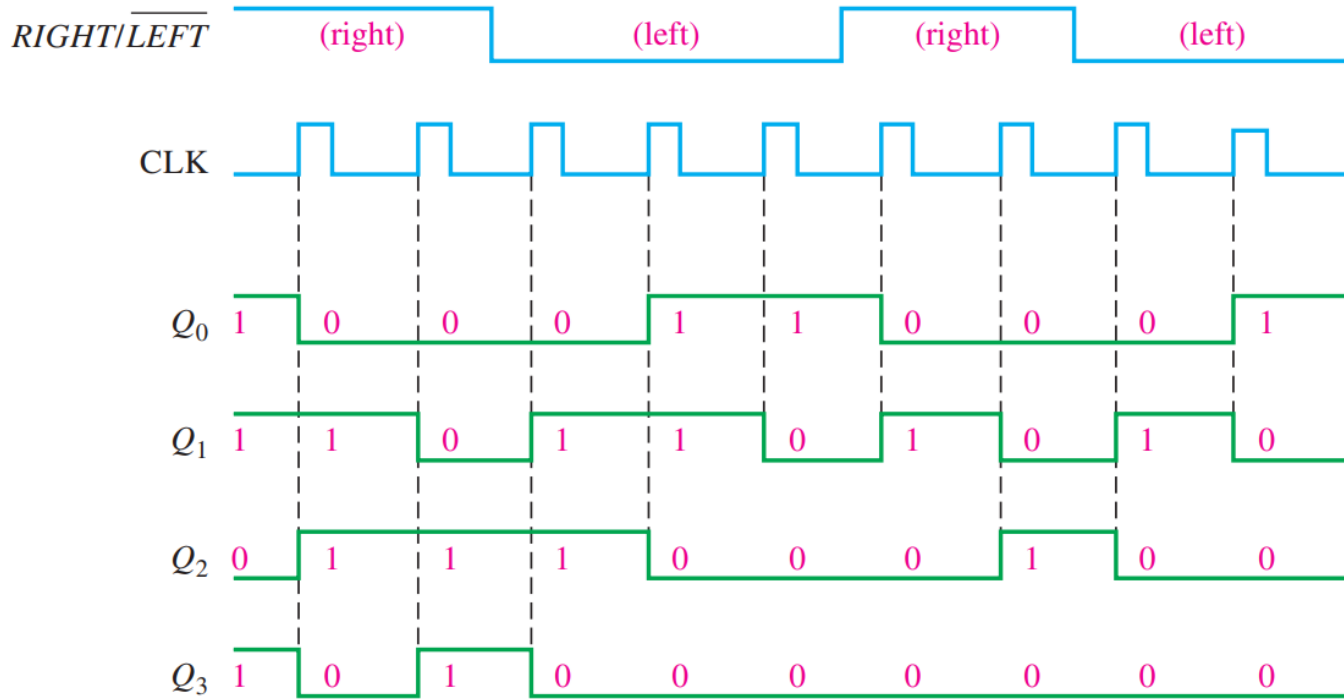



# Circuit

 

# Real Chips

- The real chips have additional functionality
  - PIPO and SIPO in one chip
  - SISO and PISO in one chip
  - SISO, SIPO, PISO, and PIPO in one chip
    - Universal shift register



# Reading

- This lecture
  - Sections 8.1-8.3
- Next lecture
  - Sections 8.4-8.7

