

Chapter 10 extra problems

P 10.3-9 For the circuit shown in Figure P 10.3-9, find (a) the impedances \mathbf{Z}_1 and \mathbf{Z}_2 in polar form, (b) the total combined impedance in polar form, and (c) the steady-state current $i(t)$.

Answer:

(a) $\mathbf{Z}_1 = 5 \angle 53.1^\circ$; $\mathbf{Z}_2 = 8\sqrt{2} \angle -45^\circ$

(b) $\mathbf{Z}_1 + \mathbf{Z}_2 = 11.7 \angle -20^\circ$

(c) $i(t) = (8.55) \cos(1250t + 20^\circ) \text{ A}$


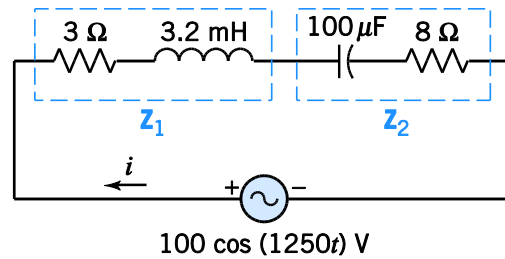


Figure P 10.3-9

Solution:

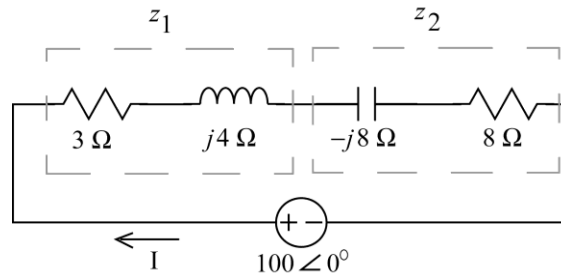

(a) $\underline{\mathbf{Z}_1 = 3 + j4 = 5 \angle 53.1^\circ \Omega}$ and $\underline{\mathbf{Z}_2 = 8 - j8 = 8\sqrt{2} \angle -45^\circ \Omega}$

(b) Total impedance = $\mathbf{Z}_1 + \mathbf{Z}_2 = 3 + j4 + 8 - j8 = 11 - j4 = \underline{11.7 \angle -20.0^\circ \Omega}$

(c) $\underline{\mathbf{I} = \frac{100 \angle 0^\circ}{\mathbf{Z}_1 + \mathbf{Z}_2} = \frac{100}{11.7 \angle -20^\circ} = \frac{100}{11.7} \angle 20.0^\circ \Rightarrow i(t) = 8.55 \cos(1250t + 20.0^\circ) \text{ A}}$

P 10.3-10 The circuit shown in Figure P 10.3-10 is at steady state. The voltages $v_s(t)$ and $v_2(t)$ are given by

$$v_s(t) = 7.68 \cos(2t + 47^\circ) \text{ V}$$

and

$$v_2(t) = 1.59 \cos(2t + 125^\circ) \text{ V}$$

Find the steady-state voltage $v_1(t)$.

Answer: $v_1(t) = 7.51 \cos(2t + 35^\circ) \text{ V}$

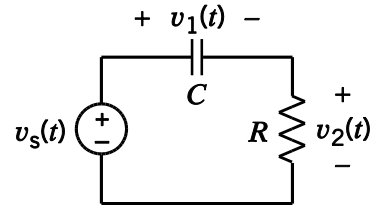


Figure P 10.3-10

Solution:

$$\begin{aligned} \mathbf{V}_1(\omega) &= \mathbf{V}_s(\omega) - \mathbf{V}_2(\omega) = 7.68\angle 47^\circ - 1.59\angle 125^\circ \\ &= (5.23 + j5.62) - (-0.91 + j1.30) \\ &= (5.23 + 0.91) + j(5.62 - 1.30) \\ &= 6.14 + j4.32 \\ &= 7.51\angle 35^\circ \\ v_1(t) &= 7.51 \cos(2t + 35^\circ) \text{ V} \end{aligned}$$

P 10.3-11 The circuit shown in Figure P 10.3-11 is at steady state. The currents $i_1(t)$ and $i_2(t)$ are given by

$$i_1(t) = 744 \cos(2t - 118^\circ) \text{ mA}$$

and

$$i_2(t) = 540.5 \cos(2t + 100^\circ) \text{ mA}$$

Find the steady-state current $i(t)$.

Answer: $i(t) = 460 \cos(2t + 196^\circ) \text{ mA}$

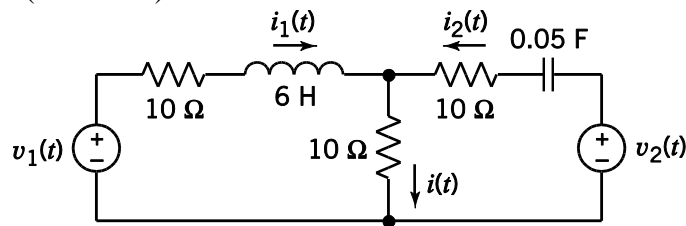


Figure P 10.3-11

Solution:

$$\begin{aligned} \mathbf{I} &= \mathbf{I}_1 + \mathbf{I}_2 = 0.744\angle -118^\circ + 0.5405\angle 100^\circ = (-0.349 - j0.657) + (-0.094 + j0.532) \\ &= (-0.349 - 0.094) + j(-0.657 + 0.532) \\ &= -0.443 - j0.125 \\ &= 0.460\angle 196^\circ \end{aligned}$$

$$i(t) = 460 \cos(2t + 196^\circ) \text{ mA}$$

P 10.3-12 Determine $i(t)$ of the RLC circuit shown in Figure P 10.3-12 when

$$v_s = 2 \cos(4t + 30^\circ) \text{ V.}$$

Answer: $i(t) = 0.185 \cos(4t - 26.3^\circ) \text{ A}$


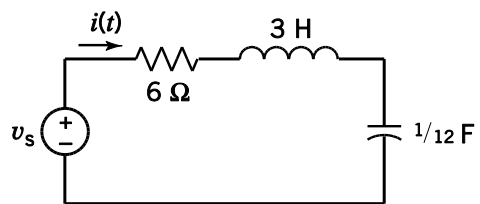


Figure P 10.3-12

Solution:

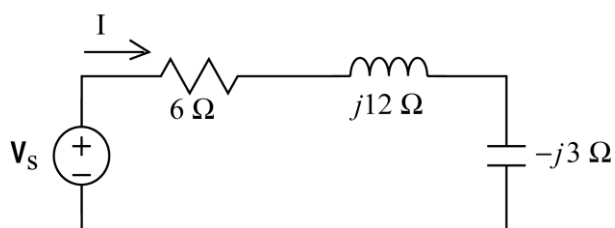


$$\mathbf{V}_s = 2 \angle 30^\circ \text{ V}$$

$$\text{and } \mathbf{I} = \frac{2 \angle 30^\circ}{6 + j12 + 3/j} = 0.185 \angle -26.3^\circ \text{ A}$$

$$\underline{i(t) = 0.185 \cos(4t - 26.3^\circ) \text{ A}}$$

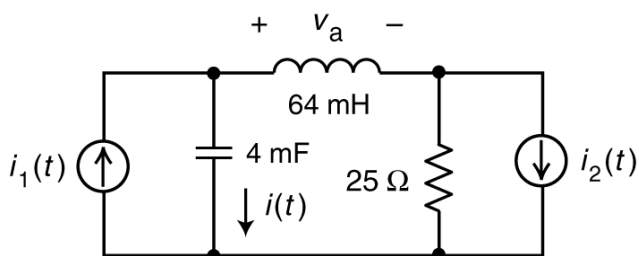P10.4-3 Represent the circuit shown in Figure P10.4-3 in the frequency domain using impedances and phasors.




$$i_1(t) = 400 \cos(25t - 24^\circ) \text{ mA}$$

$$i_2(t) = 750 \cos(25t + 60^\circ) \text{ mA}$$

Figure P10.4-3

Solution:

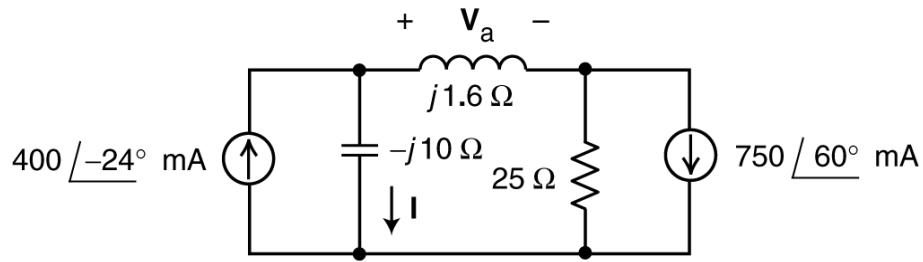

P10.4-7 The input to the circuit shown in Figure P10.4-7 is the current

$$i(t) = 82 \cos(10000t) \text{ } \mu\text{A}$$

Determine the voltage, $v(t)$, across the $50 \text{ k}\Omega$ resistor.


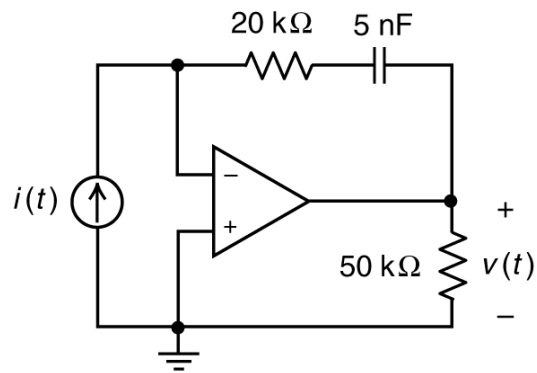


Figure P10.4-7

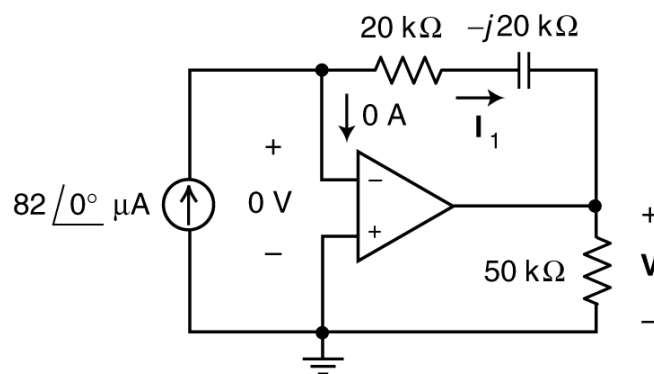Solution: Represent the circuit in the frequency domain using phasors and impedances:



Using KCL

$$82 \times 10^{-6} \angle 0^\circ = 0 + \mathbf{I}_1$$

Using KVL


$$(20 \times 10^3) \mathbf{I}_1 + (-j 20 \times 10^3) \mathbf{I}_1 + \mathbf{V} = 0$$

$$\mathbf{V} = -(20 \times 10^3 - j 20 \times 10^3)(82 \times 10^{-6}) = 2.3193 \angle 135^\circ \text{ V}$$

In the time domain


$$v(t) = 2.3193 \cos(10000t + 135^\circ) \text{ V}$$

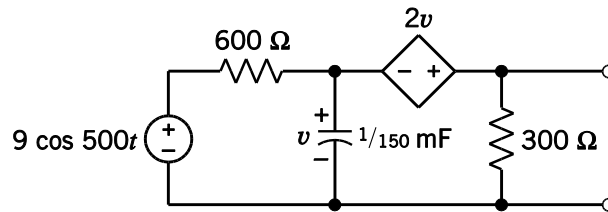P10.7-3 Determine the Thevenin equivalent of this circuit



Solution:

First, determine \mathbf{V}_{oc} :

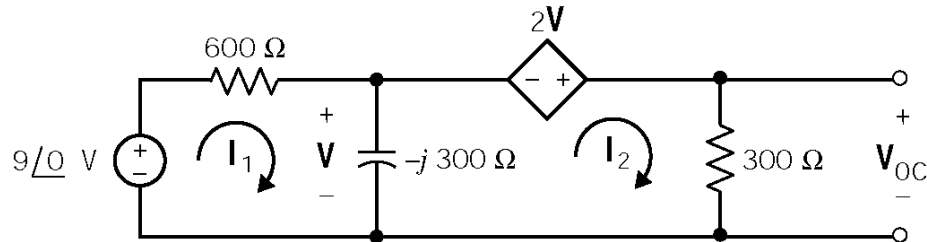

The mesh equations are

$$600 \mathbf{I}_1 - j300(\mathbf{I}_1 - \mathbf{I}_2) = 9 \Rightarrow (600 - j300) \mathbf{I}_1 + j300 \mathbf{I}_2 = 9 \angle 0^\circ$$

$$-2\mathbf{V} + 300 \mathbf{I}_2 - j300(\mathbf{I}_1 - \mathbf{I}_2) = 0 \quad \text{and} \quad \mathbf{V} = j300(\mathbf{I}_1 - \mathbf{I}_2) \Rightarrow j3 \mathbf{I}_1 + (1 - j3) \mathbf{I}_2 = 0$$


Using Cramer's rule:

$$\mathbf{I}_2 = 0.0124 \angle -16^\circ \text{ A}$$

Then

$$\mathbf{V}_{oc} = 300 \mathbf{I}_2 = 3.71 \angle -16^\circ \text{ V}$$

Next, determine \mathbf{I}_{sc} :

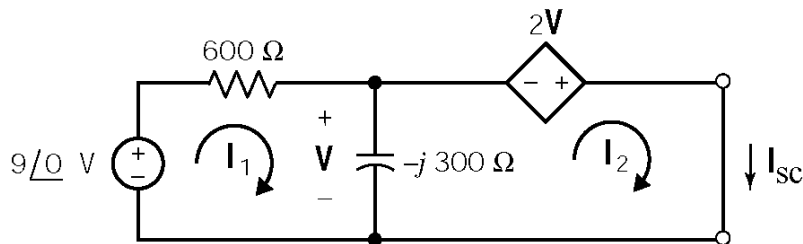


$$-2\mathbf{V} - \mathbf{V} = 0 \Rightarrow \mathbf{V} = 0 \Rightarrow \mathbf{I}_{sc} = \frac{9 \angle 0^\circ}{600} = 0.015 \angle 0^\circ \text{ A}$$


The Thevenin impedance is

$$\mathbf{Z}_T = \frac{\mathbf{V}_{oc}}{\mathbf{I}_{sc}} = \frac{3.545 \angle -16^\circ}{0.015 \angle 0^\circ} = 247 \angle -16^\circ \Omega$$

The Thevenin equivalent is

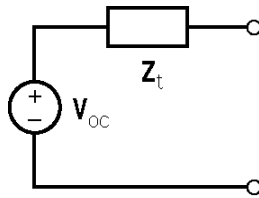

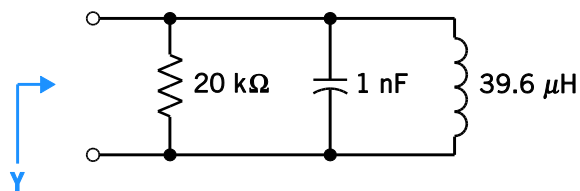P10.7-5 Determine the frequency at which \mathbf{Y} is a pure conductance



Solution:


$$\mathbf{Y} = \mathbf{G} + \mathbf{Y}_L + \mathbf{Y}_C$$

$$\mathbf{Y} = \mathbf{G} \text{ when } \mathbf{Y}_L + \mathbf{Y}_C = 0 \text{ or } \frac{1}{j\omega L} + j\omega C = 0$$


$$\omega_o = \frac{1}{\sqrt{LC}}, f_o = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{39.6 \times 10^{-15}}}$$

$$= 0.07998 \times 10^7 \text{ Hz} = 800 \text{ kHz}$$

(80 on the dial of the radio)

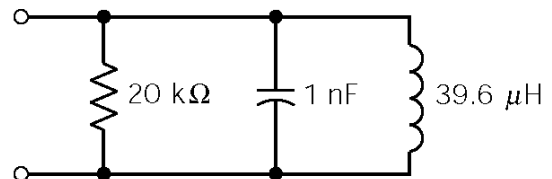


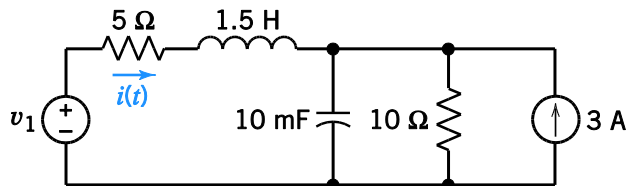P10.8-9 Determine the current $i(t)$ for this circuit when $v_1(t) = 10\cos(10t)$ V



Solution:

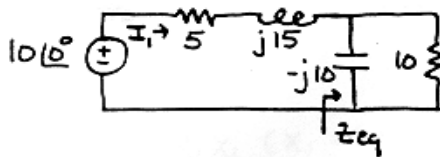Use superposition. First, find the response to the voltage source acting alone:



$$\mathbf{Z}_{eq} = \frac{-j10 \cdot 10}{10 - j10} = 5(1 - j) \Omega$$


Replacing the parallel elements by the equivalent impedance. Then write a mesh equation :

$$-10 + 5 \mathbf{I}_1 + j15 \mathbf{I}_1 + 5(1 - j) \mathbf{I}_1 = 0 \Rightarrow \mathbf{I}_1 = \frac{10}{10 + j10} = 0.707 \angle -45^\circ \text{ A}$$

Therefore:

$$i_1(t) = 0.707 \cos(10t - 45^\circ) \text{ A}$$

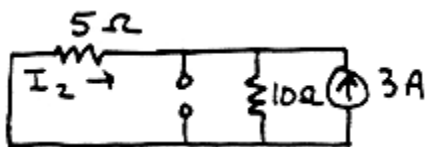Next, find the response to the dc current source acting alone:



Current division: $I_2 = -\frac{10}{15} \times 3 = -2 \text{ A}$

Using superposition:

$$i(t) = 0.707 \cos(10t - 45^\circ) - 2 \text{ A}$$

P10.10-1 The input to the circuit shown in Figure P10.10-1 is the voltage

$$v_s(t) = 2.4 \cos(500t) \text{ V}.$$

Determine the output voltage $v_o(t)$.

Answer: $v_o(t) = 6.788 \cos(500t + 135^\circ) \text{ V}$


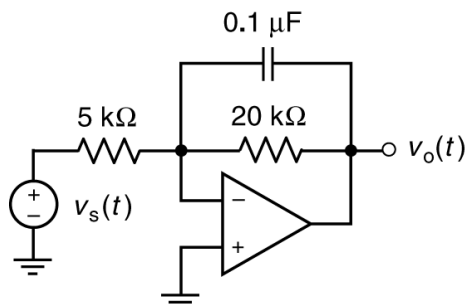


Figure P10.10-1

Solution:

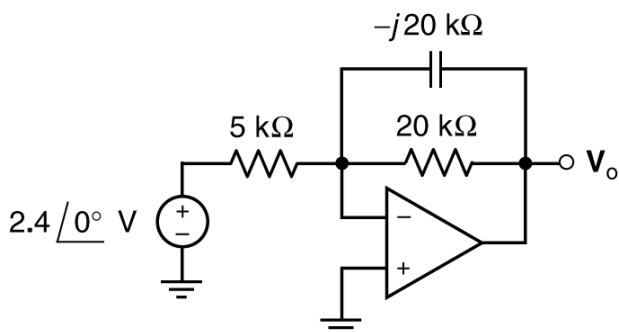Represent the circuit in the frequency domain as



Recognizing this circuit as an inverting amplifier, we can write

$$\mathbf{V}_o = \left(-\frac{20 \parallel -j20}{5} \right) (2.4 \angle 0^\circ) = \left((1 \angle 180^\circ) \frac{14.14 \angle -45^\circ}{5} \right) (2.4 \angle 0^\circ) = 6.788 \angle 135^\circ \text{ V}$$

In the time domain

$$v_o(t) = 6.788 \cos(500t + 135^\circ) \text{ V}$$

(Checked using LNAPAC 3/15/12)

P10.10-2 The input of the circuit shown in Figure P10.10-2 is the voltage

$$v_s(t) = 1.2 \cos(400t + 20^\circ) \text{ V}.$$

Determine the output voltage $v_o(t)$.


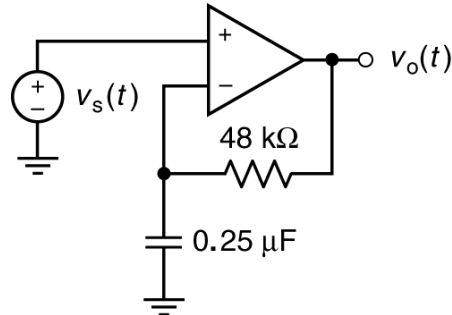


Figure P10.10-2

Solution:

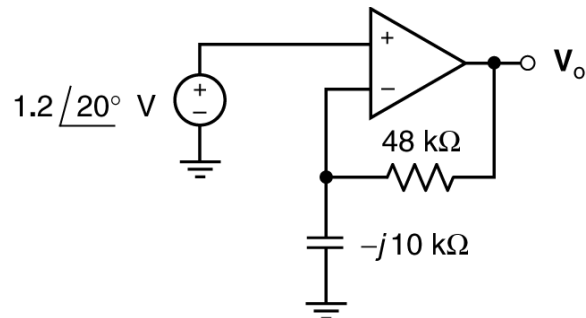Represent the circuit in the frequency domain as



Recognizing this circuit as a noninverting amplifier, we can write

$$\mathbf{V}_o = \left(1 + \frac{48}{-j10} \right) (1.2 \angle 20^\circ) = (1 + j4.8)(1.2 \angle 20^\circ) = 5.88 \angle 98^\circ \text{ V}$$

In the time domain

$$v_o(t) = 5.88 \cos(400t + 98^\circ) \text{ V}$$