

Answer all questions completely. Put a box around the final solution. Put your name on it. Show your work.

By hand:

1. Create a truth table for the following expressions:

a. $AB'C + A'B$

A	B	C	B'	AB'C	A'	A'B	Output
0	0	0	1	0	1	0	0
0	0	1	1	0	1	0	0
0	1	0	0	0	1	1	1
0	1	1	0	0	1	1	1
1	0	0	1	0	0	0	0
1	0	1	1	1	0	0	1
1	1	0	0	0	0	0	0
1	1	1	0	0	0	0	0

b. $(A + BC')(A' + C)$


A	B	C	C'	BC'	A+BC'	A'	A'+C	Output
0	0	0	1	0	0	1	1	0
0	0	1	0	0	0	1	1	0
0	1	0	1	1	1	1	1	1
0	1	1	0	0	0	1	1	0
1	0	0	1	0	1	0	0	0
1	0	1	0	0	1	0	1	1
1	1	0	1	1	1	0	0	0
1	1	1	0	0	1	0	1	1

c. $(A + B)'C'$

A	B	C	A+B	(A+B)'	C'	Output
0	0	0	0	1	1	1
0	0	1	0	1	0	0
0	1	0	1	0	1	0
0	1	1	1	0	0	0
1	0	0	1	0	1	0
1	0	1	1	0	0	0
1	1	0	1	0	1	0
1	1	1	1	0	0	0

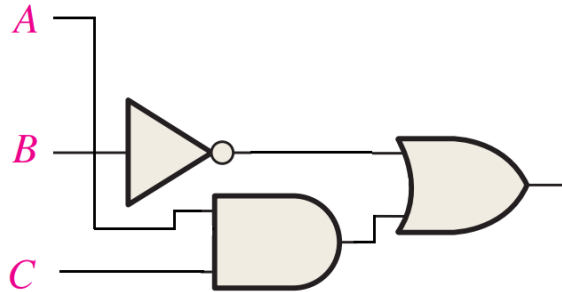
2. Draw the logic circuit represented by the following expressions:
a. $A + B(C' + D(B' + AC))$

Start at the inside most parentheses to create $B' + AC$




D

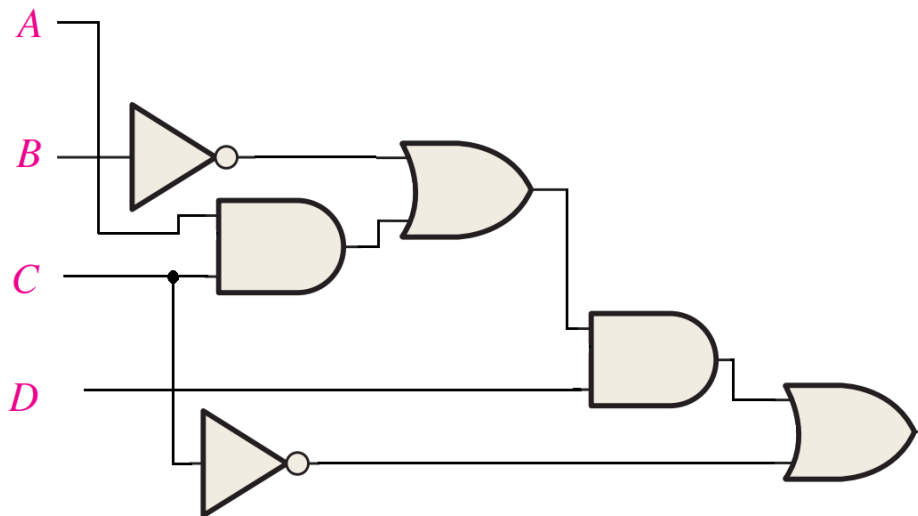Now add the circuitry for the next parenthesis out to create $C' + D(B' + AC)$



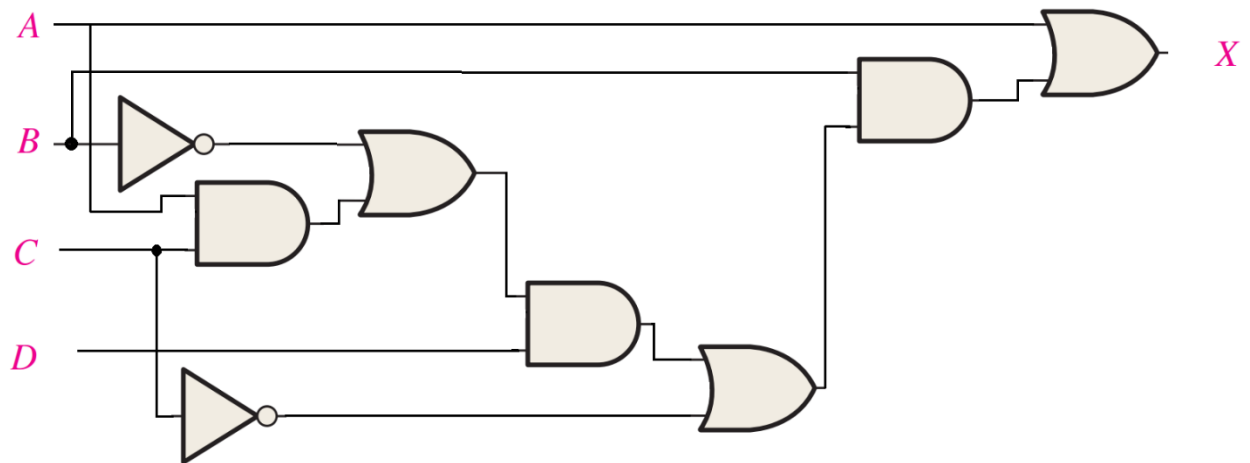Add the remaining logic to get the complete circuit




b. $AB'(C' + D)$


Starting from the inside of the expression, for $C' + D$:

A

B

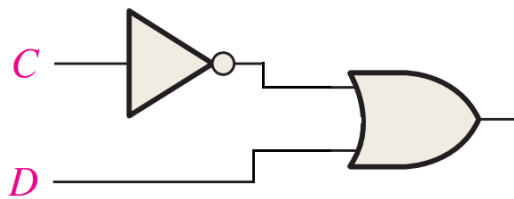

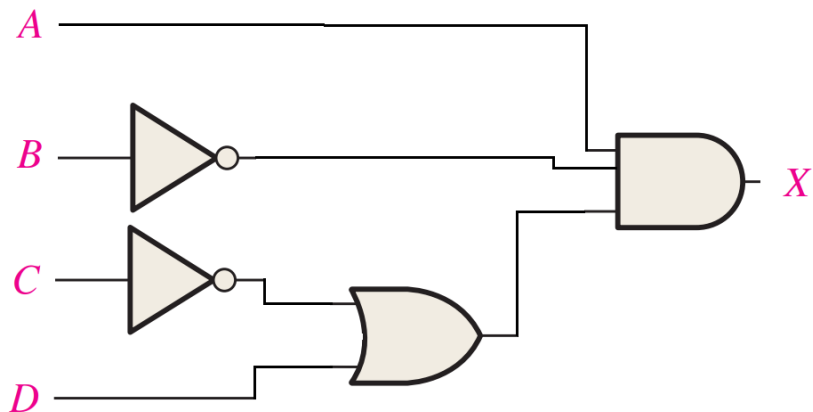Now creating the AND of the other pieces gives the final circuit



3. Convert the following expression to SOP form: $A + B(C' + D(B' + AC))$

Create the truth table for the expression

A	B	C	D	AC	B'	B'+AC	D(B'+AC)	C'	C' + D(B' + AC)	B(C' + D(B' + AC))	Output
0	0	0	0	0	1	1	0	1	1	0	0
0	0	0	1	0	1	1	1	1	1	0	0
0	0	1	0	0	1	1	0	0	0	0	0
0	0	1	1	0	1	1	1	0	1	0	0
0	1	0	0	0	0	0	0	1	1	1	1
0	1	0	1	0	0	0	0	1	1	1	1
0	1	1	0	0	0	0	0	0	0	0	0
0	1	1	1	0	0	0	0	0	0	0	0
1	0	0	0	0	1	1	0	1	1	0	1
1	0	0	1	0	1	1	1	1	1	0	1
1	0	1	0	1	1	1	0	0	0	0	1
1	0	1	1	1	1	1	1	0	1	0	1
1	1	0	0	0	0	0	0	1	1	1	1
1	1	0	1	0	0	0	0	1	1	1	1
1	1	1	0	1	0	1	0	0	0	0	1
1	1	1	1	1	0	1	1	0	1	1	1

Convert the truth table to a Karnaugh map

$AB \backslash CD$		00	01	11	10
		00	01	11	10
00		0	0	0	0
01		1	1	0	0
11		1	1	1	1
10		1	1	1	1

Circle the groupings of 1's to create the SOP expression

$AB \backslash CD$		00	01	11	10
		00	01	11	10
00		0	0	0	0
01		1	1	0	0
11		1	1	1	1
10		1	1	1	1

Writing the SOP expressions for the two circles gives the answer:
 $A + BC'$

4. For the following truth table, derive the standard SOP and standard POS expressions.

A	B	C	D	Output
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	1

For standard SOP, we write the SOP expressions for each 1 in the truth table
 $A'B'C'D' + A'B'C'D + A'B'CD' + A'B'CD + AB'C'D' + AB'C'D + ABCD' + ABCD$

For standard POS, we write the POS expressions for each 0 in the truth table
 $(A+B'+C+D)(A+B'+C+D')(A+B'+C'+D)(A+B'+C'+D')(A'+B+C'+D)(A'+B+C'+D')(A'+B'+C+D)(A'+B'+C+D')$

5. Create a Karnaugh map for the following expression, then find the minimum SOP expression using the Karnaugh map: $(A + B')(A + B + C')(B + C)$

This POS expression gives all of the 0 locations in the Karnaugh map. You can convert directly or create a truth table like this one.

A	B	C	B'	A+B'	C'	A+B+C'	B+C	Output
0	0	0	1	1	1	1	0	0
0	0	1	1	1	0	0	1	0
0	1	0	0	0	1	1	1	0
0	1	1	0	0	0	1	1	0
1	0	0	1	1	1	1	0	0
1	0	1	1	1	0	1	1	1

1	1	0	0	1	1	1	1	1
1	1	1	0	1	0	1	1	1

Convert the truth table to a Karnaugh map

$AB \backslash C$		0	1
00	0	0	
01	0	0	
11	1	1	
10	0	1	

Circle the groupings of 1's to create the SOP expression

$AB \backslash C$		0	1
00	0	0	
01	0	0	
11	1	1	
10	0	1	

Writing the SOP expressions for the two circles gives the answer:
 $AB + AC$

